

# Demystifying the Operational Transconductance Amplifier

Xavier Ramus

High-Speed Products

## ABSTRACT

Operational transconductance amplifiers (OTAs) are often among the least understood analog components. However, these devices serve a very useful function that is being implemented on a regular basis in many integrated circuits as an element for more advanced purposes; the current feedback amplifier is among the most prominent example. The purpose of this application report is to show how this building block operates. It also develops several examples of how this type of component can be put to good use for many applications.

## Contents

|   |   |   |
|---|---|---|
| 1 | Operational Transconductance Overview ..... | 1 |
| 2 | Direct Use of an OTA .....                  | 3 |
| 3 | Advanced Uses of OTA Architecture.....      | 6 |
| 4 | Advanced OTA Circuits .....                 | 9 |

## List of Figures

|    |  |    |
|----|--|----|
| 1  | Typical OTA Elements and Accepted References .....           | 2  |
| 2  | Basic OTA Circuit Architecture .....                         | 2  |
| 3  | Voltage Mode: Common-E Amplifier .....                       | 3  |
| 4  | Voltage Mode: Common-C Amplifier.....                        | 4  |
| 5  | Voltage Mode: Common-B Amplifier .....                       | 4  |
| 6  | Typical CFB Amplifier Block Diagram.....                     | 6  |
| 7  | Control-Loop Amplifier Circuit Model.....                    | 6  |
| 8  | DC-Restore Circuit Example with the OPA615 .....             | 7  |
| 9  | DC-Restore Circuit Example (CC Type 2) with the OPA656 ..... | 7  |
| 10 | Sample/Hold Circuit Example .....                            | 8  |
| 11 | Instrumentation Amplifier Approach with the OPA861 .....     | 9  |
| 12 | Low-Pass Filter Circuit Example.....                         | 9  |
| 13 | Universal Active Filter with OTA Architecture .....          | 10 |


## 1 Operational Transconductance Overview

OTAs are versatile building blocks that intrinsically offer wide bandwidth for many types of amplifiers. The OTA, or voltage-controlled current source, can be viewed as an ideal transistor. As the transistor model, it has three terminals: a high input impedance (base, or **B**); a low-impedance input/output (emitter, or **E**); and a current output (collector, or **C**). However, unlike a bipolar transistor, the OTA is self-biased and has bipolar output, meaning that the output current source can either source or sink the output current. The output current is zero for a zero base-emitter voltage. AC-inputs centered on zero produce an output current that is bipolar and also centered on zero. The transconductance element is traditionally adjustable with an external resistance, allowing trade-offs in bandwidth, quiescent current, and gain. Used as a basic building block, an OTA element simplifies designs of automatic gain control (AGC) amplifiers, light-emitting diode (LED) driver circuits, fast-pulse integrators, control loops for capacitive sensors, and active filters, as well as other applications.

All trademarks are the property of their respective owners.


## 1.1 Definitions

Over the years and depending on the writer, an OTA has been referred to as a *diamond transistor*, a *voltage-controlled current source*, a *transconductor*, a *macro transistor*, and a *positive second-generation current conveyor* or CCII+. [Figure 1](#) illustrates these terms and the corresponding symbols generally used to represent each.

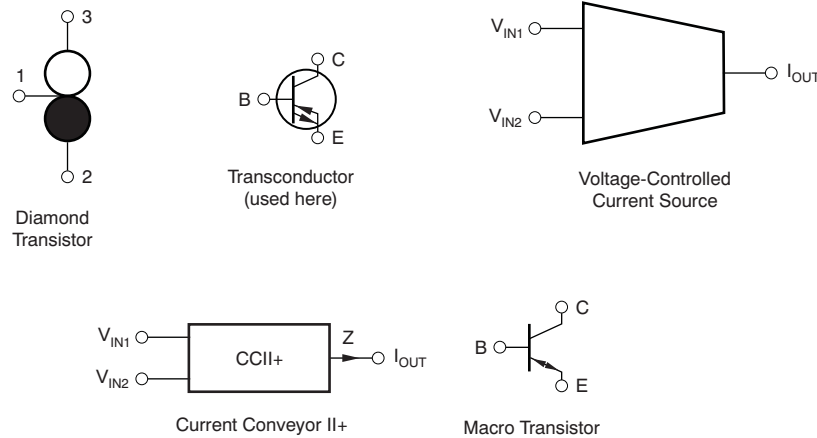

**Figure 1. Typical OTA Elements and Accepted References**

Regardless of how it is illustrated or defined, the OTA has a high impedance terminal (B); a low impedance terminal (E) that can be considered either as an input or an output depending on the circuit; and a output current source terminal (C). The output current source terminal is high impedance. Looking at the transconductor, any voltage that appears between B and E will generate a current that flows out of C. For the balance of this document, however, we will consider circuits. The first circuit that demonstrates how an OTA operates is shown in [Figure 2](#).

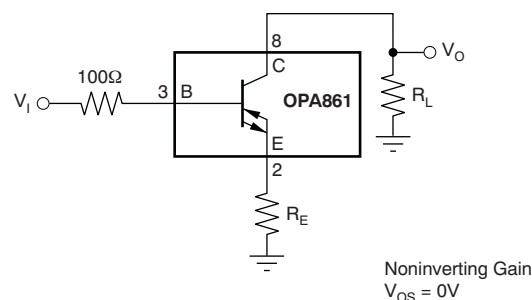

**Figure 2. Basic OTA Circuit Architecture**

Looking at the internal architecture of the OTA as shown in [Figure 2](#), a buffer is present between the B-input and the E-output. This buffer places a copy of the input voltage to the E-output. The voltage present on the E-output generates a current through the  $R_E$  resistor. The current flowing out of the  $R_E$  resistor is then duplicated and flows out of the C-output. This current is converted back to a voltage by passing through the load resistance. The total gain for the circuit illustrated in [Figure 2](#) is set by  $R_L/R_E$ . The input is high impedance and the output impedance is set by the load resistance. Note that a  $100\Omega$  resistance is placed in series with the B-input. This resistance helps isolate the parasitic input capacitance of the OTA from the earlier voltage-mode stage to help ensure stability. A value ranging from  $25\Omega$  to  $100\Omega$  is normally recommended. If a current-mode stage is used, this series resistor is not needed.

## 1.2 Recommended OTA Devices

Texas Instruments offers three devices that include an OTA:

- [OPA860](#) (an OTA and a closed-loop buffer)
- [OPA861](#) (an OTA)
- [OPA615](#) (a wide-bandwidth dc restoration circuit that contains an OTA and a switching OTA, or SOTA)


Information on these products is available through the TI web site at <http://www.ti.com>.

## 2 Direct Use of an OTA

Most circuits for the OTA section of a given application consist of variations on a few basic types. These variations are best understood by analogy to a typical transistor. When used in voltage mode, the OTA section can operate in one of three basic states: common emitter, common base, and common collector. In current mode, the OTA can be used for analog computation such as a current amplifier, a current differentiator, a current integrator, and a current summing device. This section discusses the use of an OTA in either voltage mode or current mode.

### 2.1 Voltage Mode

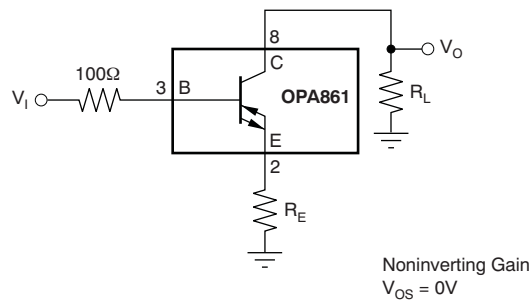Figure 3 through Figure 5 illustrate the options for using an OTA in voltage mode.

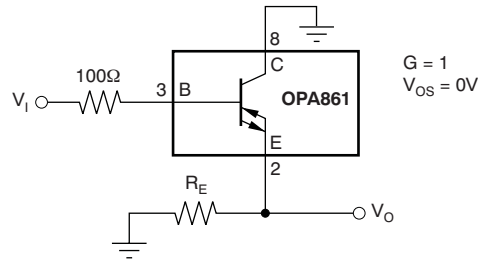


**Figure 3. Voltage Mode: Common-E Amplifier**

The gain for the common-E amplifier configuration is set by Equation 1, and the transconductance shown in Equation 2. Note that a new term appears in the equation,  $g_m$ . This term is the transconductance of the OTA stage. It may be best understood as the output impedance of the E-terminal with a value of  $1/g_m$ .

$$G = \frac{R_L}{\frac{1}{g_m} + R_E} \quad (1)$$

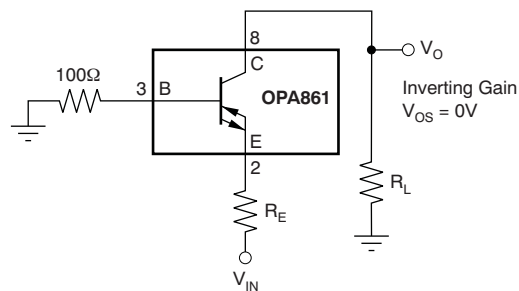
$$g_{m\_deg} = \frac{1}{\frac{1}{g_m} + R_E} \quad (2)$$


**Figure 4. Voltage Mode: Common-C Amplifier**

The gain for the common-C amplifier configuration is set by Equation 3, and the output impedance shown in Equation 4.

$$G = \frac{1}{1 + \frac{1}{g_m \times R_E}} = 1 \quad (3)$$

$$R_O = \left( \frac{1}{g_m} \parallel R_E \right) \quad (4)$$


**Figure 5. Voltage Mode: Common-B Amplifier**





The gain for the common-B amplifier configuration is set by Equation 5.

$$G = \frac{R_L}{R_E + \frac{1}{g_m}} = -\frac{R_L}{R_E} \quad (5)$$

## 2.2 Current Mode

The different current-mode OTA circuits are summarized in [Table 1](#).

**Table 1. Current-Mode Analog Computation Using an OTA Circuit**
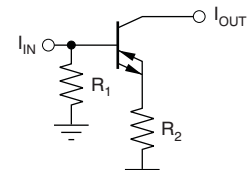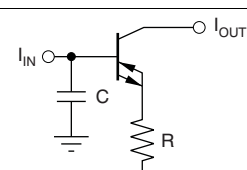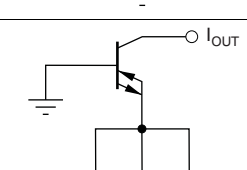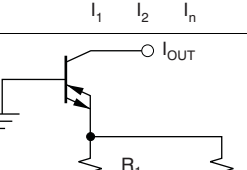
| Functional Element      | Transfer Function Equation                          | Implementation with an OTA Circuit  |
|-------------------------|---|---|
| Current Amplifier       | $I_{OUT} = \frac{R_1}{R_2} \times I_{IN}$           |   |
| Current Integrator      | $I_{OUT} = \frac{\int I_{IN} dt}{C \times R}$       |   |
| Current Summer          | $I_{OUT} = 1 \sum_{j=1}^n I_j$                      |   |
| Weighted Current Summer | $I_{OUT} = 1 \sum_{j=1}^n I_j \times \frac{R_j}{R}$ |  |

### 3 Advanced Uses of OTA Architecture

This section describes several advanced uses of an OTA element in typical applications.

#### 3.1 Current-Feedback Amplifier (CFB)

Combining a transconductance amplifier with a buffer and then adding negative feedback produces the architecture of a current-feedback (CFB) amplifier. Figure 6 shows a typical CFB block diagram.

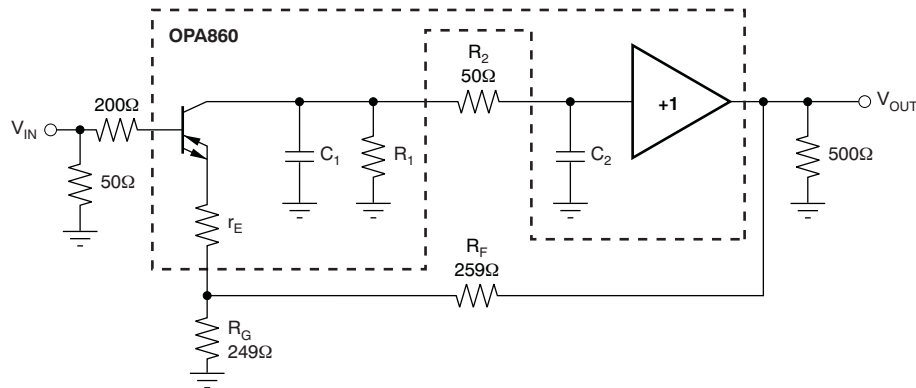


Figure 6. Typical CFB Amplifier Block Diagram

The circuit shown in Figure 6 makes use of the OPA860 because this device integrates both a buffer section and an OTA section. Notice that the E-input/output is normally defined as *inverting input* in operational amplifier nomenclature. The B-input is the noninverting input and the output of the buffer is the operational amplifier output. The C-output of the OTA is connected to the high impedance input of the buffer. Note that  $R_1$ ,  $C_1$ , and  $C_2$  are parasitic components of both the OTA and the buffer.  $R_2$  is an optional component that may help de-Q a potential RLC network as a result of component and package parasitics. If a slower amplifier were desired, to select the frequency response a capacitor in parallel with  $C_2$  can be added. Alternatively, the feedback resistor  $R_F$  can be increased.

#### 3.2 Control-Loop Amplifier

The input stage of the control-loop amplifier shown in Figure 7 is composed of two OTAs. This combination provides a high input impedance as well as excellent rejection to any common-mode signals. One C-output is left unconnected and the other C-output of the input stage is connected to an RC network, in effect forming an integrator from dc to the frequency defined by the RC time constant. A second integrator stage is then used before isolating the C-output of the second stage with a buffer to ensure ac performance and to drive subsequent output stages.

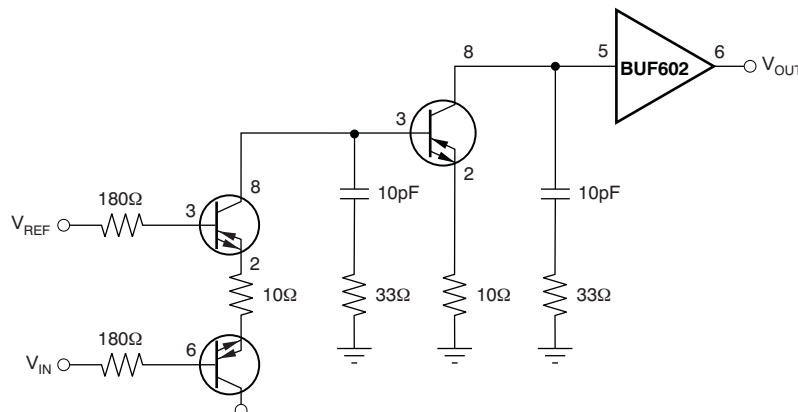


Figure 7. Control-Loop Amplifier Circuit Model

### 3.3 DC-Restore Circuit

Multiple dc-restore circuits can be developed using a modular OTA element. The circuit illustrated in Figure 8 uses a SOTA to restore the signal when it is triggered. This architecture allows a precise selection of the dc-restore point. For this purpose, we used the OPA615.

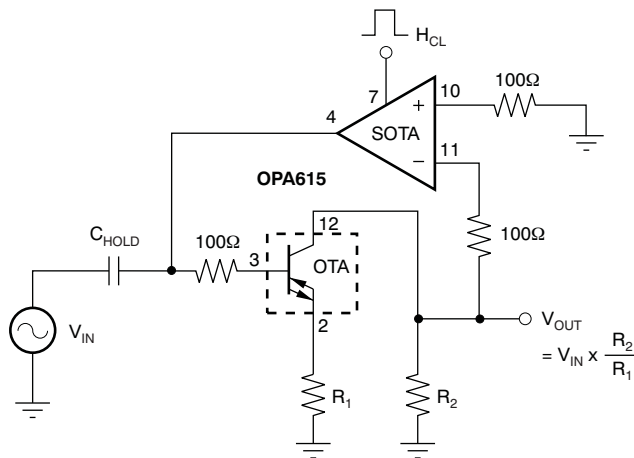


Figure 8. DC-Restore Circuit Example with the OPA615

In this example, the  $C_{\text{HOLD}}$  capacitor is being charged by the sampling OTA (SOTA), triggered at the exact point of interest. The OTA provides a means to amplify the signal. Note that because of the very high input impedance of the OTA, a small  $C_{\text{HOLD}}$  capacitor can be used for higher frequency applications; or, if a large  $C_{\text{HOLD}}$  is desired, a very low-frequency high-pass filter can be defined. The OPA615 is the fastest OTA offered by Texas Instruments with a bandwidth in excess of 700MHz. This circuit can easily be adapted to operate continuously without any trigger requirements by adding a capacitor on the SOTA inverting input. This capacitor will form, with the 100Ω series resistance at the input, a low-pass filter that allows the SOTA to charge and discharge the hold capacitor only in relation to the low frequency.

Figure 9 shows another possible implementation of a dc-restore circuit using a current conveyor Type 2 (CCII) OTA.

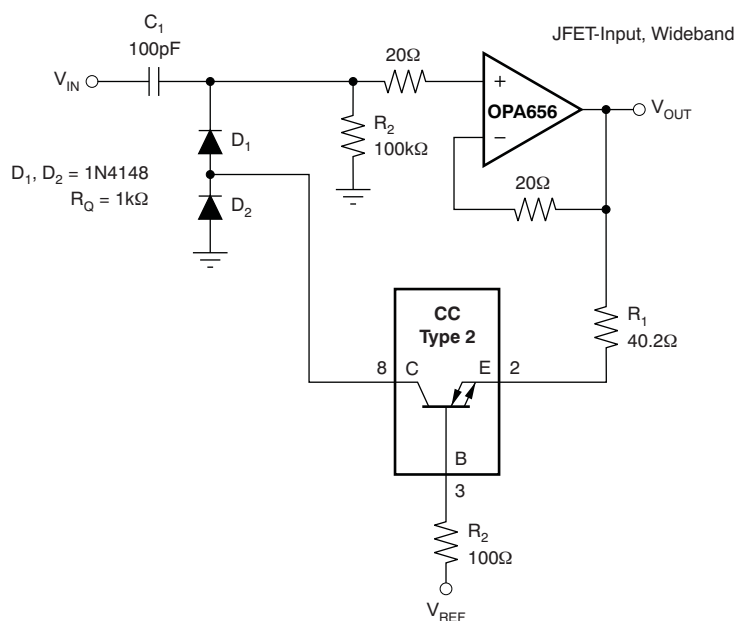



Figure 9. DC-Restore Circuit Example (CC Type 2) with the OPA656

Here, the OTA amplifier works as a current conveyor (CCII), with a current gain of 1.  $R_1$  and  $C_1$  set the dc restoration time constant.  $D_1$  adds a propagation delay to the dc restoration.  $R_2$  and  $C_1$  set the decay time constant.

The output voltage of the operational amplifier (in this case, an OPA656), is compared to a reference level. When the signal is below the level, a current is driven into the noninverting input of the amplifier, thereby raising the dc level.

### 3.4 Sample/Hold Circuit

The OPA615 can also be reconfigured as a sample/hold circuit using the approach presented in Figure 10.

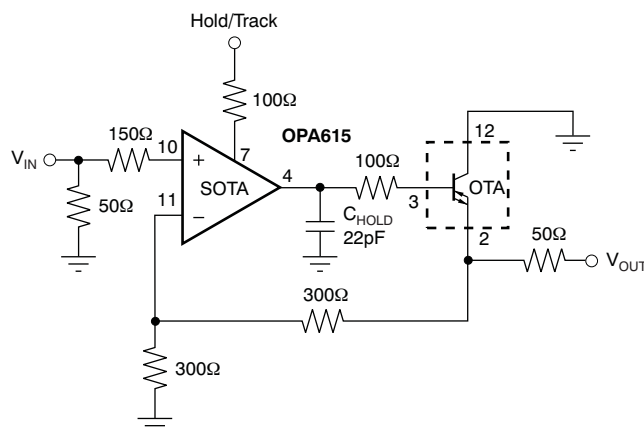

**Figure 10. Sample/Hold Circuit Example**

Ignoring the hold/track control of the SOTA for now, or considering that the SOTA is in a track mode, you may recognize a voltage-feedback amplifier architecture. The SOTA is used as the input stage, with the OTA (in a buffer configuration) to play the output stage role of a traditional voltage-feedback architecture. You can see that for any change of voltage at the input, the output will track the input with a gain of  $2V/V$ .

Activating the hold mode, the SOTA C-output is now disconnected. The charge held by the hold capacitor is set and droops only as a result of the B-input bias current of the OTA. The output voltage is set. The E-output of the OTA will then see a total load of  $(600\Omega \parallel \text{Load})$ .

As you go from track mode to hold mode, you effectively realize a sample/hold application. With a 2.5ns control delay and greater than 700MHz bandwidth, the OPA615 answers several medium- to high-speed sample/hold needs.



### 3.5 Instrumentation Amplifier

Figure 11 shows an instrumentation amplifier using three OPA861s to form the high-impedance front-end. Two OTAs are used to create the differential input stage. The third OTA is present to invert the current flowing out of the  $IN_2$  OTA. Remember that the current is flowing out of the C-output. Ground  $V_{IN2}$  for a moment and set a positive voltage on  $V_{IN1}$ . This method generates a current that flows across  $R_G$  from top to bottom, exiting the  $IN_1$  OTA and entering the  $IN_2$  OTA. The current flowing out of the C-output then flows out of the  $IN_1$  OTA and into the  $IN_2$  OTA, indicating that both currents will be of same amplitude but  $180^\circ$  out of phase. To be able to add the currents together at the inverting pin of the operational amplifier, one of the input stage current must be inverting. That function is realized by the third OTA. To compensate for the propagation delay of the second amplifier, an RC network was used. Having two currents with the same amplitude and phase, we can simply add them together and drive a transimpedance amplifier.

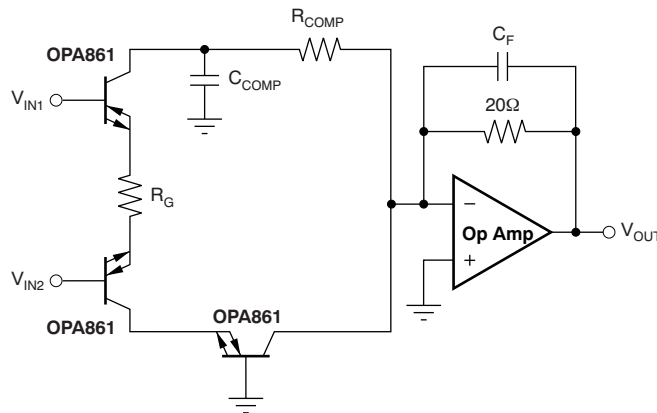


Figure 11. Instrumentation Amplifier Approach with the OPA861

Because any common-mode signal will try to generate the same opposing currents across the gain resistor, this circuit exhibits very good common-mode rejection.

## 4 Advanced OTA Circuits

From a conceptual standpoint, filtering applications using an OTA element are the most challenging because thinking in a current-mode approach is not a popular technique. However, current-mode amplifiers allow more bandwidth for a reduced quiescent current in most cases. This section describes a simple filtering circuit as well as a high-performance filter developed on an OTA element.

### 4.1 Simple Filtering Circuit

The low-pass filter circuit illustrated in Figure 12 achieves filtering through the use of a negative impedance converter.

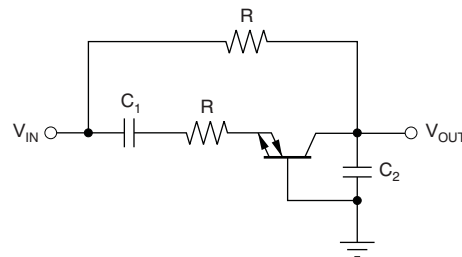


Figure 12. Low-Pass Filter Circuit Example

Equation 6 provides the design equation of the filter.

$$\frac{V_{OUT}}{V_{IN}} = \frac{1}{1 + sC_2R + s^2C_1C_2R^2} \quad (6)$$

with:

$$\omega_o = \frac{1}{\sqrt{C_1C_2}R}$$

$$Q = \sqrt{\frac{C_1}{C_2}}$$

This circuit may require some buffering, because the input impedance is set as shown in Equation 7.

$$Z_{IN} = \frac{1}{2sC} + R \frac{1 + sRC}{1 + 2sRC} \quad (7)$$

## 4.2 Advanced Filtering Circuit

A universal active filter can be achieved with an OTA using an integrator, as Figure 13 shows. Note that not all OTAs are required for different filtering functions (such as low-pass filters, high-pass filters, or band-pass filters). This circuit implements a second-order filter. Higher-order filters are possible by simply adding an additional integrator stage with its two corresponding, current-weighted OTAs.

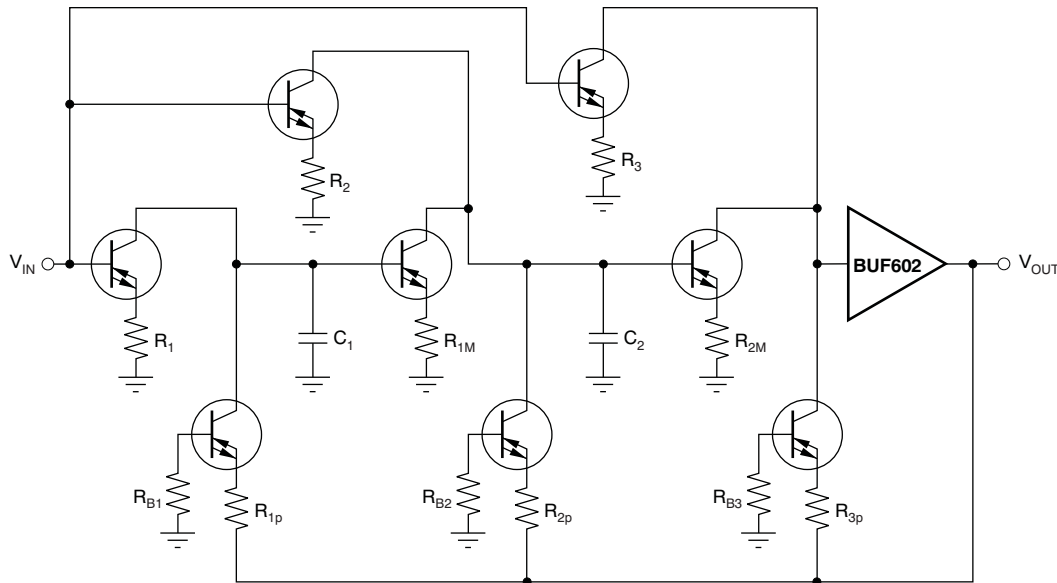


Figure 13. Universal Active Filter with OTA Architecture

With 80MHz OTAs, filter bandwidths as high as 50MHz have been achieved without considering any parasitics for predistortion reasons. These 50MHz/80MHz results compare favorably with the ratio of 50MHz/1GHz that is achieved when traditional operational amplifier circuits are considered.

Equation 8 gives the design equation for the filter shown in Figure 13.

$$F(s) = \frac{V_{OUT}}{V_{IN}} = \frac{s^2C_1C_2R_{1M} \frac{R_{2M}}{R_3} + sC1 \frac{R_{1M}}{R_2} + \frac{1}{R_1}}{s^2C_1C_2R_{1M} \frac{R_{1M}}{R_{3p}} + sC1 \frac{R_{1M}}{R_{2p}} + \frac{1}{R_{1p}}} \quad (8)$$

#### 4.2.1 Filter Characteristics

Five filter types can be designed with this structure. These five types include the following:

- For a low-pass filter, set  $R_2 = R_3 = \infty$
- For a high-pass filter, set  $R_1 = R_2 = \infty$
- For a bandpass filter, set  $R_1 = R_3 = \infty$
- For a band rejection filter, set  $R_2 = \infty$ , and  $R_1 = R_3$
- For an all-pass filter, set  $R_1 = R_{1p}$ ;  $R_2 = R_{2p}$ ; and  $R_3 = R_{3p}$

## IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

### Products

|                             |  |
|-----------------------------|--|
| Amplifiers                  | <a href="http://amplifier.ti.com">amplifier.ti.com</a>             |
| Data Converters             | <a href="http://dataconverter.ti.com">dataconverter.ti.com</a>     |
| DLP® Products               | <a href="http://www.dlp.com">www.dlp.com</a>                       |
| DSP                         | <a href="http://dsp.ti.com">dsp.ti.com</a>                         |
| Clocks and Timers           | <a href="http://www.ti.com/clocks">www.ti.com/clocks</a>           |
| Interface                   | <a href="http://interface.ti.com">interface.ti.com</a>             |
| Logic                       | <a href="http://logic.ti.com">logic.ti.com</a>                     |
| Power Mgmt                  | <a href="http://power.ti.com">power.ti.com</a>                     |
| Microcontrollers            | <a href="http://microcontroller.ti.com">microcontroller.ti.com</a> |
| RFID                        | <a href="http://www.ti-rfid.com">www.ti-rfid.com</a>               |
| RF/IF and ZigBee® Solutions | <a href="http://www.ti.com/lprf">www.ti.com/lprf</a>               |

### Applications

|                    |  |
|--------------------|--|
| Audio              | <a href="http://www.ti.com/audio">www.ti.com/audio</a>                   |
| Automotive         | <a href="http://www.ti.com/automotive">www.ti.com/automotive</a>         |
| Broadband          | <a href="http://www.ti.com/broadband">www.ti.com/broadband</a>           |
| Digital Control    | <a href="http://www.ti.com/digitalcontrol">www.ti.com/digitalcontrol</a> |
| Medical            | <a href="http://www.ti.com/medical">www.ti.com/medical</a>               |
| Military           | <a href="http://www.ti.com/military">www.ti.com/military</a>             |
| Optical Networking | <a href="http://www.ti.com/opticalnetwork">www.ti.com/opticalnetwork</a> |
| Security           | <a href="http://www.ti.com/security">www.ti.com/security</a>             |
| Telephony          | <a href="http://www.ti.com/telephony">www.ti.com/telephony</a>           |
| Video & Imaging    | <a href="http://www.ti.com/video">www.ti.com/video</a>                   |
| Wireless           | <a href="http://www.ti.com/wireless">www.ti.com/wireless</a>             |

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2009, Texas Instruments Incorporated