



## EMERGENCY LIGHTING APPLICATIONS

G. Consentino

### 1. ABSTRACT

This application note shows the topologies implemented in the Emergency Lighting Applications and the STMicroelectronics's power bipolar transistors used.

Today, the Emergency Lamps market has grown considerably due to the new improved safety rules. In fact, the Emergency Lamps are used in all public places and, also, in private homes replacing the traditional lighting applications.

### 2. STSA851 DESCRIPTION

The STMicroelectronics's power bipolar transistor STSA851 is housed in the TO-92 package. This device is manufactured in NPN planar technology using a 'Base Island' layout that involves a very high gain performance and a very low saturation voltage.

The main characteristics of the STSA851 device are:

- 1)  $V_{ce0} \geq 60$  V;
- 2)  $V_{ces} \geq 150$  V;
- 3)  $V_{ebo} \geq 7$  V;
- 4)  $I_c = 5$  A (continuous current);
- 5)  $I_b = 1$  A (continuous current);
- 6)  $V_{ce(sat)} = 140$  mV (typ) @  $I_b = 50$  mA @  $I_c = 2$  A (typical conditions);
- 7)  $H_{fe} = 270$  (typ) @  $I_c = 2$  A @  $V_{ce} = 1$  V (typical conditions).

### 3. HIGH EFFICIENCY DC-AC CONVERTERS

The part of the circuit used to drive the emergency lamp is composed of DC-AC converters. The DC-AC converters transform the low DC input voltage in high AC output voltage required by the fluorescent tube. Fluorescent tubes are employed in these applications because they are much more efficient at converting electrical energy into light than conventional incandescent bulbs increasing the battery life. Usually, DC-AC converters used in these applications are the Push-Pull switching converter forced to run in synchronized mode by the inclusion of a supply inductor, and the Forward converter. Mainly, the DC-AC converters have suitable transformers that increase the output voltage and allow the electrical isolation between the secondary and primary of the transformer, and suitable switches. Usually, the switches are power bipolars driven by a third winding magnetically coupled to the transformer, like in the PUSH-PULL current FED converter.

The power bipolar transistor collector current  $I_c$  depends on the load, turns rapport

$$K = \frac{N_2}{N_1/2} \quad (3.1)$$

where  $N_2$  is the secondary turn number and  $N_1$  is the primary turn number of the transformer, and it also depends on the battery voltage.

Usually, in these applications the lamp power is in the range of 8-24W, and the turns rapport

$$\frac{N_2}{N_1/2} \quad (3.2)$$

is about 30, the current  $I_c$  is in the range of 1.5-3.0A. Furthermore, usually, the emergency lighting boards are powered with an input voltage in the range of 3.6-6.0  $V_{dc}$  so that the typical  $V_{ce\_max}$  is around 10-20  $V_{dc}$ . The voltage and current values ranges,  $V_{ce\_max}$  and  $I_c$ , are inside the SOA of the STSA851 so that these devices can be used in all emergency lighting applications. The emergency lamp applications drive a lamp up to 58W. Usually, these emergency lighting applications do not supply such output powers but only 10-20 % of the nominal lamp power. Sometimes, such applications are used to power lamps that commonly light up rooms. When the net voltage disappears the emergency lamp switches on supplying around 10-20 % of the nominal lamp power just to light up the room.

#### 4. FLUORESCENT TUBE CHARACTERISTICS

Fluorescent lamps are generally made with tubes filled with a gas mixture at a low pressure. The inner sides of the tubes are covered with fluorescent elements. When the net voltage disappears, before the tube lights on, the lamp has a higher resistance. In this moment, the electrodes voltage increases up to around 500V and the electrodes start to warm up and emit ions. Figures 1 and 2 show the V-time and I-time waveforms and the V-I waveform respectively before the start-up of a 24W tube.

Figure 1: V-time and I-time Waveforms Before the Striking


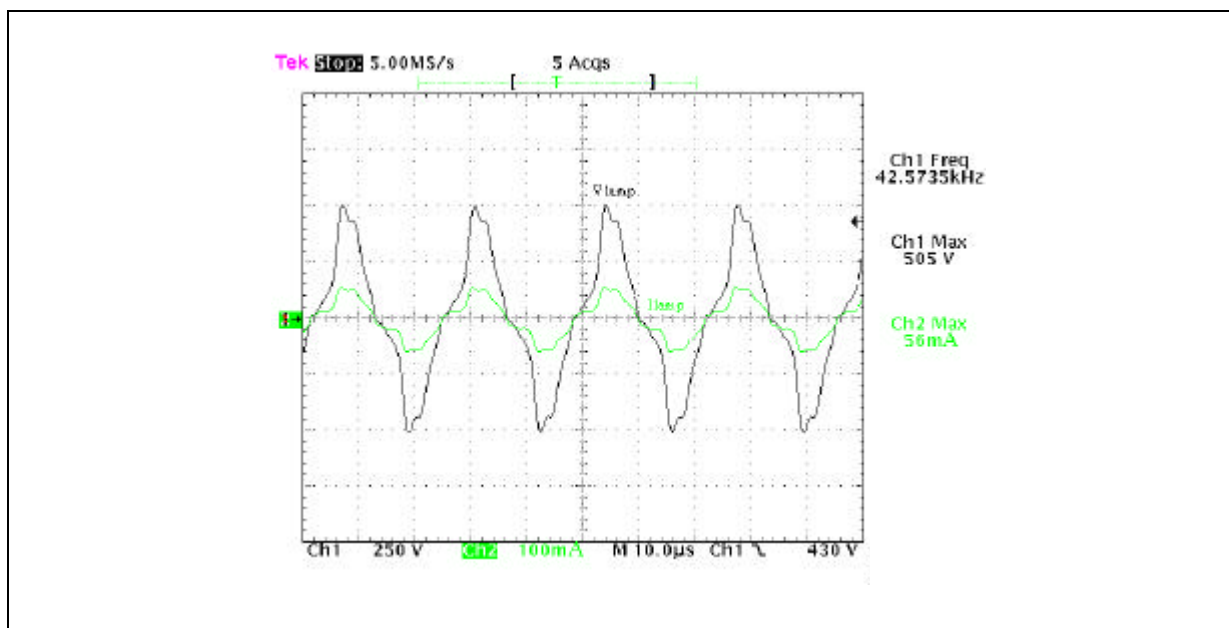


Figure 2: V-I waveform before the striking

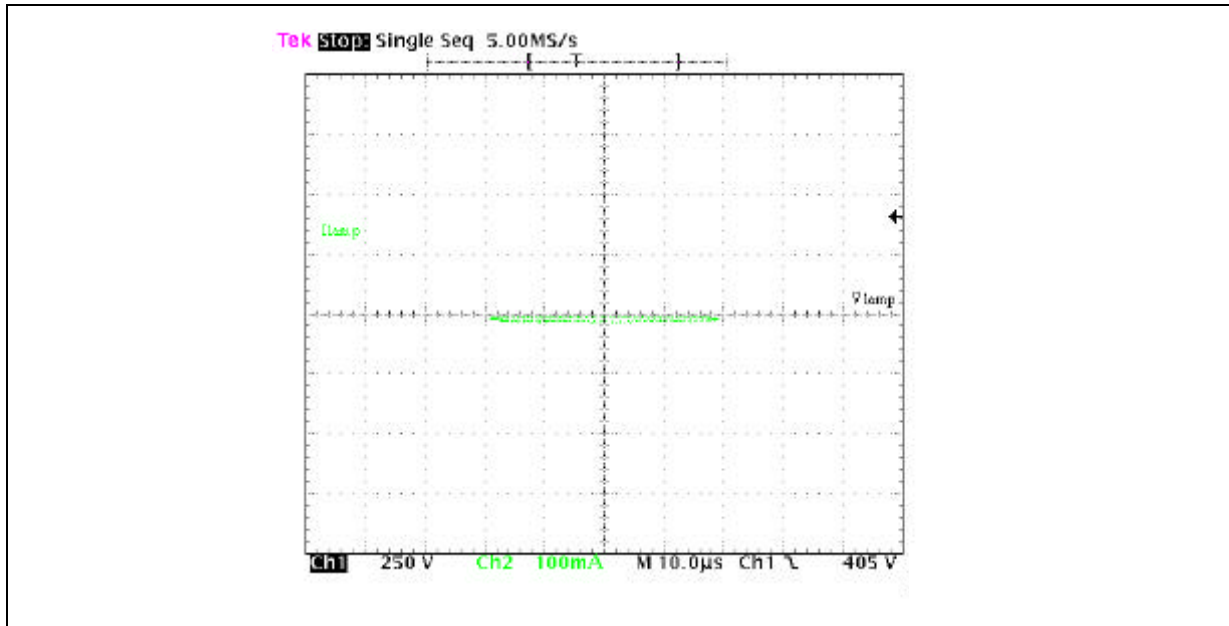

As shown above, to strike the fluorescent tube the electrodes voltage reaches up to 505V of peak. Furthermore, the current that flows through the lamp is very low, 56 mA, because the resistance before the striking is high (around 10 KOhm).

When the fluorescent lamp lights on, the gas mixture inside is fully ionized, and an arc across the electrodes occurs. In this new condition, the lamp resistance drops to around 1 KOhm value (Figures 3 and 4 show the V-time and I-time waveforms and the V-I waveform after the striking).

Figure 3: V-time and I-time waveforms after the striking


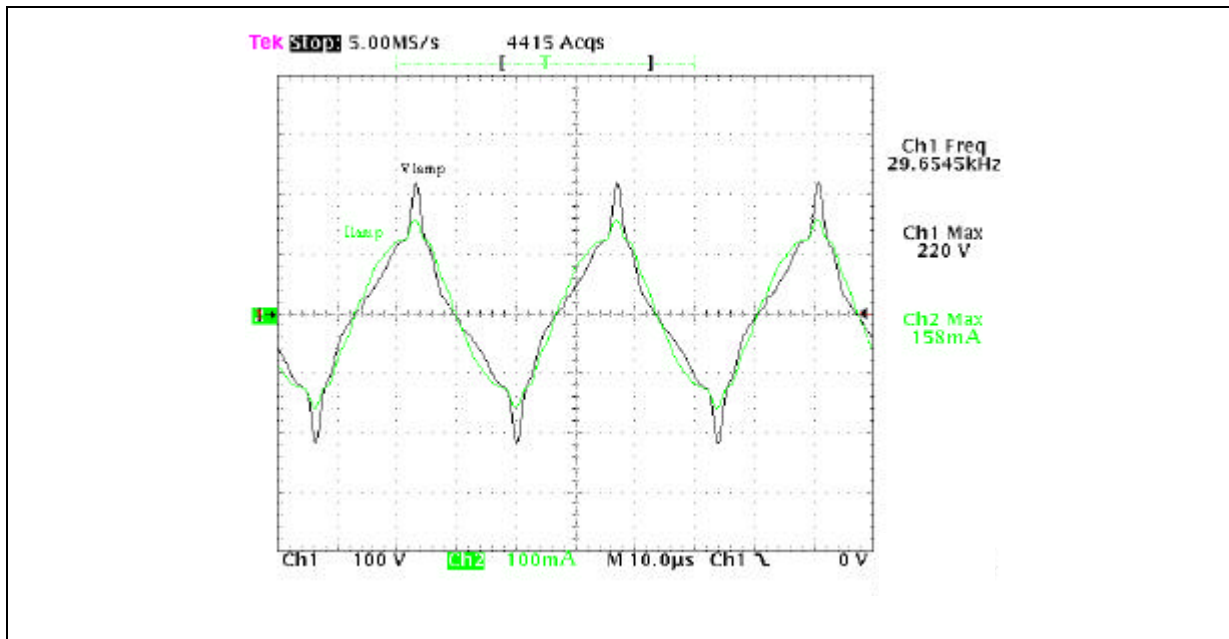


Figure 4: V-I waveform after the striking

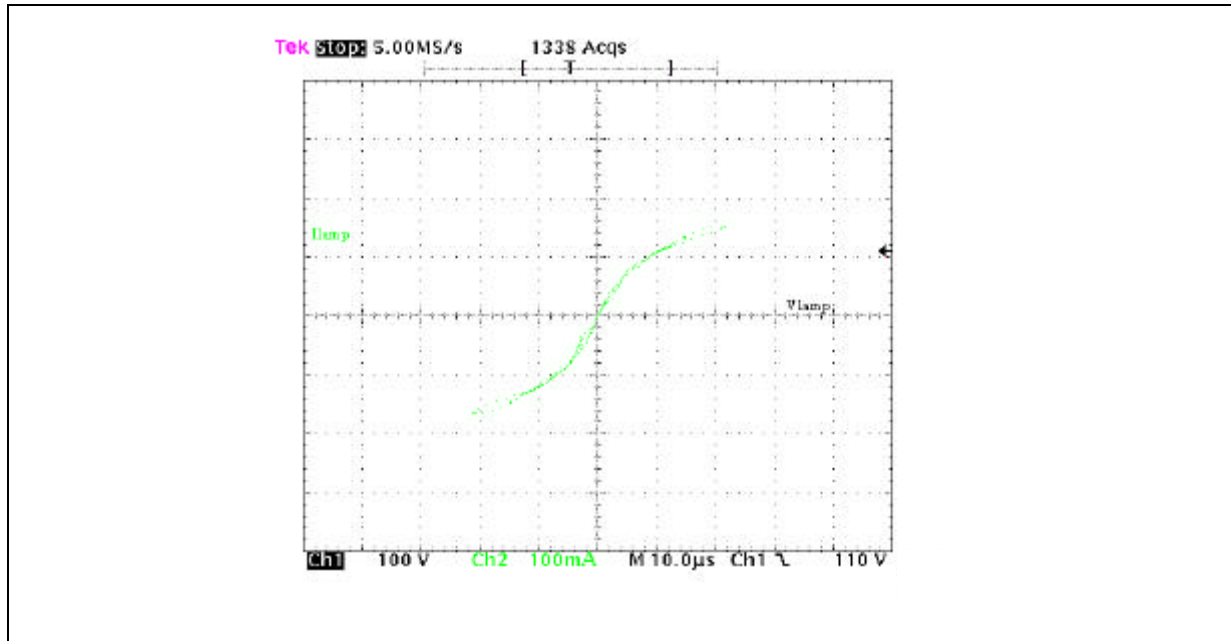


After the striking, the gas mixture emits radiations that excite the fluorescent elements inside the tube producing the light in the visible spectrum. In this example, after the striking, the voltage across the electrodes drops from 505V of peak to 220V of peak and the current increases from 56mA of peak to 158mA of peak.

Usually, after the striking, in order to increase the lamp efficiency up to 15%, the operation frequency is in the range of 25-30KHz. Furthermore, as shown in Fig. 4, the waveform I-V has a linear behavior until the established voltage value is kept. In fact, if the voltage across the electrodes overcomes this established voltage value, the characteristic becomes flat because no ion can emit other radiations.

## 5. PUSH-PULL CURRENT FED CONVERTER TOPOLOGY INTRODUCTION

As previously exposed, a topology solution for emergency lighting applications is the PUSH-PULL current FED converter topology. This topology solution has a Push-Pull switching converter forced to run in synchronized mode by the inclusion of a supply inductor.

**Figure 5: PUSH-PULL current FED converter schematic circuit**

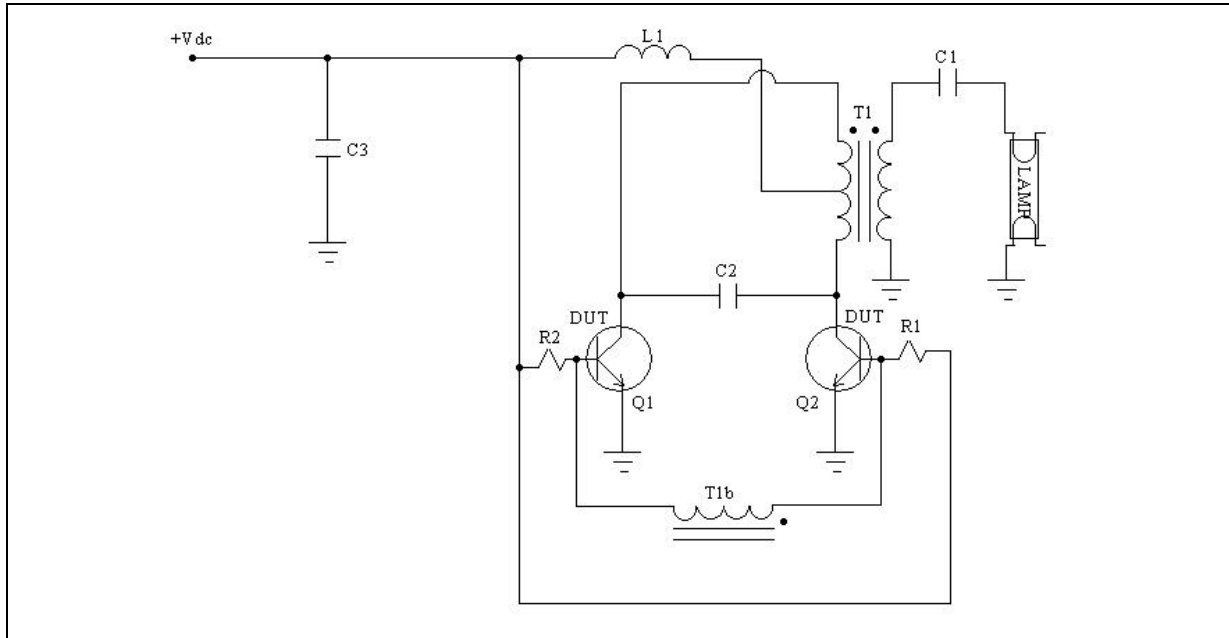

The components values of capacitors, resistors, and inductors are selected operation on the input voltage, power lamp, and operation frequency.

## 6. TRANSFORMER DESCRIPTION OF PUSH-PULL TOPOLOGY

In figure 5 the transformer named  $T_1$  has three windings. The primary winding vices are connected to the collectors of the NPN power bipolar transistors  $Q_1$  and  $Q_2$ . The same primary winding has a central vice where the inductor  $L_1$  is connected. The secondary winding vices are connected to the load.

The third winding vices are connected to the base of the transistors  $Q_1$  and  $Q_2$  so that when the first is on, the second is off and vice versa. During the  $Q_2$  on state, the current flows through the same device and the respective half primary winding and vice versa. Usually the primary inductance  $L_T$  of the transformer  $T_1$  is much lower compared to the inductance  $L_1$ . The resonance frequency of the PUSH-PULL converter is also due to  $L_T$ .  $N_2$  (secondary winding turns) and  $N_1/2$  (half primary winding turns) rapport is around 60, while  $N_1/2$  and  $N_3$  (third winding turns) rapport is around 5. Considering a  $6 V_{dc}$  input voltage, the voltage  $v_{1max}$  (the max voltage across the vice of the primary winding central point and the reference) can be written as:

$$v_{1max} = \frac{\pi}{2} \cdot V_{dc} = \frac{3.14}{2} 6 \cong 9V \quad (6.1)$$

$v_{2max}$  (the max voltage across the secondary winding vices) can be written as:


$$v_{2max} = \frac{\pi}{2} \cdot V_{dc} \cdot \frac{N_2}{(N_1/2)} = \frac{3.14}{2} \cdot 6 \cdot 60 \cong 560V \quad (6.2)$$

$v_{3max}$  (the max voltage across the vices of the third winding) can be written as:

$$v_{3max} = \frac{\pi}{2} \cdot V_{dc} \cdot \frac{N_3}{N_1/2} = \frac{3.14}{2} \cdot 6 \cdot \frac{1}{5} \cong 2V \quad (6.3)$$

As exposed above, it is highlighted  $N_1/2$  and not  $N_1$ . In order to understand the reason of it, it is necessary to consider the graph below.

Figure 6: Particular of  $T_1$

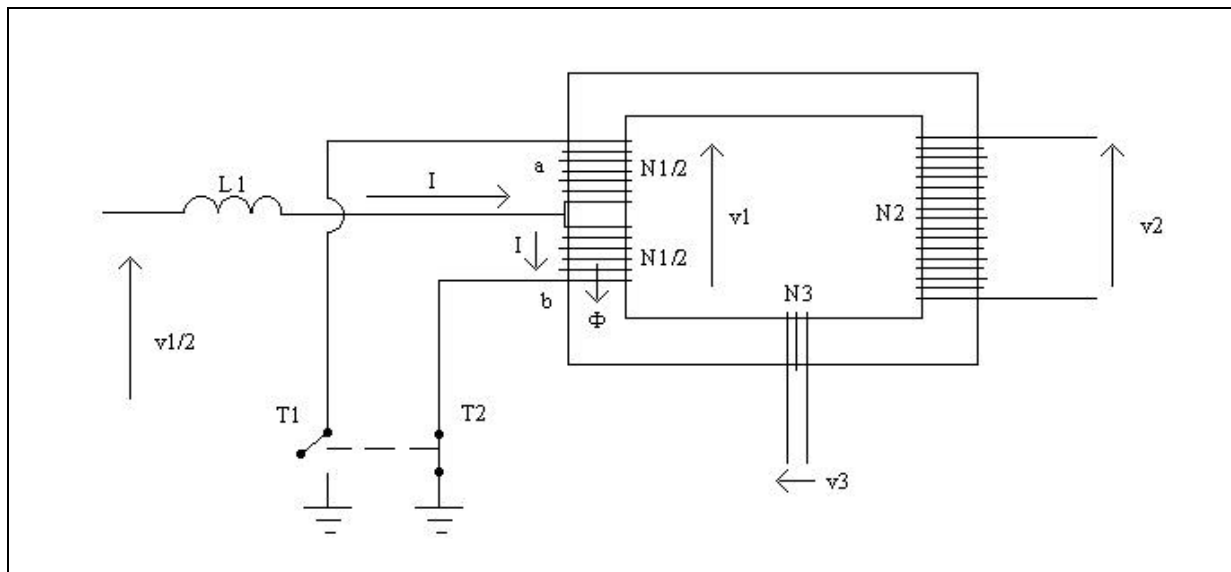

When  $Q_2$  is on,  $Q_1$  is off and vice versa. Now, considering fig. 6 where  $T_2$  is on; the current 'I' flows through the half primary winding 'b' and it generates a magnetic force (Hopkinson law):

$$\frac{N_1}{2} \cdot I = \mathfrak{R} \cdot \Phi \quad (6.4)$$

$\Phi$  is the magnetic flux and  $\mathfrak{R}$  is the magnetic reluctance of the  $T_1$  core;  $\Phi$  can be written as:

$$\Phi = \frac{N_1 \cdot I}{\mathfrak{R}} \quad (6.5)$$

$\mathfrak{R}$  can be written as:

$$\mathfrak{R} = \frac{l}{\mu \cdot A} \quad (6.6)$$

$\mu$  is the core permeability,  $A$  is the core section and  $l$  is the core length. When  $T_2$  switches off,  $T_1$  switches on, the current flows through the other half primary winding 'a' and the flux  $\Phi$  inverts its direction. Such flux flows into the transformer core creating a link with  $N_2$ ,  $N_3$  and also with the other

turns  $N_1/2$ , generating the voltages  $v_2$  and  $v_3$  (magnetic law-Lenz law):

$$\begin{aligned} v_2 &= -N_2 \frac{\Delta\Phi}{\Delta t}; \\ v_3 &= -N_3 \frac{\Delta\Phi}{\Delta t}; \\ v_{1/2} &= -\frac{N_1}{2} \frac{\Delta\Phi}{\Delta t} \end{aligned} \quad (6.7)$$

$$\frac{v_2}{v_1} = \frac{N_2}{N_1/2}, \frac{v_3}{v_1} = \frac{N_3}{N_1/2}, \frac{v_{c2}}{v_1} = 2 \quad (6.8)$$

Furthermore,  $i_2$  (the current that flows through the lamp) can be written as:

$$i_2 = I \frac{N_1/2}{N_2} = I \frac{1}{K} \quad (6.9)$$

In fact, the apparent input power can be written as:

$$A_{in} = v_1 I \quad (6.10)$$

The output power can be written as:

$$A_{out} = v_2 i_2 \quad (6.11)$$


Considering an ideal transformer:

$$v_2 i_2 = v_1 I \quad (6.12)$$

$$\frac{i_2}{I} = \frac{v_1}{v_2} = \frac{N_1/2}{N_2} = \frac{1}{k} \quad (6.13)$$

Before the lamp strike, or when the lamp is disconnected, the operation frequency (about 60 KHz) is due to the resonance between  $C_2$  and the primary transformer winding inductance LT (see fig. 7).


**Figure 7: Resonant Schematic Circuit Before the Lamp Strike**

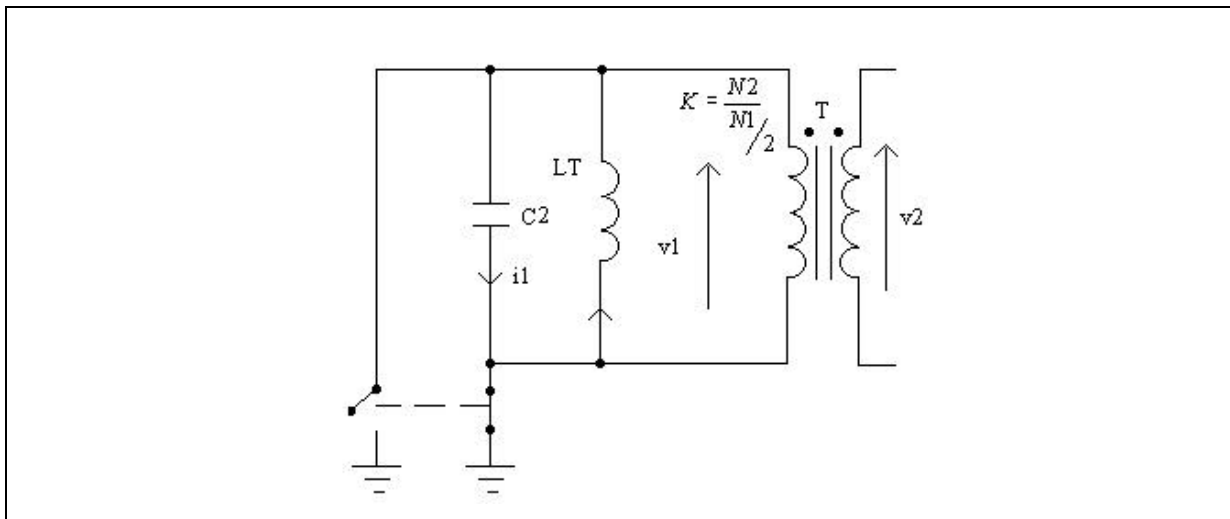

$$f = \frac{1}{2 \cdot p \sqrt{LTC^2}} \quad (6.14)$$

When the lamp is connected, the transformer circuit can be showed as in the graph below.

**Figure 8: Ideal Schematic Circuit of the Transformer After the Lamp Strike**

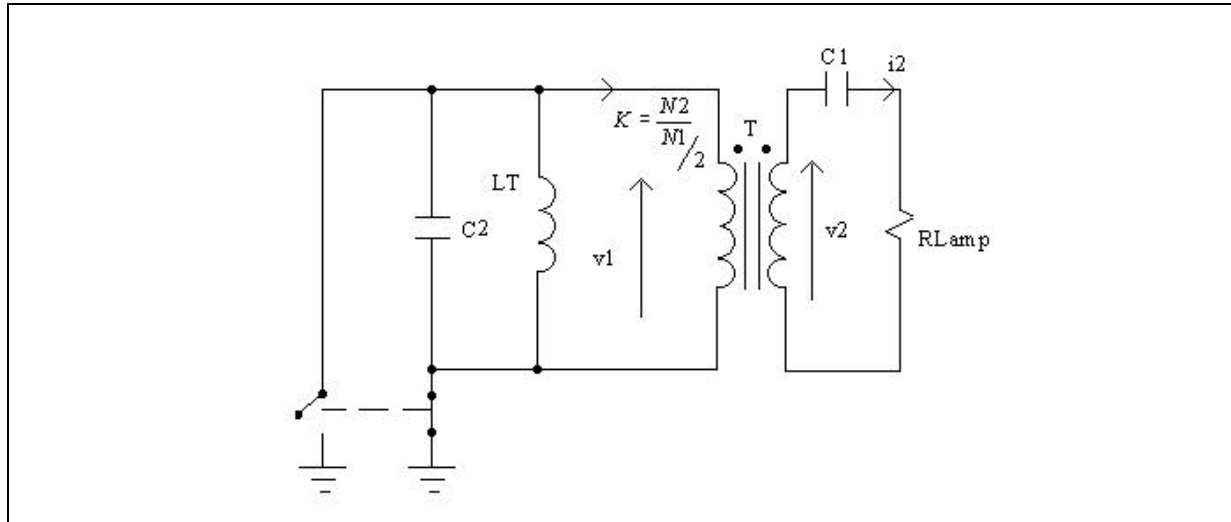


The input apparent power can be written as:

$$A_{in} = v_1 i_1 \quad (6.15)$$

Now it is possible to consider an equivalent circuit to fig. 8, as in fig. 9, where the apparent input power is equal.


**Figure 9: Equivalent Schematic Circuit of the Transformer After the Lamp Strike**

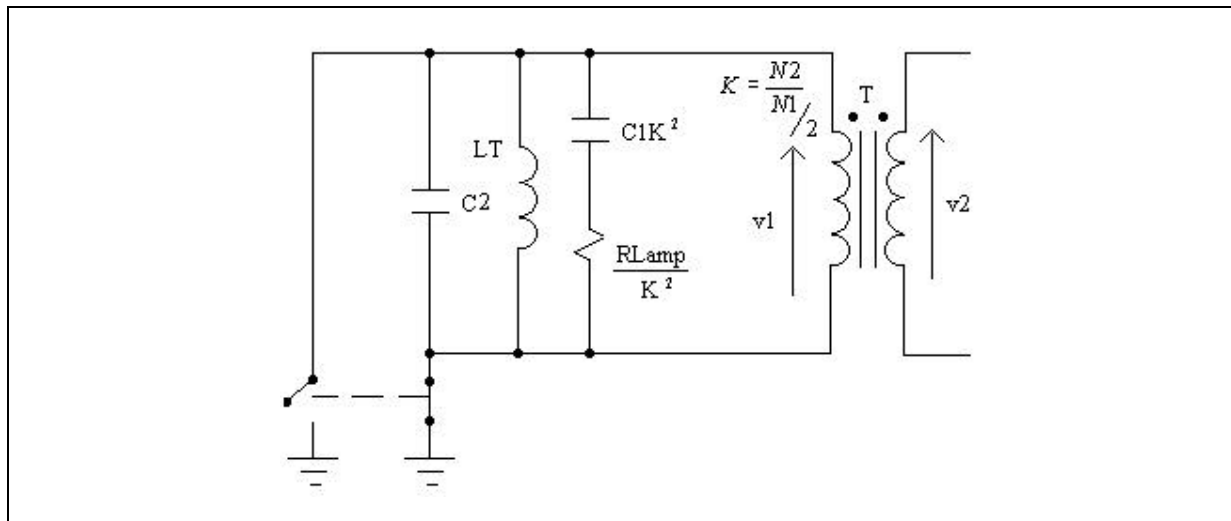

Furthermore, after the lamp strike, the resonant schematic circuit can be represented as in figure 10 where, usually, the operation frequency is due to LT, C2 and C1K<sup>2</sup> (25-30 KHz).



Figure 10: Resonant Schematic Circuit of the Transformer After the Lamp Strike

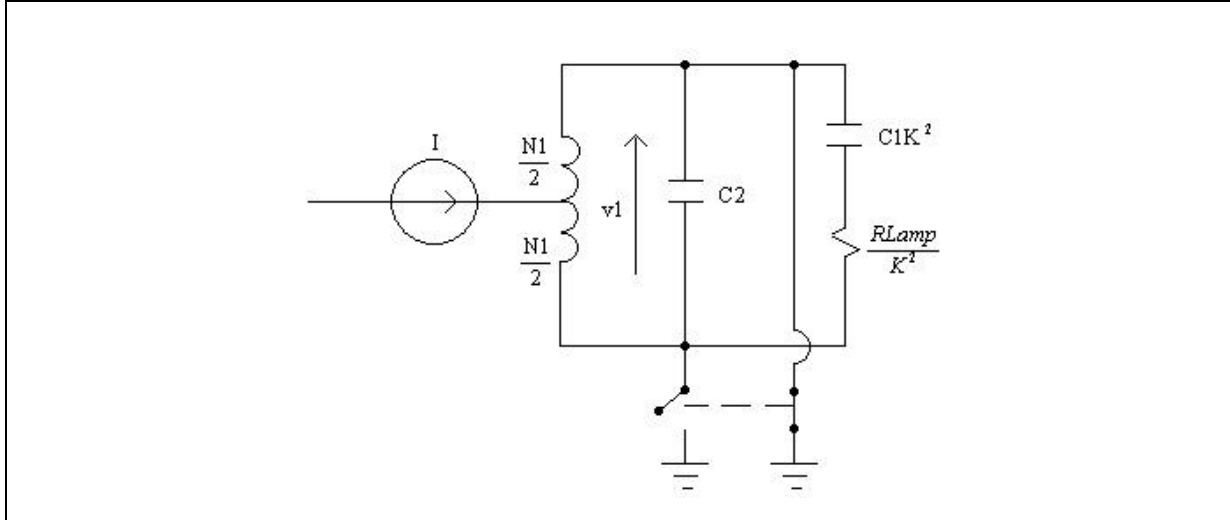

In this transformer equivalent circuit the output impedance has been transferred from the secondary winding to the primary winding.

$$v_1 I = v_2 i_2 = i_2^2 \left( R_{Lamp} - j \frac{1}{\omega \cdot C_1} \right) \quad (6.16)$$

$$\frac{v_1 I}{i_2^2} = \left( R_{Lamp} - j \frac{1}{\omega \cdot C_1} \right) = \frac{V_1}{i_2} \frac{I}{i_2} = \frac{v_1}{I} \frac{N_2^2}{\left( \frac{N_1}{2} \right)^2} = \frac{v_1}{I} k^2 \quad (6.17)$$

$$\frac{v_1}{I} = z_{eq1} = \frac{1}{k^2} \left( R_{Lamp} - j \frac{1}{\omega \cdot C_1} \right) \quad (6.18)$$

Where:

$$\frac{R_{LAMP}}{k^2} \quad (6.19)$$

is the primary equivalent resistance and where:

$$C_1 K^2 \quad (6.20)$$

is the primary equivalent capacitance.

Now, the equivalent primary admittance ( $Y_{eq1}$ ) can be written as:

$$Y_{eq1} = \frac{-j}{\omega \cdot L T} + j\omega \cdot C_2 + \frac{k^2 j\omega C_1}{(1 + j\omega C R_{Lamp} \omega)} \quad (6.21)$$

and where:

$$\frac{k^2 j\omega \cdot C_1}{(1 + j\omega C R_{Lamp} \omega)} \quad (6.22)$$

is the admittance of the series net

$$\frac{R_{Lamp}}{k^2} - C_1 k^2 \quad (6.23)$$

Considering

$$\frac{R_{Lamp}}{k^2} \tag{6.24}$$

negligible compared to

$$\frac{1}{w \cdot C_1 k^2} \tag{6.25}$$

deriving  $Y_{eq1}$  compared to the pulsation and equal to zero, it is possible to achieve the frequency that maximizes, the  $Y_{eq1}$  (such frequency is the resonance frequency of the application during the lamps on state).

$$w^2 \cong \frac{1}{LT(C_2 + k^2 C_1)} \tag{6.26}$$

$$f \cong \frac{1}{2 \cdot p \sqrt{LT(C_2 + k^2 C_1)}} \tag{6.27}$$


When the board is powered,  $R_1$  and  $R_2$  enable  $Q_1$  and  $Q_2$  and the lamp turns on. After the lamp start-up, during the  $Q_2$  on state, the current flows through  $L_1$ , the half primary winding transformer  $T_1$  and  $Q_2$ , and it increases as:

$$tga = \frac{V_{L1} \cdot \Delta t}{L_1} \tag{6.28}$$

angular coefficient but, after a while, the current curves and it becomes flat. However, in the permanent state, even if the current oscillates around its average value, there is a ripple of this same value. The current ripple decreases increasing the inductance value  $L_1$ .

Figure 11 shows the PUSH-PULL current FED converter schematic circuit with the theoretical waveform of 'I'.

**Figure 11: PUSH-PULL Current FED Converter Schematic Circuit with the Theoretical Waveform**

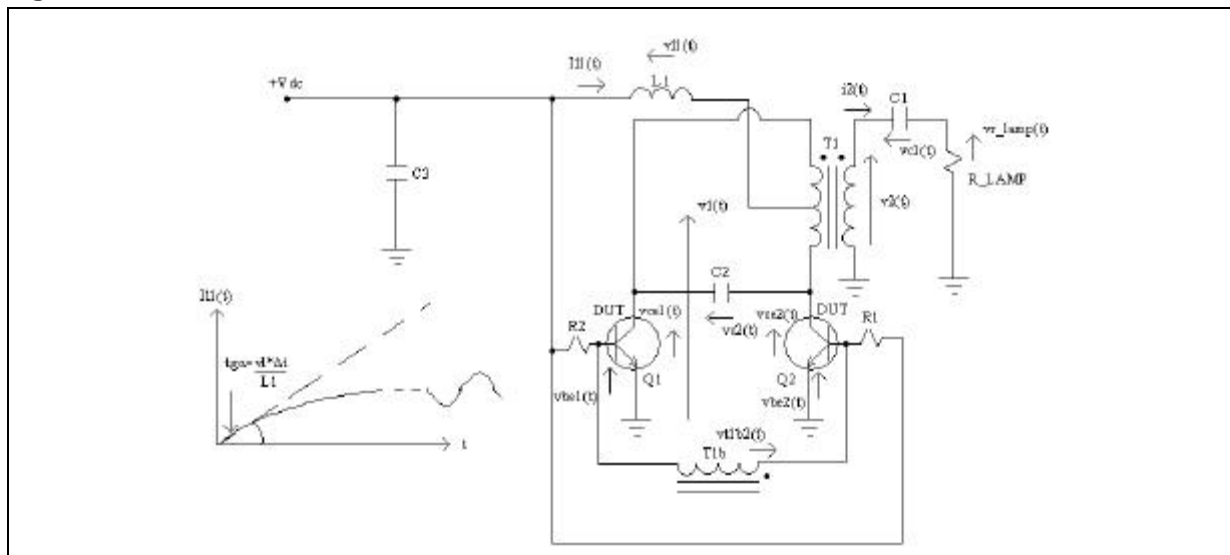


After the strike, 'I' generates the current  $i_2$  and, at the beginning, the same  $i_2$  can be written as:

$$i_2 = \frac{V_2}{R_{Lamp}} \quad (6.29)$$


because the capacitor  $C_1$  is discharged. Immediately after,  $C_1$  gets charged and  $i_2$  decreases to zero until the voltage across  $C_1$  reaches the maximum value. At this time, the current  $i_2$  inverts its direction and the capacitors  $C_1$  start discharging until the charge inside it becomes zero and the current  $i_2$  reaches its maximum negative value. Furthermore, when  $i_2$  inverts itself, also the voltage across the third winding inverts its direction so that  $Q_2$  switches off and  $Q_1$  switches on and 'I' flows through the other half primary winding of the transformer  $T_1$  (see fig. 11).

**Figure 12: PUSH-PULL Current FED Converter Schematic Circuit with  $v_{c1}$ ,  $v_{c2}$ ,  $i_2$ , and  $v_{t1b2}$  Theoretical Waveforms**

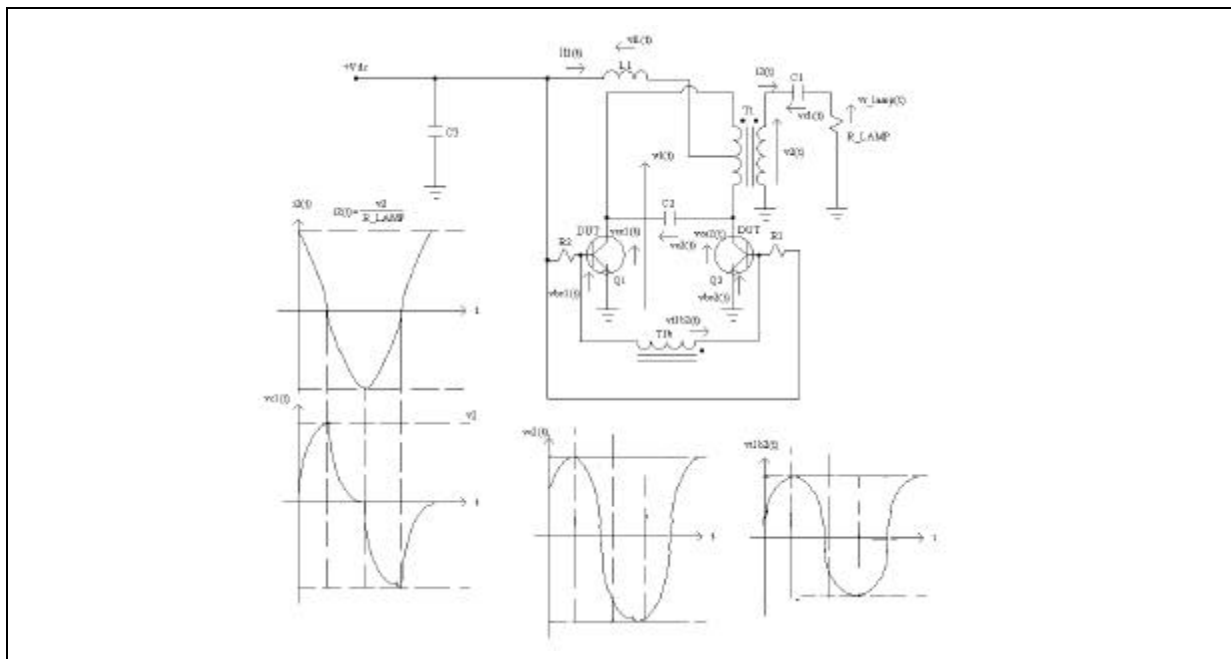

In the above graph,  $v_{c2}$  is the voltage between the vices of the  $Q_1$  and  $Q_2$  collectors. The maximum value of such voltage is twice  $v_1$ , where  $v_1$  is the voltage between the vices of the central point of the primary winding of  $T_1$  and the reference. The voltage  $v_1$  is a half positive sine wave and this reaches the maximum value when  $Q_1$  or  $Q_2$  are on, while it drops to zero during the turn-off and the turn-on of the same transistors (see fig. 13).


Figure 13: PUSH-PULL current FED converter schematic circuit with  $v_{c2}$ ,  $v_1$ , and  $v_{L1}$  theoretical waveforms

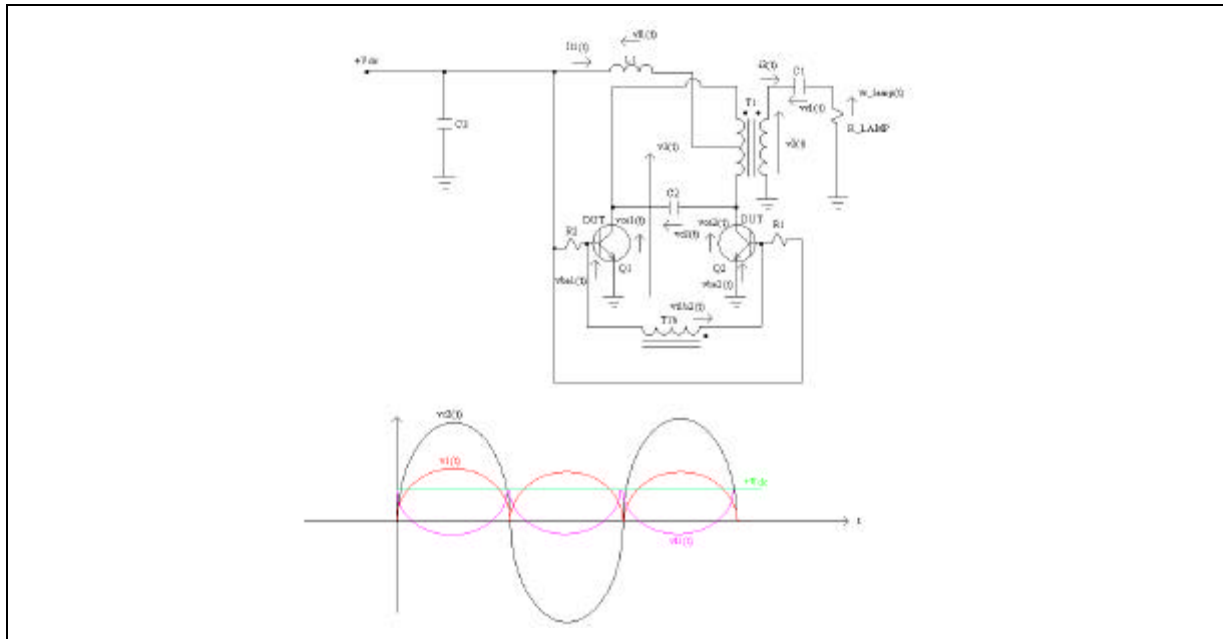

The figure above also highlights the  $v_{L1}$  voltage. This is the voltage across  $L_1$  and it is achieved considering the difference between  $V_{dc}$  and  $v_1$ .

Now focusing the attention on only one half-period of  $v_1$  as showed in fig. 14, it is evident that the area  $A2$  must be equal to the area  $A1$  because  $v_1$  and  $V_{dc}$  must have the same average value.

Figure 14:  $v_1$  waveforms

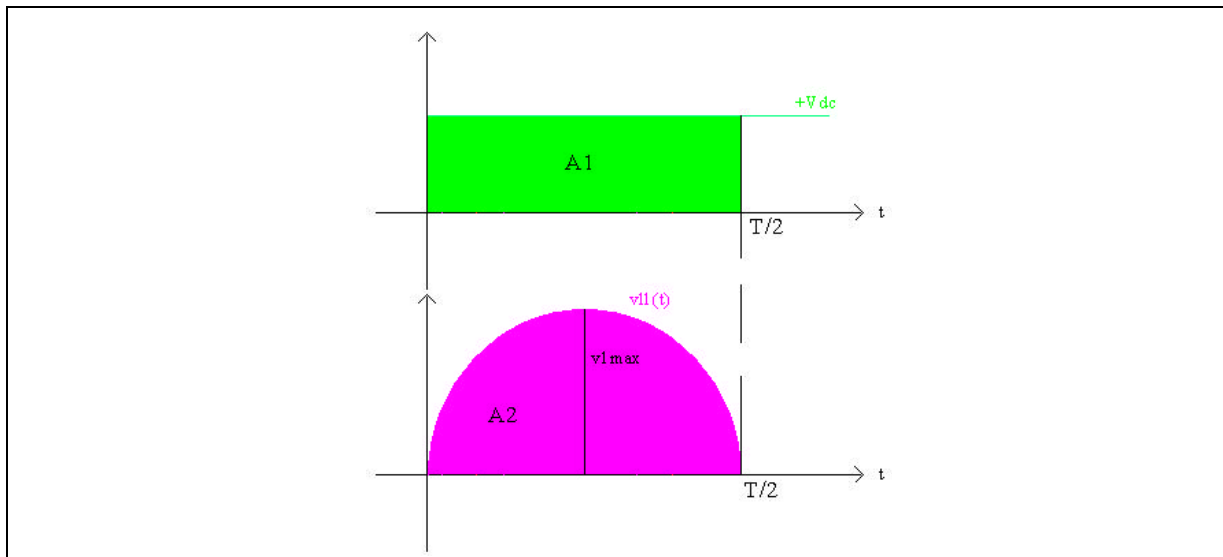

$A1$  can be written as:

$$A1 = V_{dc} \frac{T}{2} \tag{6.30}$$

A2 can be written as:

$$A_2 = \int_0^{\frac{T}{2}} V_{1\max} \sin\left(\frac{2p}{T}t\right) dt = \tag{6.31}$$

$$= \frac{T}{2p} V_{1\max} \left[-\cos\left(\frac{2p}{T}t\right)\right]_0^{\frac{T}{2}} = \frac{T}{p} V_{1\max}$$

considering:

$$A_1 = A_2 \tag{6.32}$$


$$V \frac{T}{2} = \frac{T}{p} V_{1\max} \Rightarrow V_{1\max} = \frac{p}{2} V_{dc} \tag{6.33}$$

$V_{c2\max}$  can be written as:

$$V_{2\max} = p \cdot V_{dc} \tag{6.34}$$

$V_{c2\max}$  is also the maximum voltage value between the collector-emitter vices of  $Q_1$  or  $Q_2$ . The theoretical voltages and the currents waveforms of  $Q_1$  or  $Q_2$  are shown below.

Figure 15:  $Q_1$  and  $Q_2$  theoretical waveforms

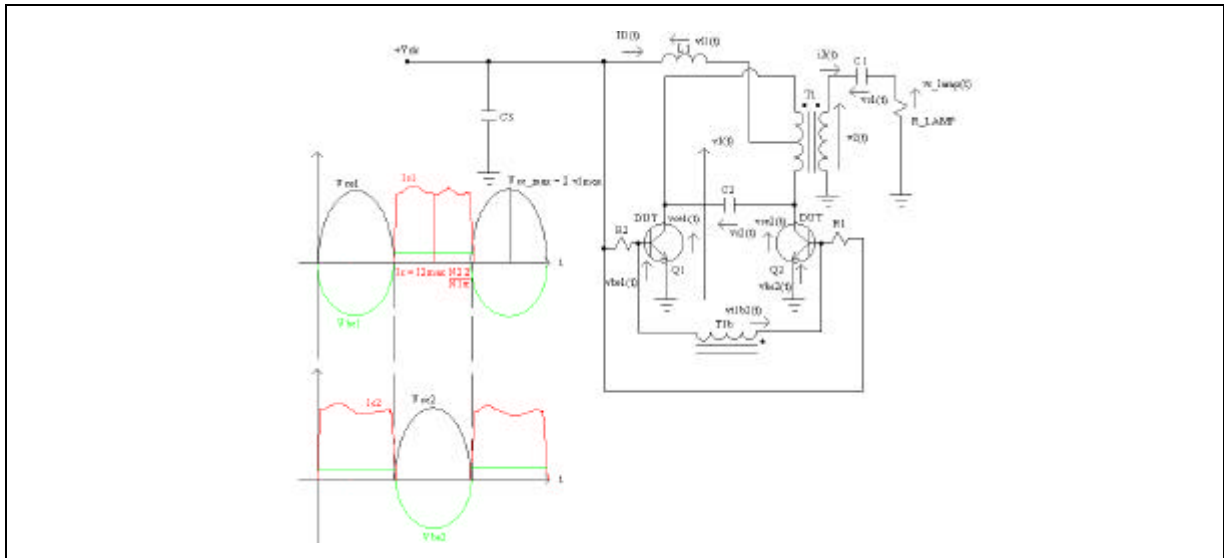

$I_{c1}$  and  $I_{c2}$  can be written as:

$$I_{c1\max} = I_{2\max} \frac{N_2}{N_1/2} \tag{6.35}$$


$$P_{out} = R_{Lamp} \left(\frac{I_{2\max}}{\sqrt{2}}\right)^2 \tag{6.36}$$

$$I_{2max} = \sqrt{2 \frac{P_{out}}{R_{Lamp}}} \quad (6.37)$$

$$I_{c1max} = \frac{N_2}{N_1/2} \sqrt{2 \frac{P_{out}}{R_{Lamp}}} \quad (6.38)$$

$R_1$  and  $R_2$  can be also used to adjust the  $I_{b1on}$  and  $I_{b2on}$ .  
Now focusing the attention on only one half-period of  $v_{L1}$ :

Figure 16:  $v_{L1}$  theoretical waveform detail

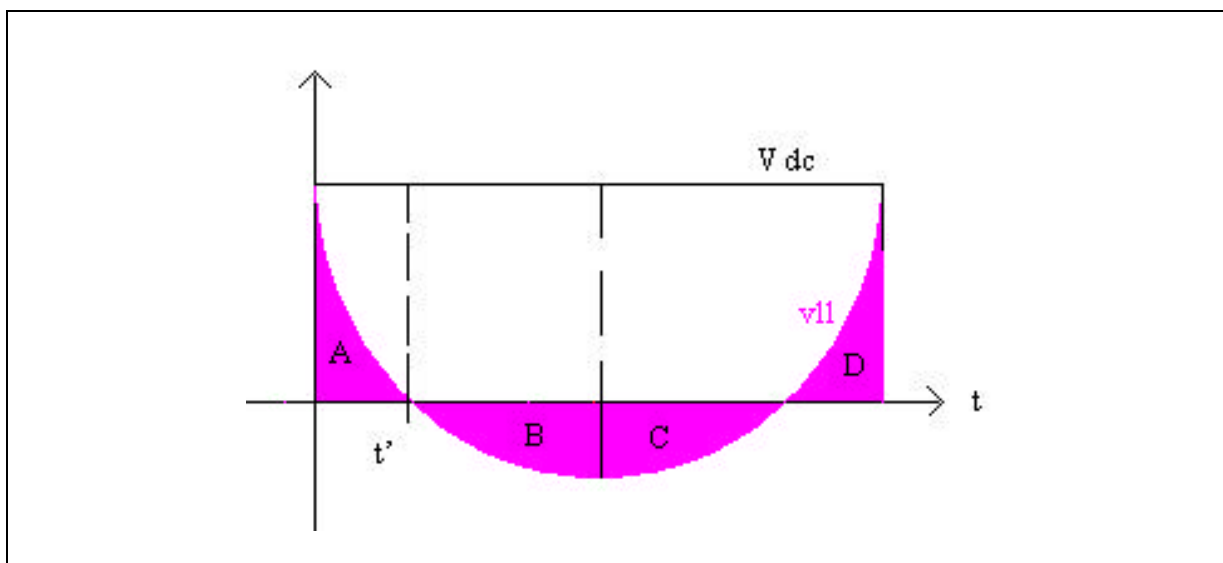

After the lamps strike 'I' fluctuates around its average value:

$$I_{max} - I = I - I_{min} = \Delta I \quad (6.39)$$

because:

$$v_{med} = 0 \quad (6.40)$$

where  $v_{med}$  is the average value of  $L_1$ .

$v_{med}$  can be written as:

$$v_{med} = \frac{(A + D - B - C)}{T} \quad (6.41)$$

T is the period of  $v_{L1}$ .

$$A + D = B + C \quad (6.42)$$

$$A = B \quad (6.43)$$

$$C = B, D = A \quad (6.44)$$

$v_{L1}$  can be written as:

$$v_{L1} = V_{dc} - \frac{p}{2} V_{dc} \cdot \text{sen}\left(\frac{2 \cdot p}{T} t\right) \quad (6.45)$$

$t'$  is the time when  $v_{L1}$  is zero:

$$0 = V_{dc} - \frac{p}{2} V_{dc} \cdot \text{sen}\left(\frac{2 \cdot p}{T} t'\right) \quad (6.46)$$

$$t' = \frac{T}{2 \cdot p} \arcsen\left(\frac{2}{p}\right) \quad (6.47)$$

Considering that:

$$\Delta I_{\text{max}\%} = \frac{\Delta I_{\text{max}}}{I_{\text{med}}} \quad (6.48)$$

$$\Delta I_{\text{max}\%} \cdot I_{\text{med}} = \Delta I_{\text{max}} \quad (6.49)$$

Considering the Lenz law:

$$v_{\text{med}} = L_{\text{min}} \frac{\Delta I_{\text{max}}}{\Delta t} \quad (6.50)$$

It is possible to achieve  $L_{\text{min}}$  (the minimum  $L_1$  value that allows the established current ripple to be obtained) as:

$$L_{\text{min}} = \frac{\Delta t}{\Delta I_{\text{max}}} v_{\text{med}} \quad (6.51)$$

During the time interval 0- $t'$   $I$  increases by:

$$\frac{\Delta I_{\text{max}}}{2} \quad (6.52)$$

$v_{\text{med}}$  can be written as:

$$v_{\text{med}} = \frac{1}{t'} \int_0^{t'} v_{L1} \cdot dt = \frac{1}{t'} \int_0^{t'} \left[ V_{dc} - \frac{p}{2} V_{dc} \cdot \text{sen}\left(\frac{2 \cdot p}{T} t\right) \right] dt \quad (6.53)$$

$$v_{\text{med}} = \frac{1}{t'} \left\{ V_{dc} \cdot t' - \frac{T}{4} V_{dc} [1 - \cos\left(\frac{2 \cdot p}{T} t'\right)] \right\} \quad (6.54)$$

$L_{\text{min}}$  can be written as:


$$L_{\text{min}} = \frac{2}{\Delta I_{\text{max}}} \left\{ V_{dc} \cdot t' - \frac{T}{4} V_{dc} [1 - \cos\left(\frac{2 \cdot p}{T} t'\right)] \right\} \quad (6.55)$$

7. EXAMPLE OF AN EMERGENCY LAMP APPLICATION

The following example takes into consideration a real emergency lamp application with a PUSH-PULL current FED converter topology using a 24W lamp and powered with 6 V<sub>dc</sub> with STSA851.

The graph below shows I<sub>c</sub>, I<sub>b</sub>, and V<sub>ce</sub> waveforms of the STN851 device when the lamp is connected.

Figure 17: Steady state of STSA851

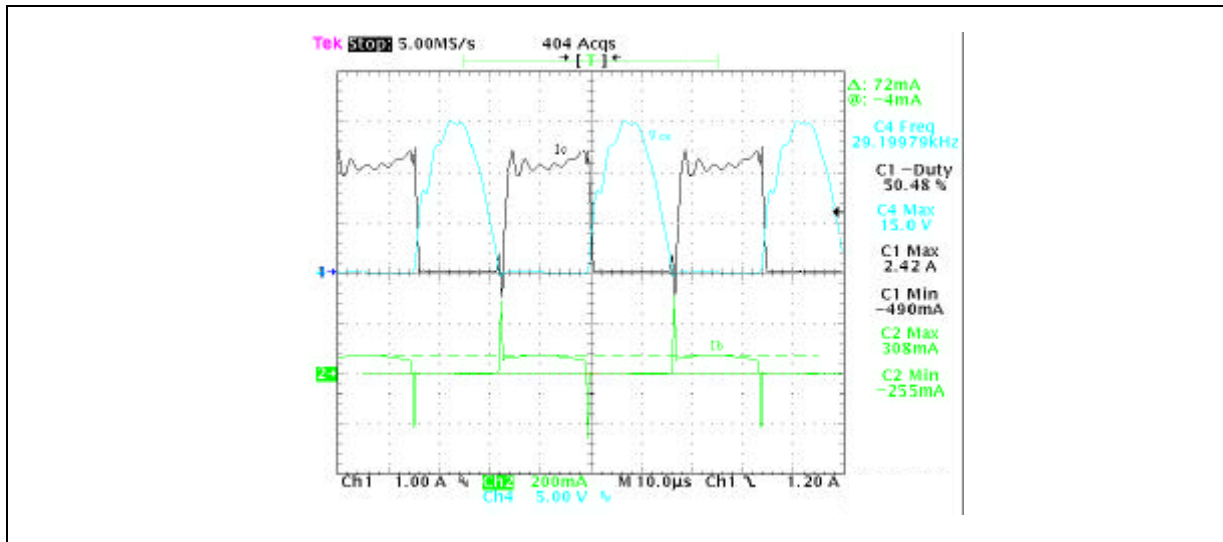

The following graphs show the turn-off and turn-on switch modes respectively.

Figure 18: Turn-off of STSA851


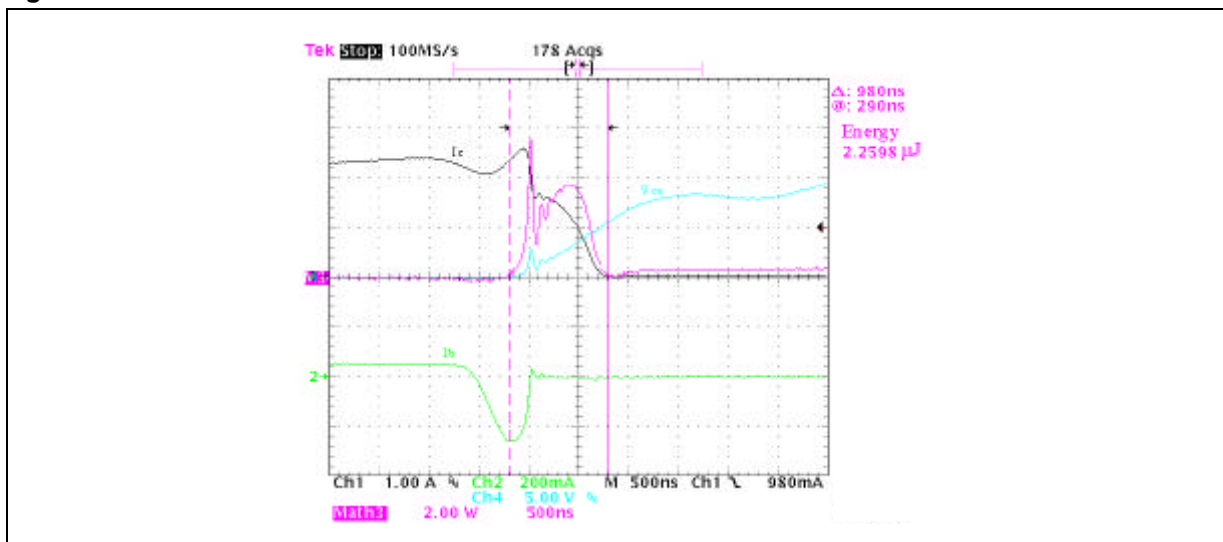


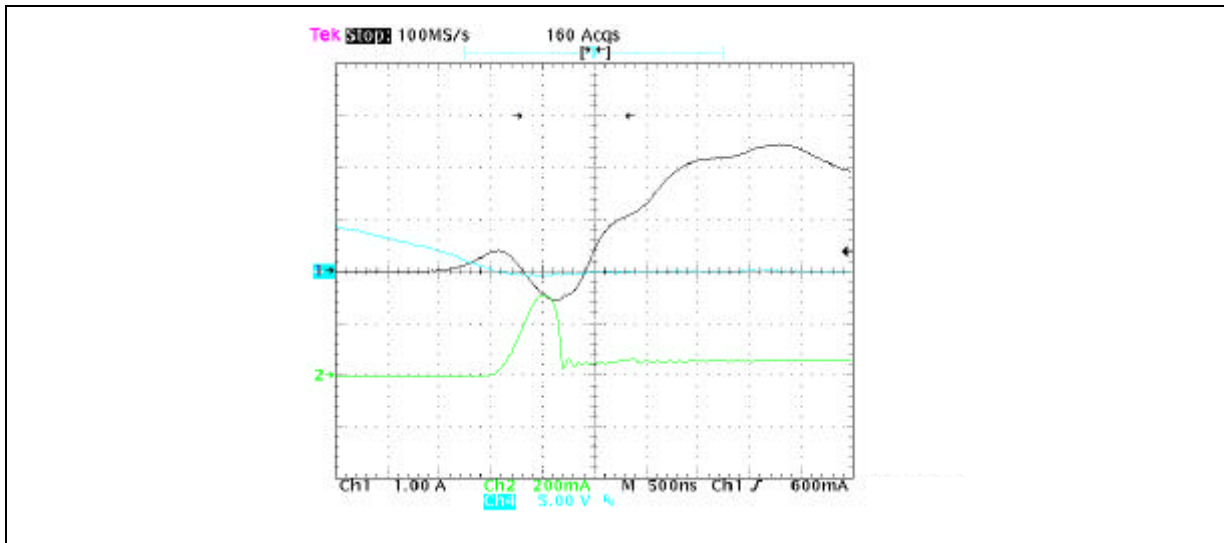


Figure 19: Turn-on of STSA851



In these graphs it is possible to see that the operation frequency is around 30KHz,  $I_c$  is around 2.4A and that  $I_{bon}$  is around 70mA. The  $I_b$  spike during the turn-on switch mode is due to the collector-base junction charge, while, the negative  $I_b$  spike during the turn-off switch mode is due to the storage charges extraction. Furthermore, in this example, during the turn-off switch mode, the dissipated energy is due to a  $C_2$ , discharging on the power bipolar device, that decelerates  $I_c$  decreasing. Sometimes, in order to decrease the turn-off dissipated energy, two capacitors between the vices of the collector-emitter of both devices are connected.

The figure below shows the steady state of the STSA851 device without the lamp.

Figure 20: Steady state of STSA851 without the lamp

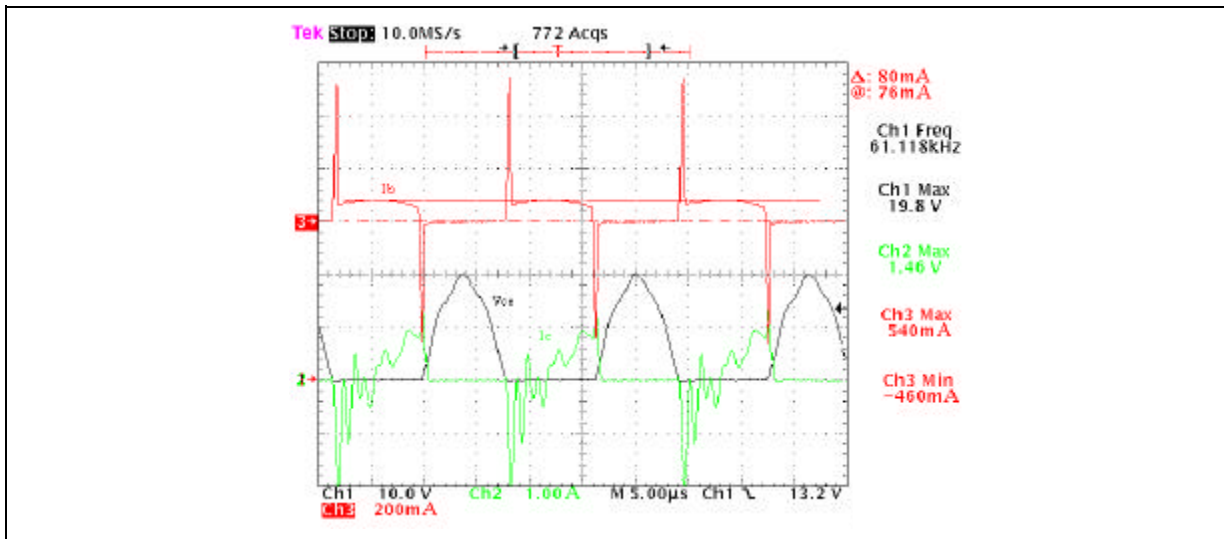

In this case the operation frequency is around 60 KHz.

The current and the voltage values measured on the power bipolar device are inside the STSA851 specifics.

The next graphs show the  $v_{L1}$ , 'I' and  $v_{C2}$  waveforms with and without lamp respectively.

Figure 21:  $v_{L1}$  and I Waveforms With Lamp Connected

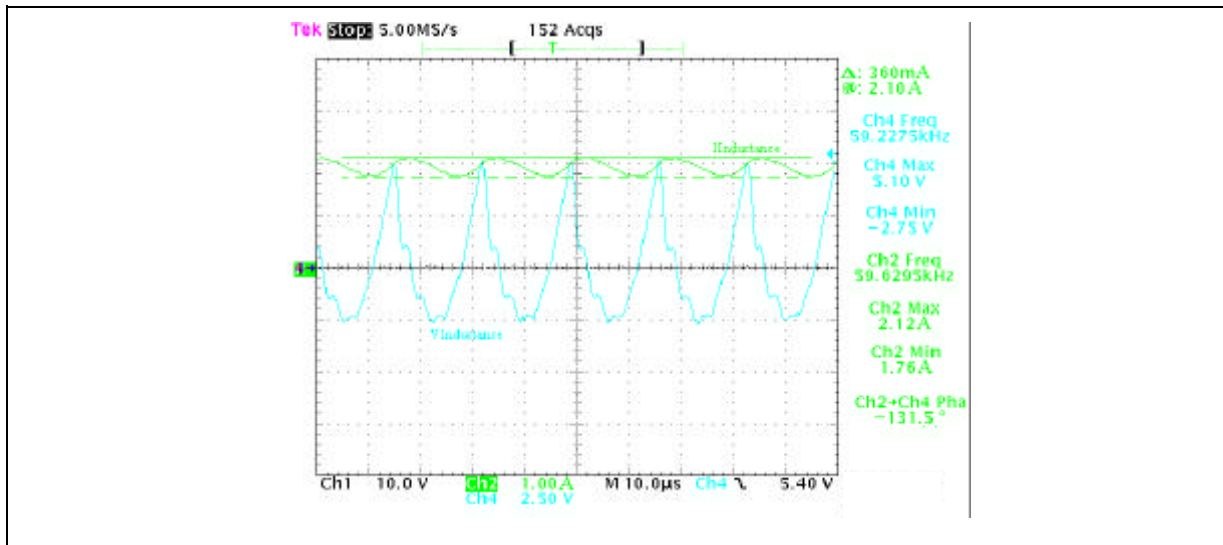


Figure 22:  $v_{C2}$  Waveform With Lamp Connected

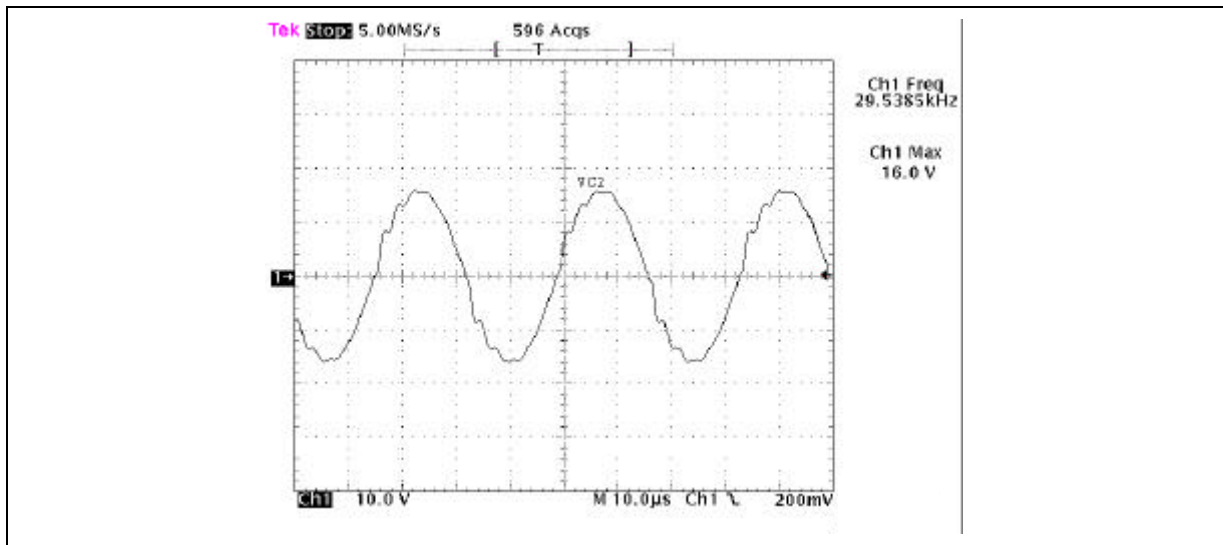


Figure 23:  $v_{L1}$  and I Waveforms Without Lamp Connected


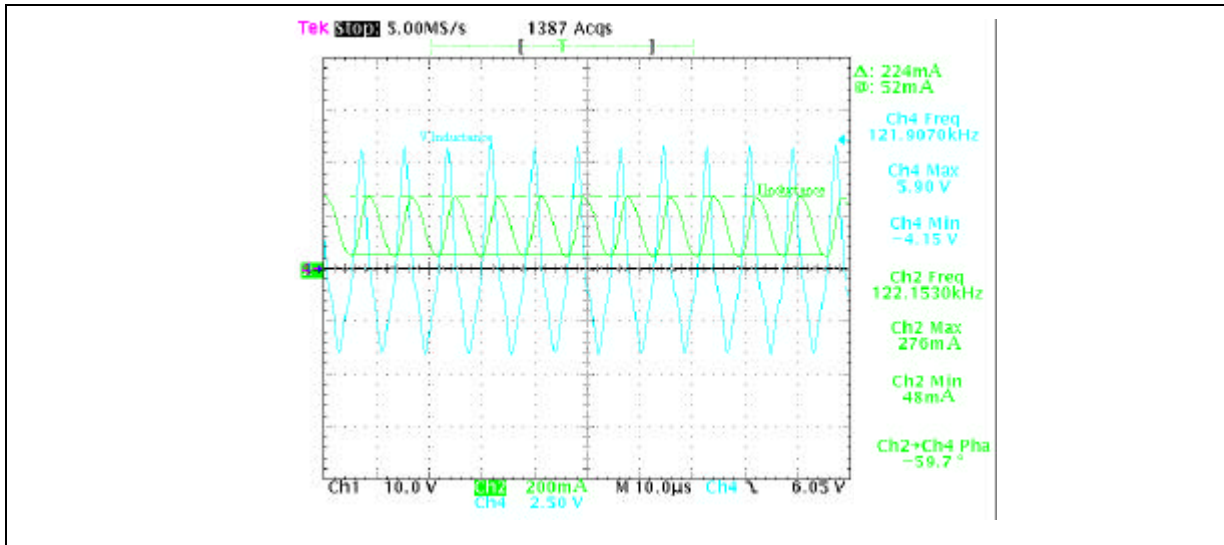



Figure 24:  $v_{c2}$  Waveform Without Lamp Connected

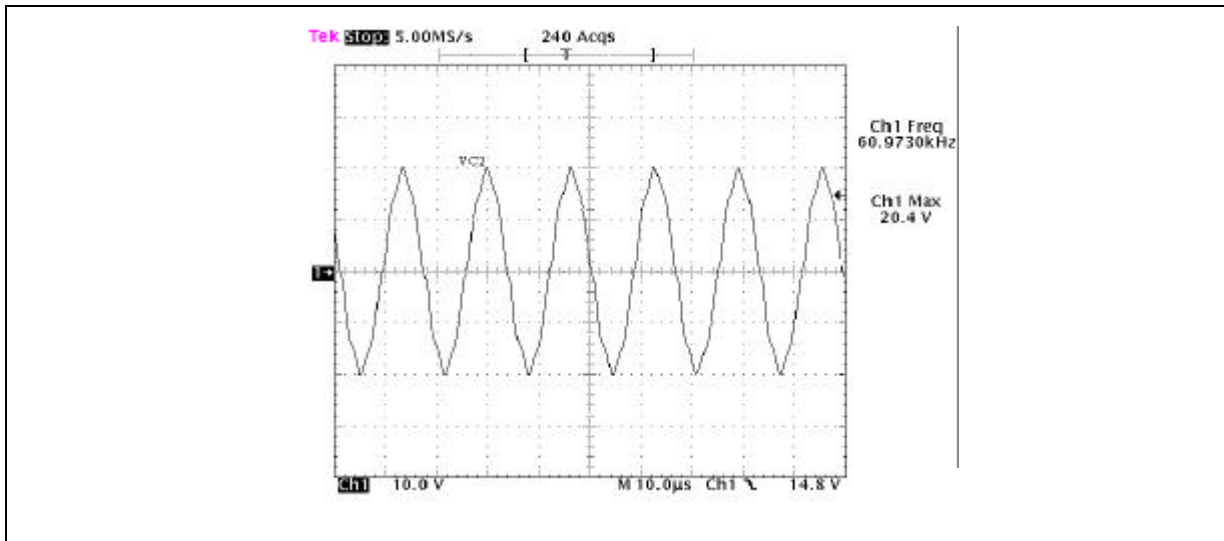

### 8. FORWARD VOLTAGE FED CONVERTER TOPOLOGY

As previously exposed, another topology solution for emergency lighting applications is the FORWARD voltage FED converter solution that uses a transformer with three windings.

**Figure 25: FORWARD Voltage FED Converter Schematic Circuit**

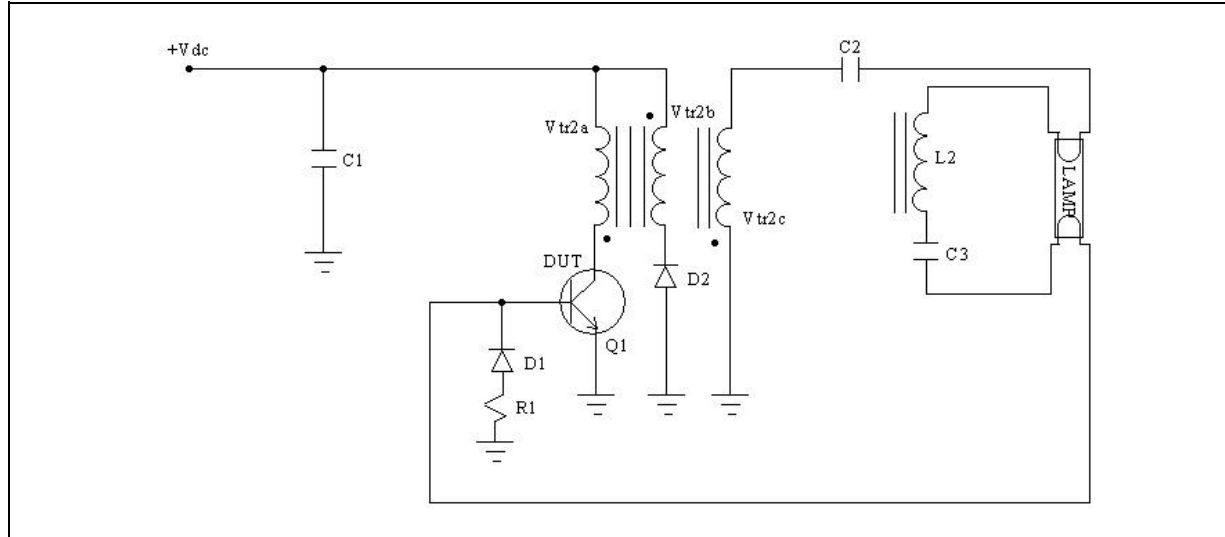

As shown in the PUSH-PULL current FED converter solution, the components values of capacitors, resistors, and inductors are designed in order to have an operation frequency of around 30 KHz, after the lamp strike and before too, in order to supply the right voltages to the load before and after the lamp strike considering the voltage value of the battery.

When the board is powered, a suitable trigger circuitry, usually consisting of a small signal bipolar transistor and a resistor, enables  $Q_1$  and, immediately after, a current flows through the  $V_{tr2a}$  primary winding of the transformer  $T_{r2}$  and the same transistor. During the  $Q_1$  on state, the input battery voltage  $V_{dc}$  is applied to the  $V_{tr2a}$  vices winding and the same voltage appears in the vice of the second winding  $T_{r2b}$ , in fact, the coils number of the both windings is the same, but no current flows through  $T_{r2b}$  because the diode  $D_2$  is disabled. At the same time, a voltage appears in the winding  $V_{tr2c}$  and a current flows through the same winding depending on the output impedance. The  $V_{tr2c}$  voltage depends on the input voltage battery  $V_{dc}$  by means of the  $N_2/N_1$  rapport.

In particular,  $V_{tr2}$  can be written as:

$$V_{tr2c} = V_{dc} \frac{N_2}{N_1} \quad (8.1)$$

$I_{1eff}$ , the RMS of the primary winding current, can be written as:

$$I_{1eff} = I_{2eff} \frac{N_2}{N_1} \quad (8.2)$$


where  $N_1$  and  $N_2$  are the turn numbers of  $V_{tr2a}$  and  $V_{tr2c}$  respectively,  $I_{2eff}$  is the RMS of the lamp current and can be written as:

$$I_{2eff} = \frac{V_{tr2c}}{Z_{eq}} \quad (8.3)$$

where  $Z_{eq}$  is the output impedance.


At the beginning, before the lamp strike, the lamp resistance is very high and the equivalent circuit can be showed as in the figure below.

**Figure 26: Schematic Circuit Before the Lamp Strikes**

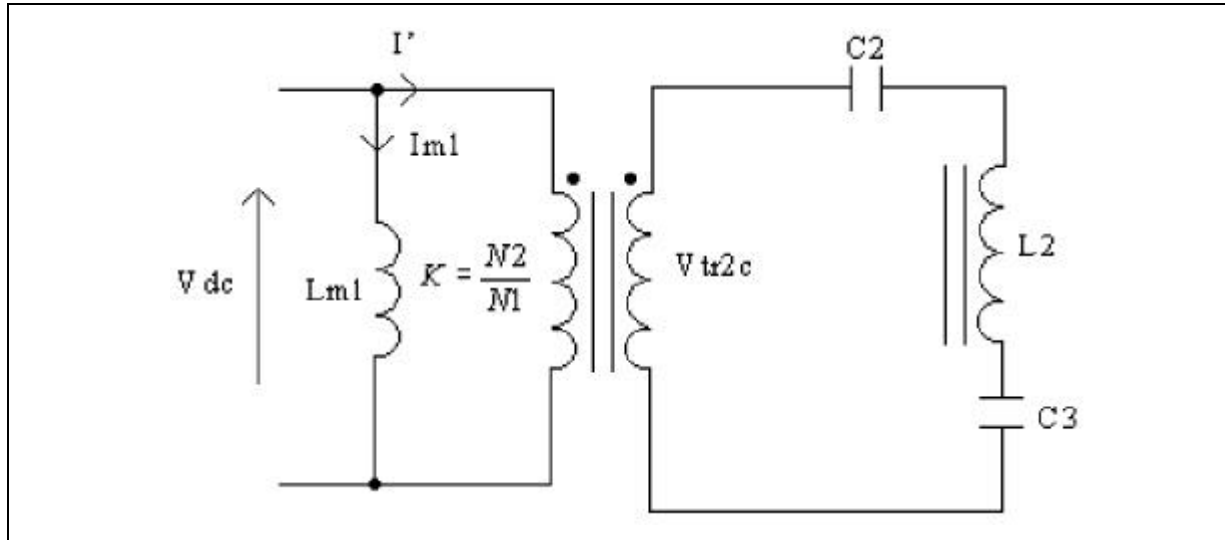


Usually, the capacitor value of  $C_3$  is higher compared to the same of  $C_2$ , so that the simplified schematic circuit can be showed as in fig. 27.

**Figure 27: Simplified Schematic Circuit Before the Lamp Strikes**

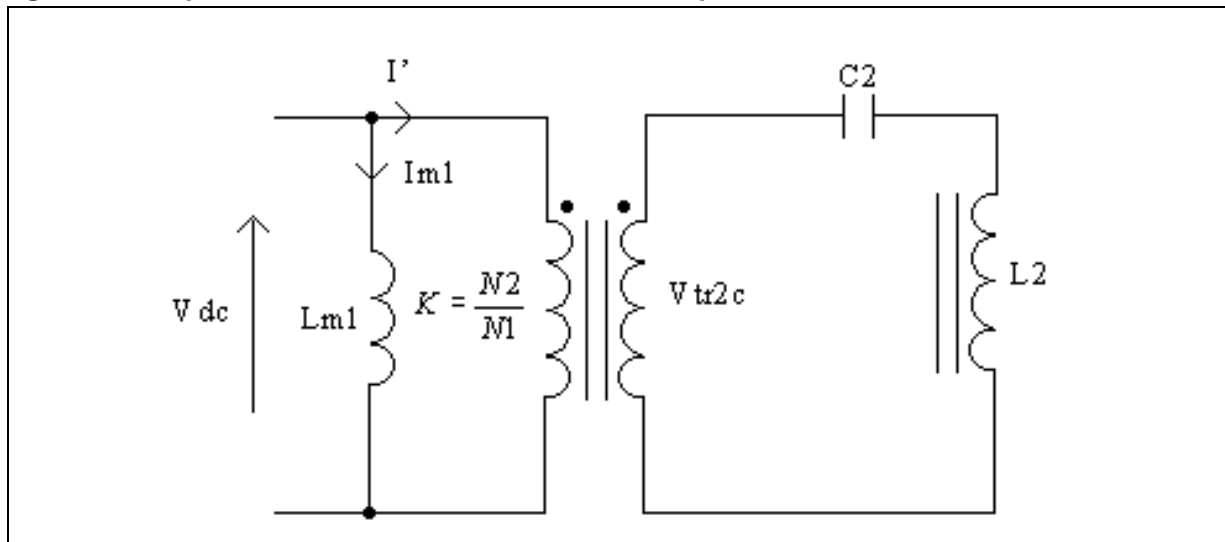

It is also possible to consider an equivalent circuit as in fig. 28 where the output impedance is transferred in the primary of the transformer.

**Figure 28: Equivalent Schematic Circuit Before the Lamp Strikes**

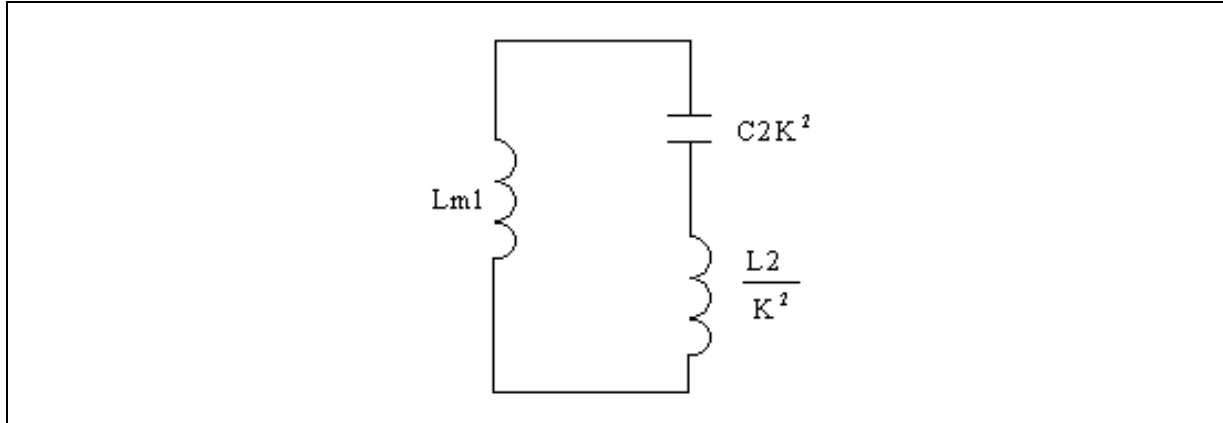

The series net  $K^2 C_2 - L_2 / K^2$  can be written as:

$$j \frac{\omega \cdot L_2}{K^2} - j \frac{1}{\omega \cdot K^2 C_2} = j \frac{\omega^2 L_2 C_2 - 1}{\omega \cdot K^2 C_2} \quad (8.4)$$

The equivalent impedance can be written as:

$$Z_{eq} = j \frac{L_1 L_2 C_2 - L_1}{C_2 (L_1 K^2 + L_2) - 1} \quad (8.5)$$


Deriving  $Z_{eq}$  from  $\omega$  it is possible to obtain the resonance frequency.

$$\frac{\partial Z_{eq}}{\partial \omega} = 0 \quad (8.6)$$

$$\omega^2 = 1 / L_2 C_2 \Rightarrow f = 1 / 2 \cdot \pi \sqrt{L_2 C_2} \quad (8.7)$$


In order to know the resonance frequency after the lamp starts up, it is necessary to consider the schematic circuit with a short circuit condition.

**Figure 29: Schematic circuit considering a short circuit condition**

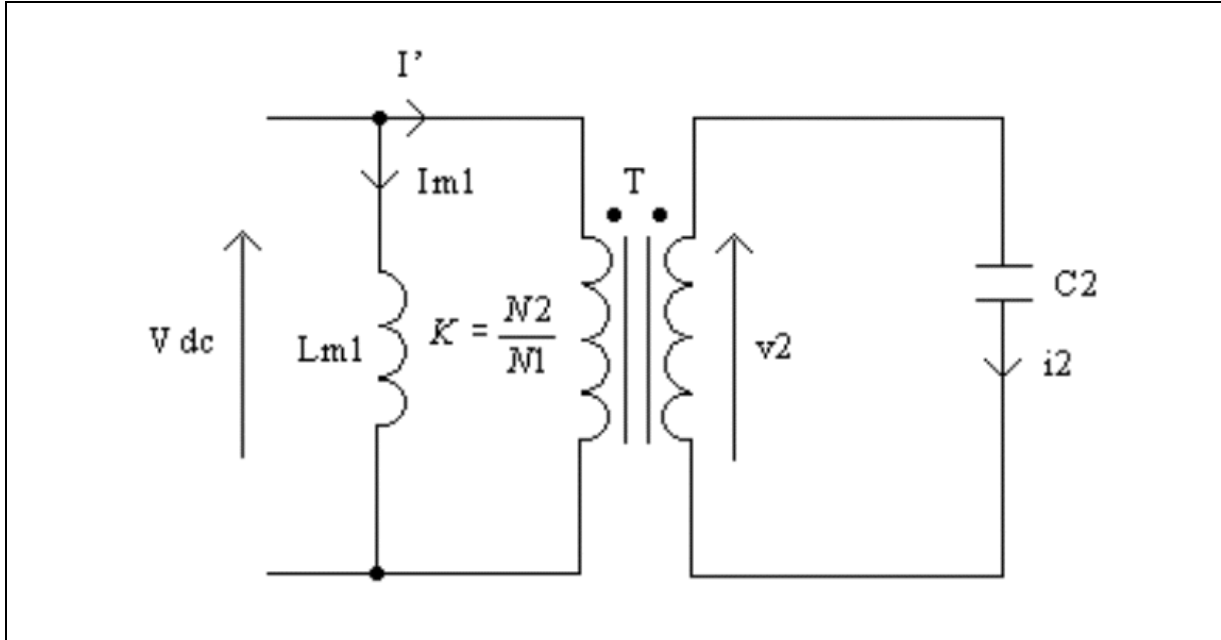

Furthermore, it is possible to consider the equivalent schematic circuit as in fig. 30 transferring the output impedance in the primary winding.

**Figure 30: Equivalent Schematic Circuit Considering a Short Circuit Condition**

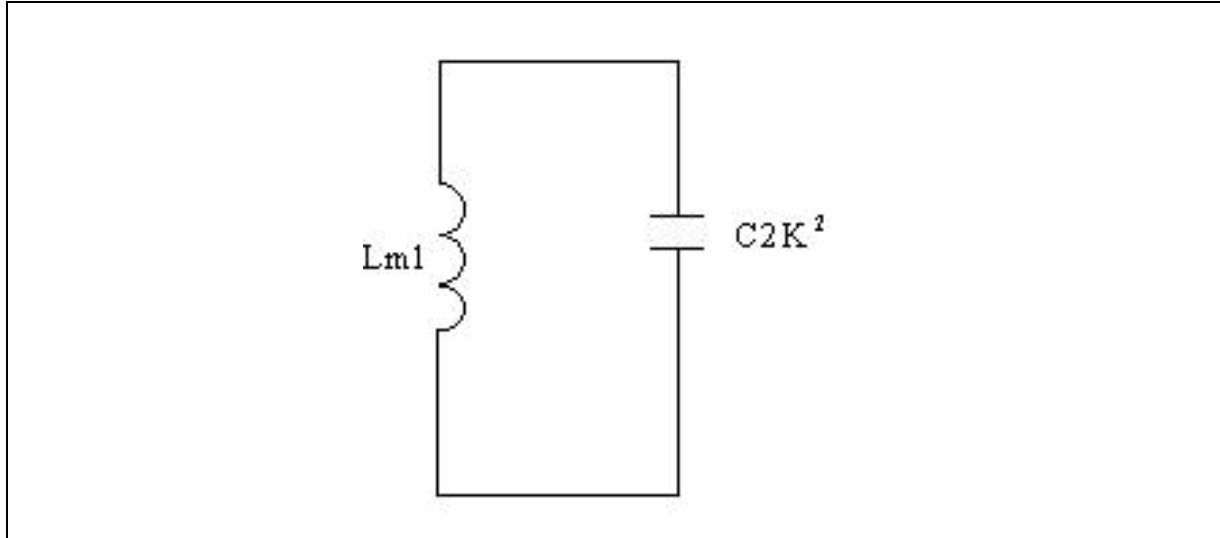

The resonance frequency in this condition can be written as:

$$\omega^2 = \frac{1}{L_1 C_2 K^2} \Rightarrow f = \frac{1}{2 \cdot \pi \sqrt{L_1 C_2 K^2}} \quad (8.8)$$


Usually, the resonance frequency considering the output short circuit condition is lower compared to the resonance frequency before the lamp start-up condition. The resonance frequency after the lamp start-up has got a value which is between the frequency before the lamp start-up and the output short circuit frequency.

$$\frac{1}{2 \cdot \pi \sqrt{L_1 C_2 K^2}} < f < \frac{1}{2 \cdot \pi \sqrt{L_2 C_2}} \quad (8.9)$$

However, after the start-up, the resonance frequency is almost equal to the resonance frequency before the lamp start-up. Fig. 31 shows the resonance frequency after the lamp start-up considering several loads.



Figure 31: Resonance Frequency After the Lamp Start-up vs. Resistance Load

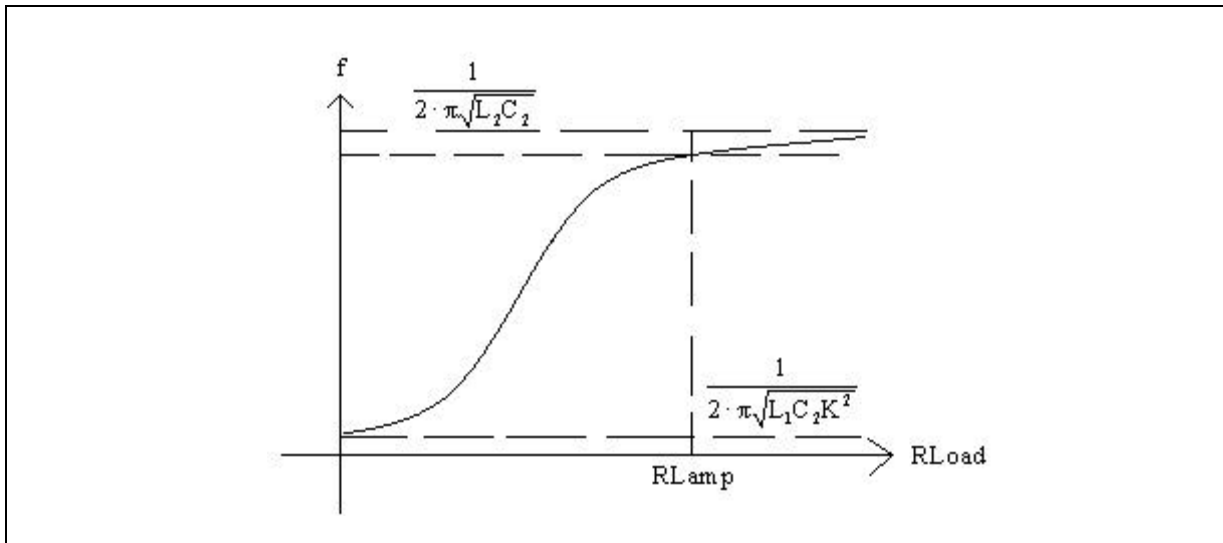

During the positive half-wave,  $i_2$  is the same as  $I_b$  because this flows through the base of the power bipolar transistor; instead, during the negative half-wave, when the current inverts its direction,  $i_2$  flows through the net  $R_1$ -  $D_1$ . At the same time, the voltages across  $T_{r2a}$ ,  $T_{r2b}$  and  $T_{r2c}$  windings invert their directions,  $Q_1$  switches off,  $I_c$  drops to zero, and  $V_{ce}$  increases up to:

$$V_{ce} = 2V_{dc} \quad (8.10)$$


the sum of the input battery voltage  $V_{dc}$  and the third winding voltage:

$$V_{tr2a} = V_{dc} \quad (8.11)$$

However, after  $Q_1$  switches off, an extra-voltage can appear across collector-emitter vices due to a quick decrease in the  $I_c$  that flows through the  $V_{tr2a}$  winding. In order to avoid this effect,  $V_{tr2b}$  enables  $D_2$  and the current passing through it creates a magnetic force  $N_3 I_3$  opposed to  $N_1 I_c$  ( $N_3$  and  $I_3$  are the turn number and the current that flows through  $T_{r2b}$ ).


The graph below shows the output schematic circuit and the theoretical waveforms before the lamp strike.

**Figure 32: Output Schematic Circuit Before the Lamp Strike and Theoretical Waveforms of the Main Output Electrical Parameter**

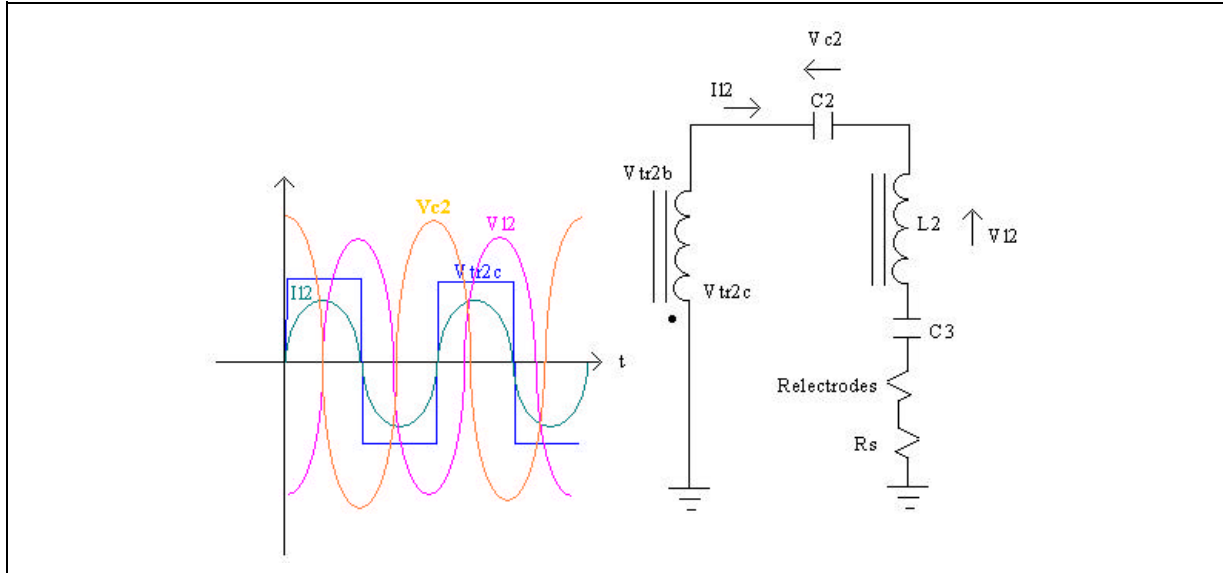

The voltage across  $V_{tr2c}$  generates an  $i_2$  having the same phase.  $v_{c2}$  (the voltage across  $C_2$ ) is  $+90^\circ$  out-phase compared to the  $i_2$ , while  $v_{L2}$  (the voltage across  $L_2$ ) is  $-90^\circ$  out-phase compared to  $i_2$ . The graph below shows the  $I_b$ ,  $V_{ce}$  and  $I_c$  theoretical waveforms of  $Q_1$ .

**Figure 33:  $Q_1$  Theoretical Waveforms**

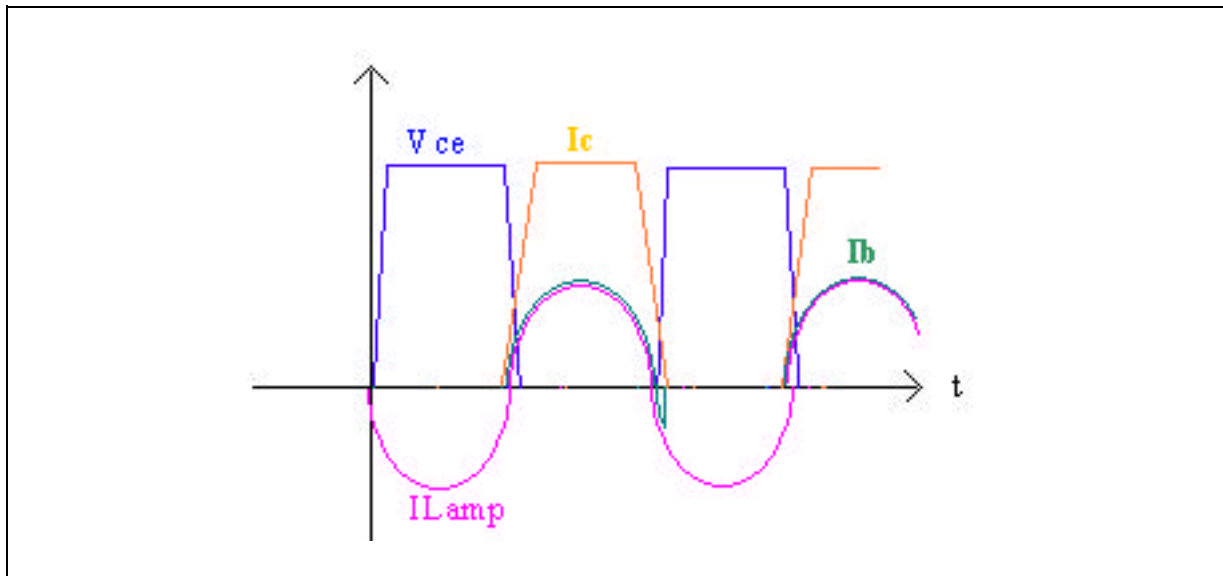


**Note:** a circuit similar to the Forward Voltage FED Converter shown in Fig. 25 is also described in the Italian Patent N.1285621 in the name of Beghelli S.p.A.

## 9. TRANSFORMER DESCRIPTION

The transformer has three windings. The primary winding vices are connected to the input voltage and the other vice to the collector of  $Q_1$ , while the secondary winding vices are connected to the load. The third winding vices are connected between the input voltage and the cathode of  $D_2$ . The schematic of the transformer can be shown as in fig. 34.

**Figure 34: Transformer Detail**

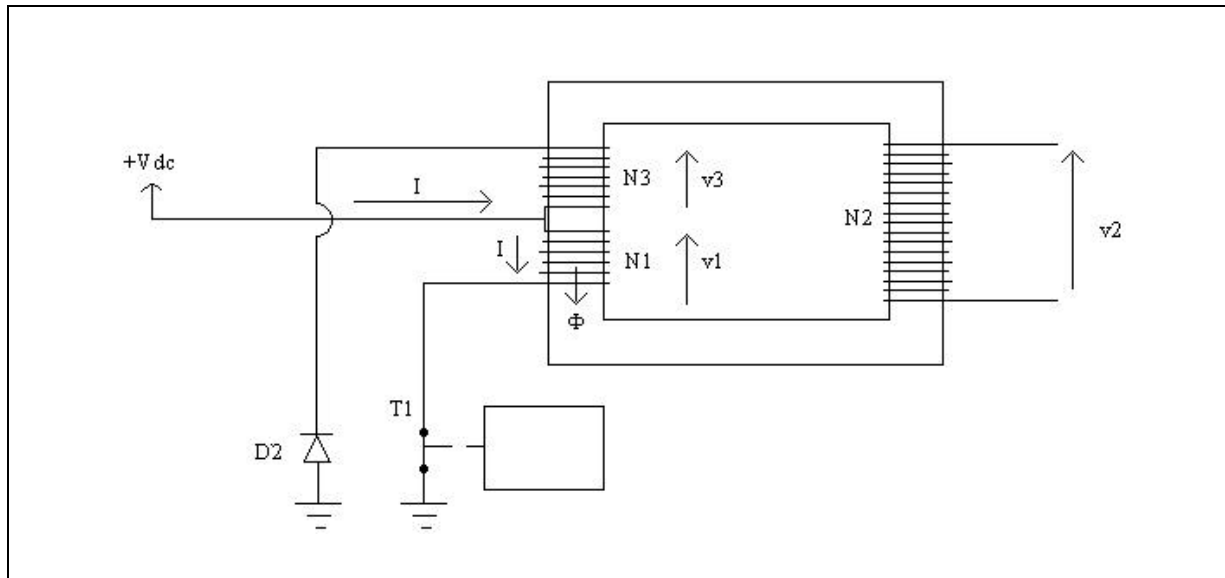

The FORWARD converter works during the  $Q_1$  on state (in this graph the switch  $T_1$  is the equivalent component of  $Q_1$ ). In such operation condition, current flows through the turn  $N_1$  and a flux is generated.

$$\Phi = \frac{N_1 I}{\mathfrak{R}} \quad (9.1)$$

This flux flows through the magnetic core of the transformer creating a link respectively with the turns  $N_2$  and  $N_3$  and it generates the voltages  $v_2$  and  $v_3$ .

$$v_3 = -N_3 \frac{\Delta\Phi}{\Delta t} \quad (9.2)$$

$$v_2 = -N_2 \frac{\Delta\Phi}{\Delta t} \quad (9.3)$$

However, during the  $Q_1$  on state, no current flows through the third winding because the diode  $D_2$  is disabled, while output current flows through the secondary winding and the load. The voltage across the primary winding, equal to  $V_{dc}$ , can be written as:

$$v_1 = V_{dc} = -L_{m1} \frac{\Delta I}{t_{on}} \quad (9.4)$$


$L_{m1}$  is the inductance of the primary winding and  $t_{on}$  is the time during the  $Q_1$  on state.

When the secondary winding current inverts its direction,  $Q_1$  switches off, the current 'I' suddenly

becomes zero and an overvoltage appears across the turn  $N_1$ . However, during the  $Q_1$  switching off, a magnetic force appears across the third winding opposing the primary winding magnetic force and avoiding the extra voltage on  $Q_1$  (see fig. 35).


$$N_1 I = N_3 I_3 \quad (9.5)$$

Figure 35: Transformer Detail When  $T_1$  Switches on

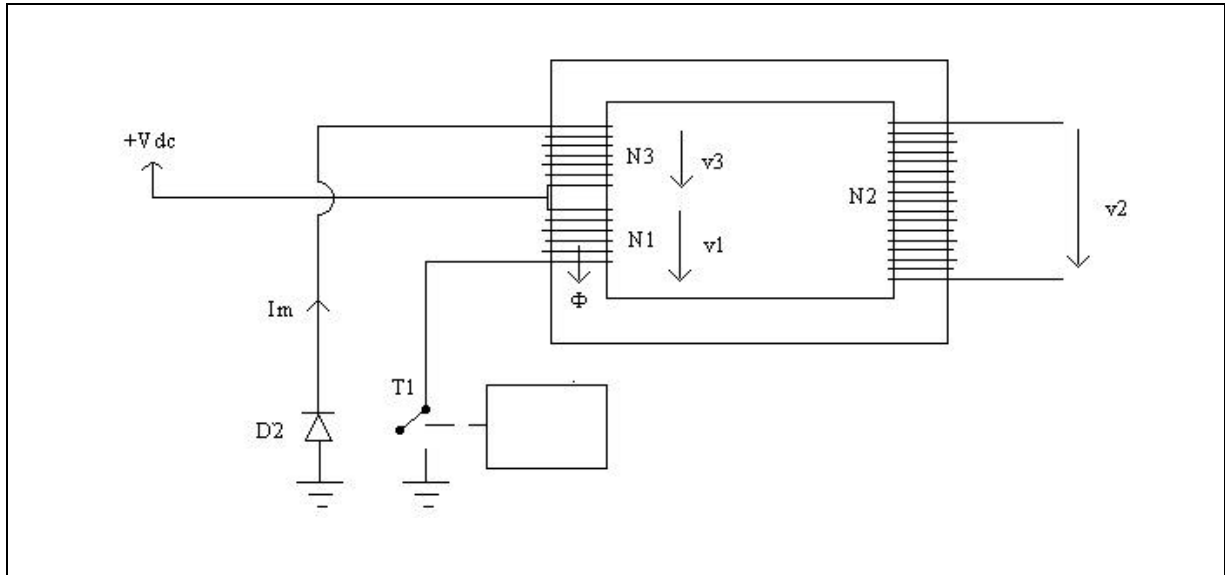


It is important to highlight that the current 'I' is the sum of the currents  $I_m$  and  $I'$  (see fig. 36). The extra voltage on  $Q_1$  is due to  $I_m$ .

Figure 36: Detail of the Transformer Highlighting  $I_{m1}$  and  $I'$

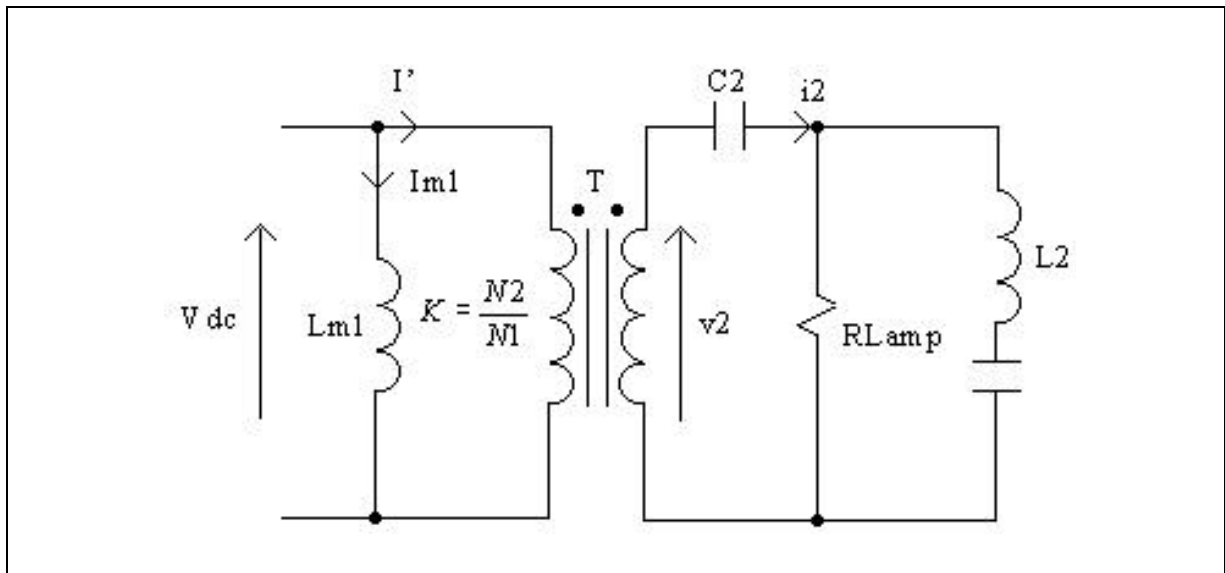


In the FORWARD converter it is important to consider the right turn  $N_3$  and the right duty cycle, it is possible to have an increasing current  $I_m$  and a saturation of the transformer core might occur.

**Figure 37: Theoretical Behavior of  $I_m$  Involving the Transformer Core Saturation**

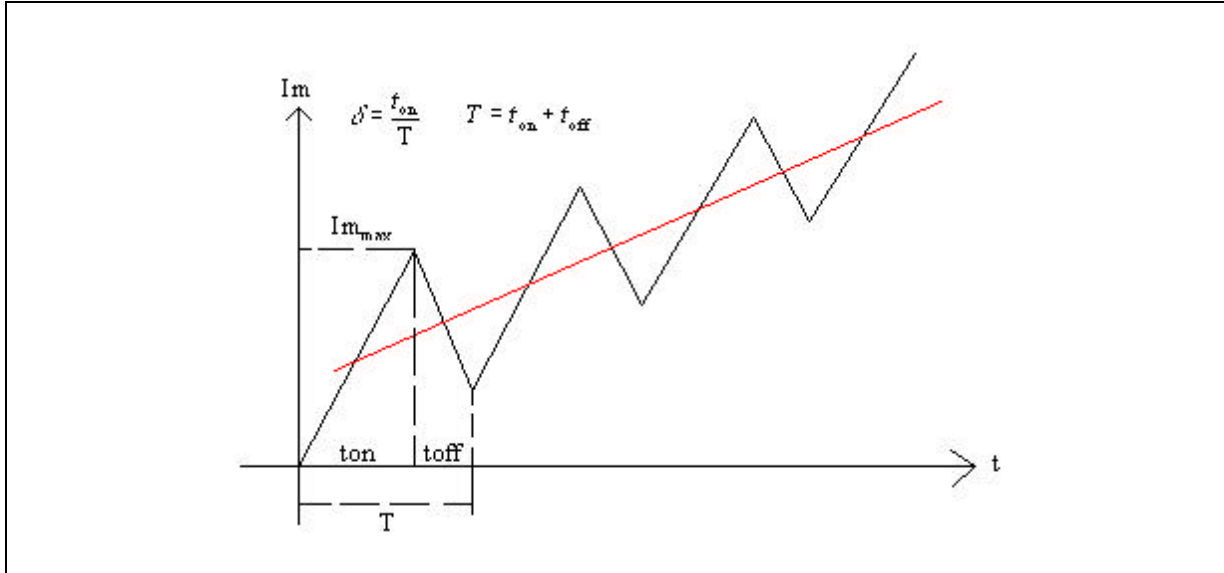

In fact, the B-H characteristic, where B is the induction vector and H is the magnetic vector, can be represented as in fig. 38.

**Figure 38: Theoretical B-H characteristic**

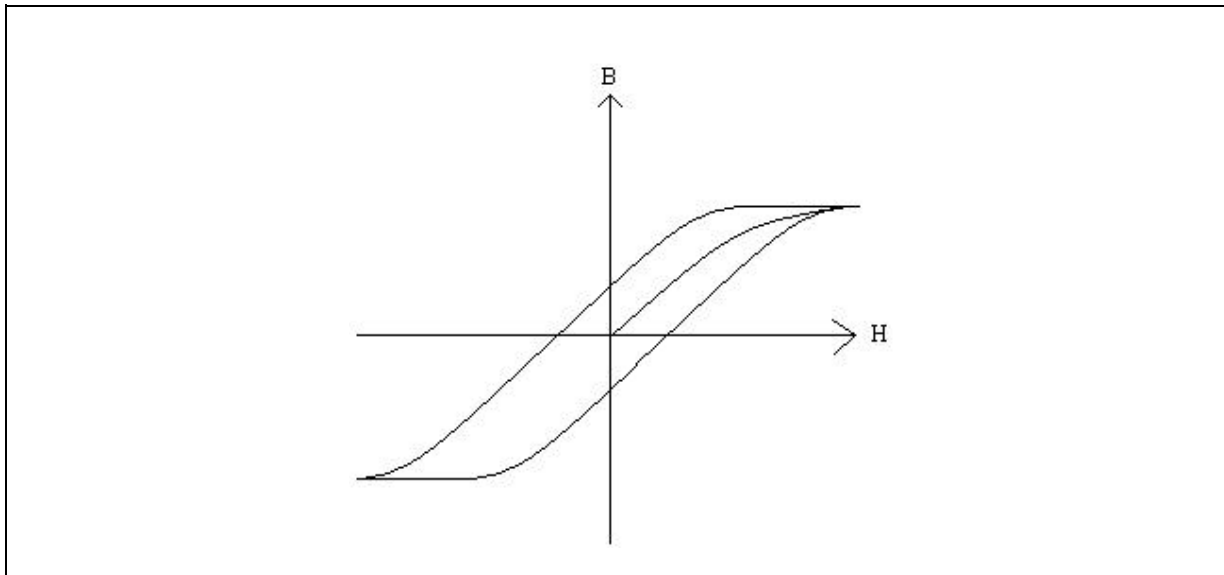

H can be written as:


$$H = \frac{N_1 I}{l} \quad (9.6)$$

When 'I' increases then also H increases, and if H overcomes an established value even if H keeps increasing, B remains constant.

In order to avoid the core saturation, it is necessary to choose a right  $N_3$  and duty cycle. The right limit

case is shown in fig. 39.

**Figure 39: Theoretical Behavior of  $I_m$  Considering the Right Limit Case**

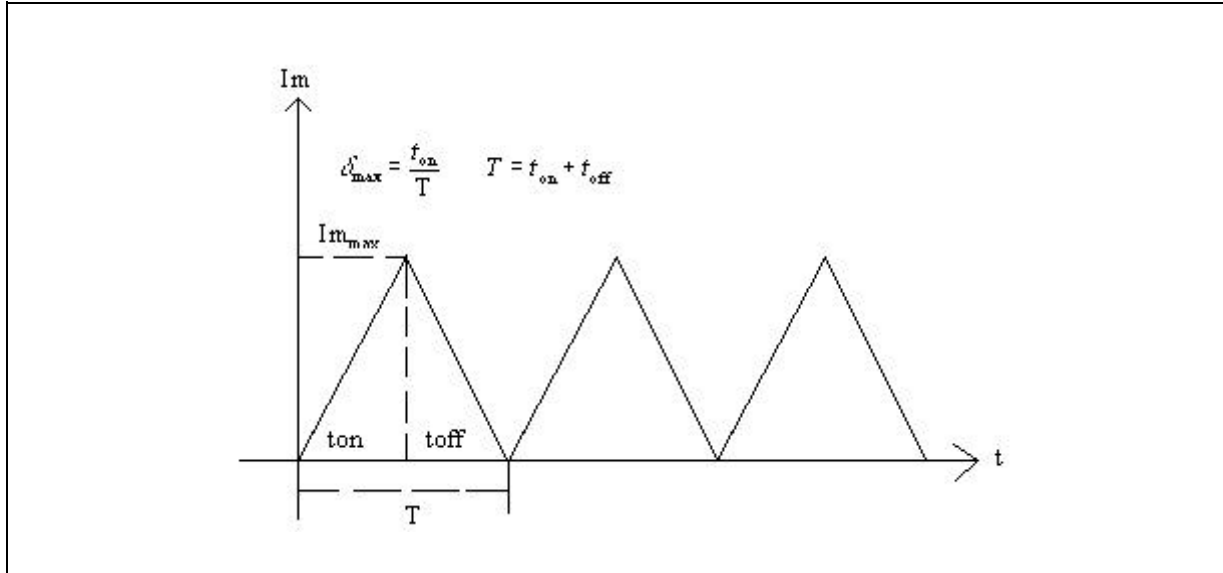

In this condition,  $v_1$  and  $v_3$  can be written as:

$$v_1 = v_3 = V_{dc} = -N_1 \frac{\Delta\Phi}{t_{on}} = -N_3 \frac{\Delta\Phi}{t_{off}} \quad (9.7)$$

$$\frac{N_1}{t_{on}} = \frac{N_3}{t_{off}} \Rightarrow \frac{t_{on}}{N_1} = \frac{t_{off}}{N_3} = \frac{T}{N_3} - \frac{t_{on}}{N_3} \quad (9.8)$$

$$\delta = \frac{t_{on}}{T} = \frac{1}{1 + \frac{N_3}{N_1}} \quad (9.9)$$

Usually,  $N_1$  and  $N_3$  are equal so that the minimum duty cycle that avoids the saturation of the core is:


$$\delta = \frac{1}{2} \quad (9.10)$$

The Emergency Lamp applications using the FORWARD topology work in resonance mode and their duty cycle is, obviously, 0.5.

## 10. EXAMPLE OF AN EMERGENCY LAMP APPLICATION WITH FORWARD TOPOLOGY

The following example analyzes a real emergency lamp application with FORWARD voltage FED converter topology using 8W lamp and powered with 3.6  $V_{dc}$  and using also STSA851 (when the application is powered with the battery the output power on the lamp is around 30% of the nominal power lamp). In the graph below the steady state of  $Q_1$ , after the lamp strike, is showed.

Figure 40: Steady State of STSA851

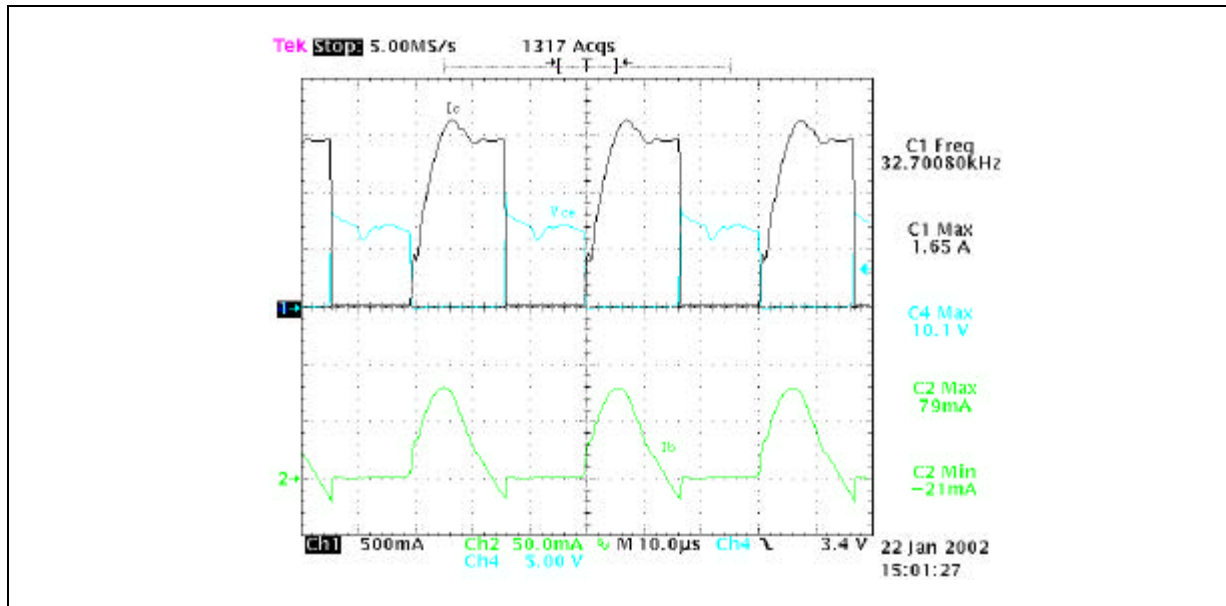

The following graphs show the turn-off and the turn-on switch modes respectively.

Figure 41: Turn-off of STSA851



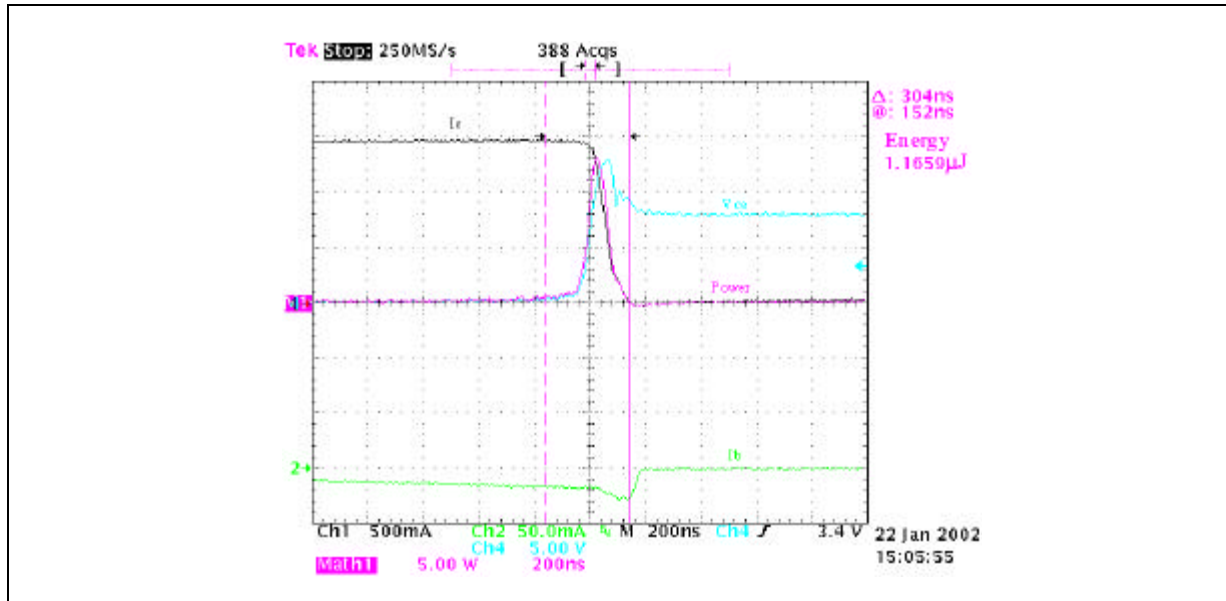


Figure 42: Turn-on of STSA8511

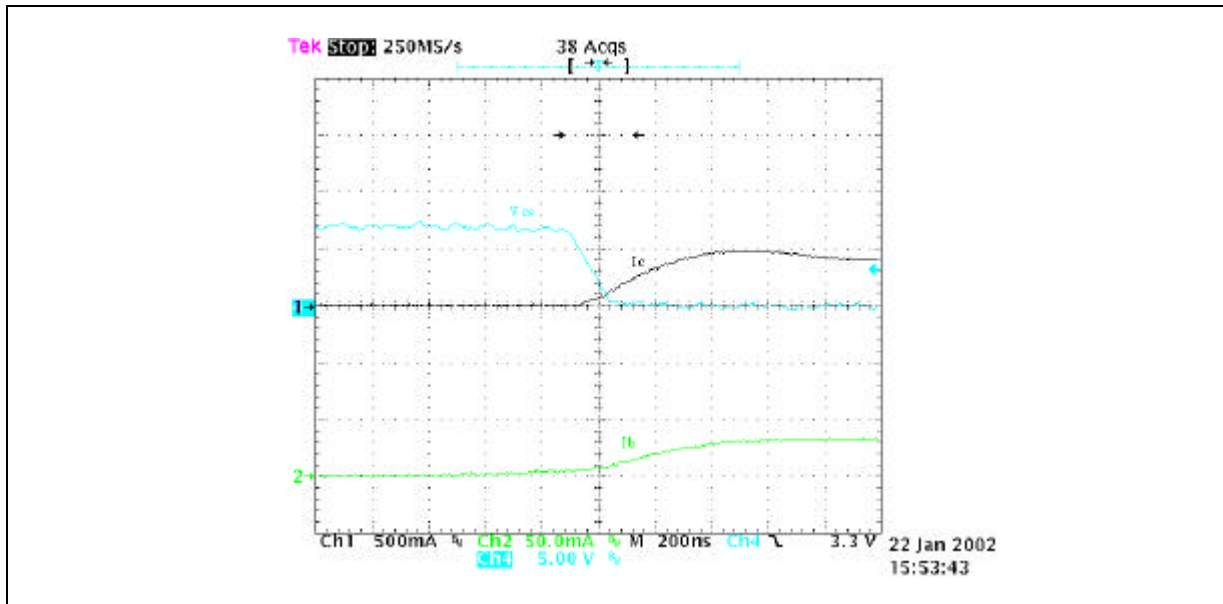

The graph below shows the waveforms of  $V_{tr2a}$ ,  $V_{tr2b}$  and  $V_{tr2c}$  after the lamp strike.


Figure 43: Voltages on  $V_{tr2a}$ ,  $V_{tr2b}$  and  $V_{tr2c}$  Windings1

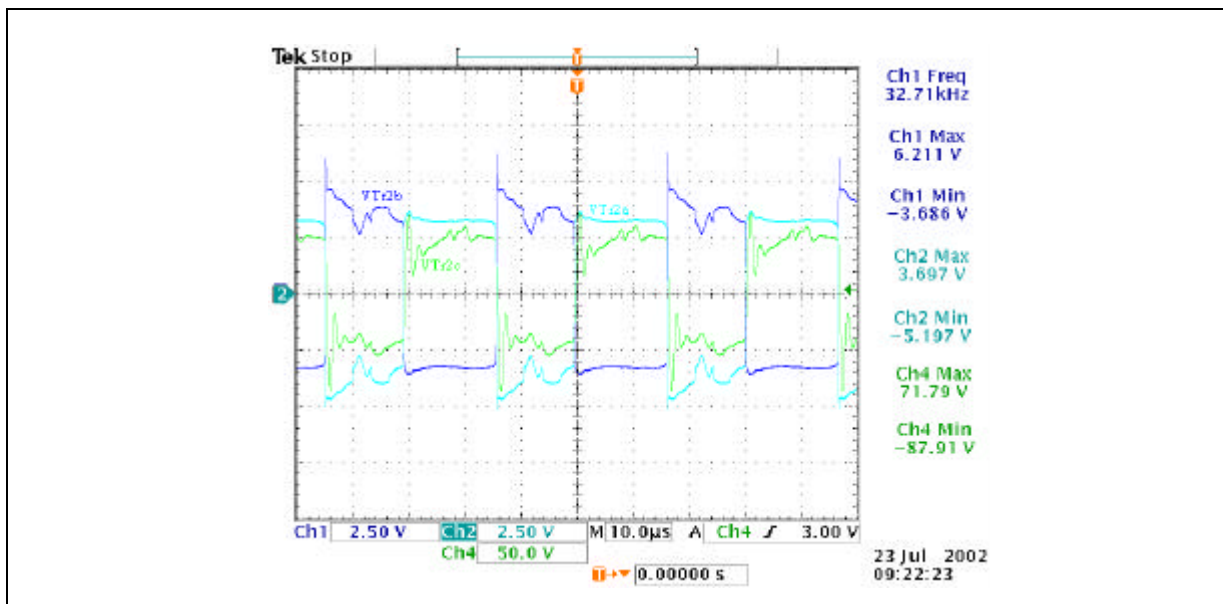




During  $Q_1$  on state, the voltage on  $V_{tr2a}$  is imposed by the battery ( $V_{dc}=3.6$  V) so that no noise is observed, instead, during  $Q_1$  off state noise is highlighted on  $V_{tr2a}$  and  $V_{tr2b}$ . The next graph shows the waveforms of the electrical parameters considering the output impedance after the lamp strike.

Figure 44:  $V_{tr2c}$ ,  $V_{c2}$ ,  $V_{L2}$  and  $i_2$  Waveforms1

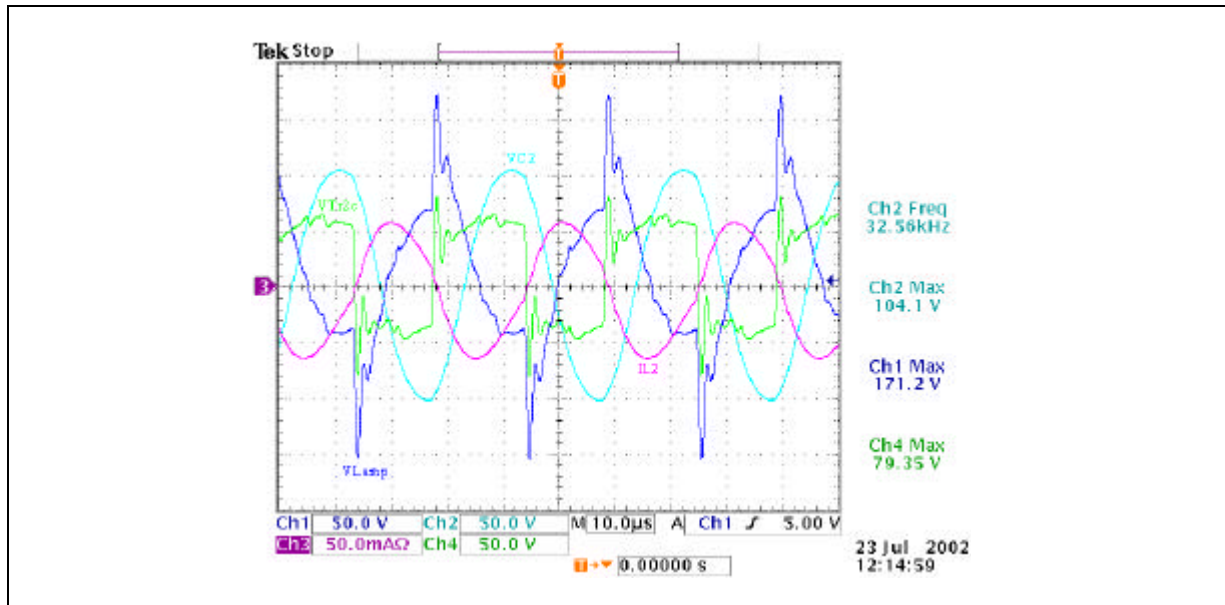

The graph below shows the lamp current and the current  $I_b$  waveforms.

Figure 45:  $i_2$  and  $I_b$  Waveforms

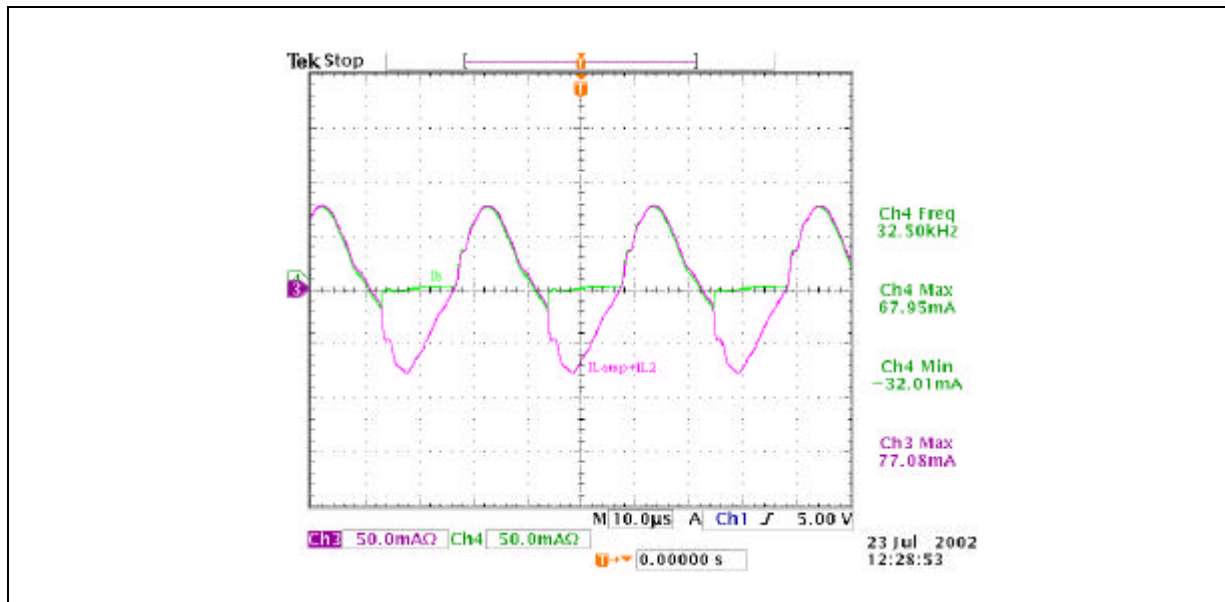

The graphs below show the steady state of  $Q_1$  and the electrical parameters waveforms of the output stage before the lamp strike.

Figure 46: Steady State of STSA851 Before the Lamp Strike


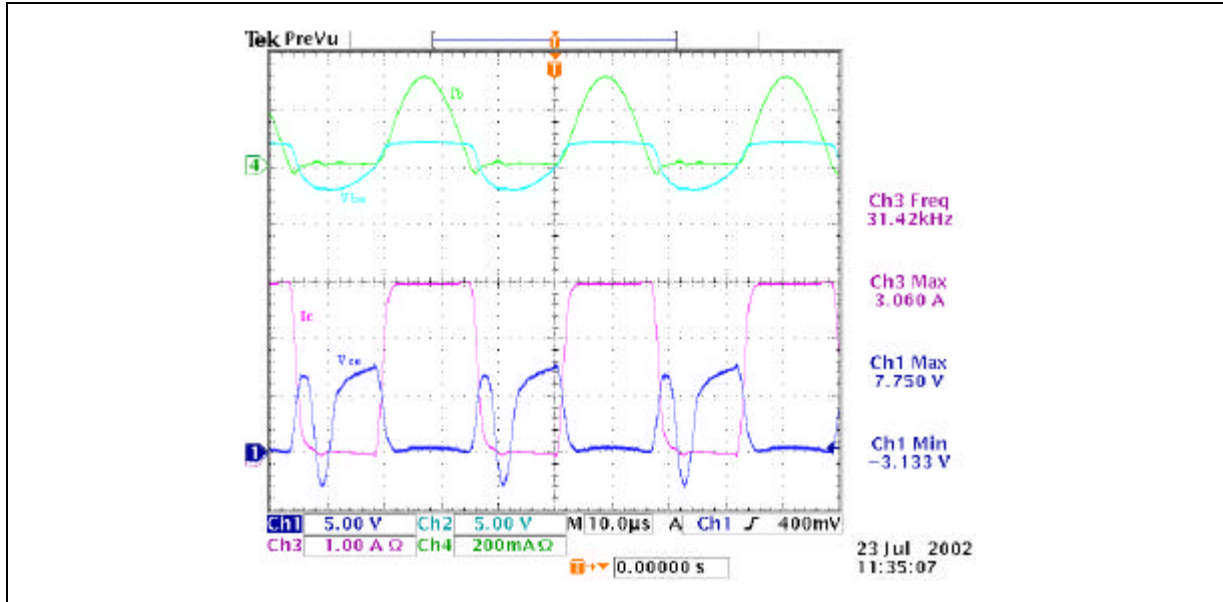


Figure 47:  $I_2$ ,  $V_{tr2c}$ ,  $V_{tr2a}$  and  $V_{Lamp}$  Waveforms Before the Lamp Strike

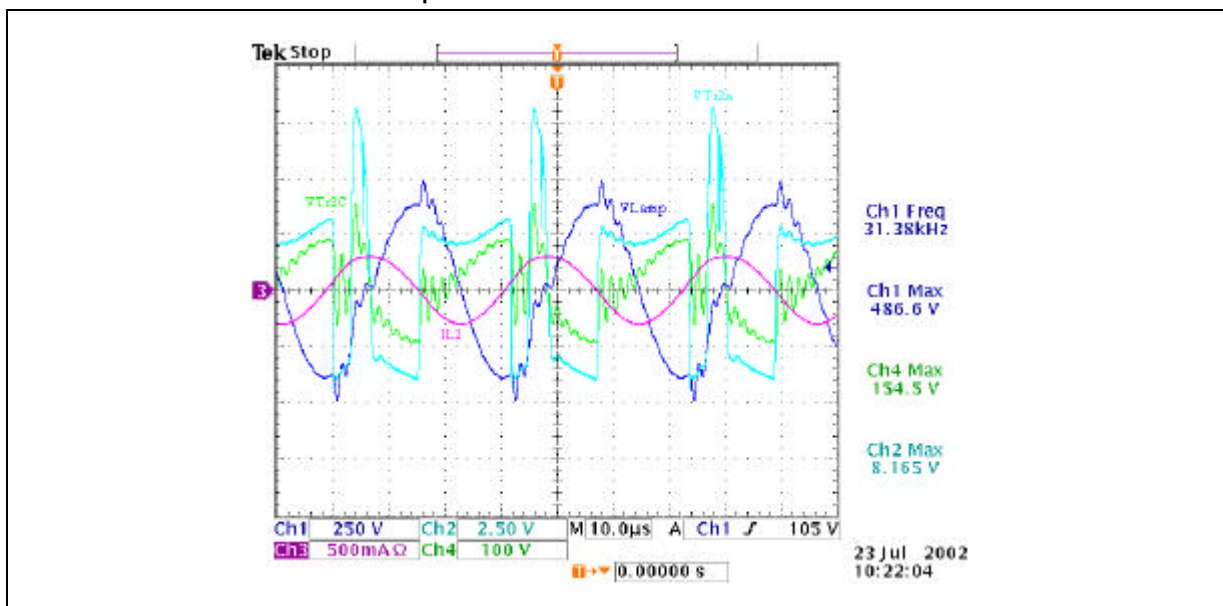

## 11. CONCLUSIONS

Today the Emergency Lighting applications are used in all public places and private homes due to new safety rules. Such applications use fluorescent tubes and are powered with 3.6 Vdc or 6 Vdc input voltages. Usually, the output power can be 8W or 24W but, sometimes, the Emergency Lamp applications can be used also to drive 58W fluorescent tubes. In this last case, however, the applications supply only around 10-15% to the nominal lamp power. The main topologies used are PUSH-PULL current FED and FORWARD. In the first solution, the frequency before the lamp strike is about 60 KHz, while after the lamp strike is about 30 KHz, the current  $I_c$  is about 2.5A,  $I_{on}$  around 80mA and  $V_{cemax}$  around 15V considering an input voltage of 6Vdc. Using the second topology solution and a 3,6Vdc input voltage, the current  $I_c$  is about 1,7A,  $V_{cemax}$  10V,  $I_{on}$  around 70mA and the operation frequency, before and after the lamp strike, is around 30 Khz. However, considering both topology solutions, the power bipolar device STSA851 can be used because the voltages and currents values are inside the SOA area.

Information furnished is believed to be accurate and reliable. However, STMicroelectronics assumes no responsibility for the consequences of use of such information nor for any infringement of patents or other rights of third parties which may result from its use. No license is granted by implication or otherwise under any patent or patent rights of STMicroelectronics. Specifications mentioned in this publication are subject to change without notice. This publication supersedes and replaces all information previously supplied. STMicroelectronics products are not authorized for use as critical components in life support devices or systems without express written approval of STMicroelectronics.

The ST logo is a registered trademark of STMicroelectronics.  
All other names are the property of their respective owners

© 2004 STMicroelectronics - Printed in Italy - All rights reserved

STMicroelectronics GROUP OF COMPANIES

Australia - Belgium - Brazil - Canada - China - Czech Republic - Finland - France - Germany - Hong Kong - India - Israel - Italy - Japan - Malaysia - Malta - Morocco - Singapore - Spain - Sweden - Switzerland - United Kingdom - United States

<http://www.st.com>

