

**High-Performance Analog Products**

# **Analog Applications Journal**

**First Quarter, 2011**



© Copyright 2011 Texas Instruments

**[www.BDTIC.com/TI](http://www.BDTIC.com/TI)**

## IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

### Products

Audio	<a href="http://www.ti.com/audio">www.ti.com/audio</a>
Amplifiers	<a href="http://amplifier.ti.com">amplifier.ti.com</a>
Data Converters	<a href="http://dataconverter.ti.com">dataconverter.ti.com</a>
DLP® Products	<a href="http://www.dlp.com">www.dlp.com</a>
DSP	<a href="http://dsp.ti.com">dsp.ti.com</a>
Clocks and Timers	<a href="http://www.ti.com/clocks">www.ti.com/clocks</a>
Interface	<a href="http://interface.ti.com">interface.ti.com</a>
Logic	<a href="http://logic.ti.com">logic.ti.com</a>
Power Management	<a href="http://power.ti.com">power.ti.com</a>
Microcontrollers	<a href="http://microcontroller.ti.com">microcontroller.ti.com</a>
RFID	<a href="http://www.ti-rfid.com">www.ti-rfid.com</a>
RF/IF and ZigBee® Solutions	<a href="http://www.ti.com/lprf">www.ti.com/lprf</a>

### Applications

Communications and Telecom	<a href="http://www.ti.com/communications">www.ti.com/communications</a>
Computers and Peripherals	<a href="http://www.ti.com/computers">www.ti.com/computers</a>
Consumer Electronics	<a href="http://www.ti.com/consumer-apps">www.ti.com/consumer-apps</a>
Energy and Lighting	<a href="http://www.ti.com/energy">www.ti.com/energy</a>
Industrial	<a href="http://www.ti.com/industrial">www.ti.com/industrial</a>
Medical	<a href="http://www.ti.com/medical">www.ti.com/medical</a>
Security	<a href="http://www.ti.com/security">www.ti.com/security</a>
Space, Avionics and Defense	<a href="http://www.ti.com/space-avionics-defense">www.ti.com/space-avionics-defense</a>
Transportation and Automotive	<a href="http://www.ti.com/automotive">www.ti.com/automotive</a>
Video and Imaging	<a href="http://www.ti.com/video">www.ti.com/video</a>
Wireless	<a href="http://www.ti.com/wireless-apps">www.ti.com/wireless-apps</a>

**TI E2E™ Community Home Page**

**[e2e.ti.com](http://e2e.ti.com)**

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265

Copyright © 2011, Texas Instruments Incorporated

# Contents

**Introduction** ..... 4

**Data Acquisition**

**The IBIS model, Part 2: Determining the total quality of an IBIS model** ..... 5

TI is developing a new arsenal of digital input/output buffer information specification (IBIS) simulation models to meet a variety of customer needs. This article, the second of a three-part series, investigates IBIS-model validation. Since it is important to know the quality of an IBIS model, this article covers the four stages of the IBIS Open Forum's QC process that help insure that the IBIS model provides reliable simulations with signal integrity.

**Power Management**

**An introduction to the Wireless Power Consortium standard and TI's compliant solutions** ..... 10

Inductive coupling is the method by which efficient and versatile wireless power can be achieved. This article provides an overview of the Wireless Power Consortium (WPC) standard and the design considerations for the power transmitted, the power received, and the communications protocol. Also included is an introduction to TI's WPC-compliant solutions in the form of three newly developed ICs.

**Fine-tuning TI's Impedance Track™ battery fuel gauge with LiFePO<sub>4</sub> cells in shallow-discharge applications** ..... 13

Impedance Track technology has been established as an accurate tool for determining a battery pack's state of charge (SOC). In applications where full discharge of the battery with a long rest period is not possible, it is necessary to explore a shallow-discharge option to determine the SOC. As demonstrated in this article, new battery chemistries like LiFePO<sub>4</sub> require the Impedance Track algorithm to be customized to achieve accurate SOC measurements when shallow-discharge cycles are necessary. Included are calculations and examples for adjusting the algorithm parameters for a specific battery pack.

**Interface (Data Transmission)**

**Designing an isolated I<sup>2</sup>C Bus® interface by using digital isolators** ..... 17

Applications with an I<sup>2</sup>C Bus interface often include machinery and equipment that require isolation. This article addresses the challenge of designing an isolated I<sup>2</sup>C interface with standard digital isolators. Included is an overview of I<sup>2</sup>C Bus operation, followed by an analysis of how the bidirectional digital isolators can affect propagation delays.

**Index of Articles** ..... 21

**TI Worldwide Technical Support** ..... 26

To view past issues of the  
**Analog Applications Journal, visit the Web site**  
[www.ti.com/aaj](http://www.ti.com/aaj)

# Introduction

*Analog Applications Journal* is a collection of analog application articles designed to give readers a basic understanding of TI products and to provide simple but practical examples for typical applications. Written not only for design engineers but also for engineering managers, technicians, system designers and marketing and sales personnel, the book emphasizes general application concepts over lengthy mathematical analyses.

These applications are not intended as “how-to” instructions for specific circuits but as examples of how devices could be used to solve specific design requirements. Readers will find tutorial information as well as practical engineering solutions on components from the following categories:

- Data Acquisition
- Power Management
- Interface (Data Transmission)
- Amplifiers: Op Amps

Where applicable, readers will also find software routines and program structures. Finally, *Analog Applications Journal* includes helpful hints and rules of thumb to guide readers in preparing for their design.

# The IBIS model, Part 2: Determining the total quality of an IBIS model

By **Bonnie C. Baker**

*Senior Applications Engineer*

This article is Part 2 of a three-part series. Part 1 (see Reference 1) discussed the fundamental elements of digital input/output buffer information specification (IBIS) simulation models and how they are generated in the SPICE environment. This article, Part 2, investigates IBIS-model validation. Part 3, which will appear in a future issue of the *Analog Applications Journal*, will show how IBIS users investigate signal-integrity issues and problems during the development phase of a printed circuit board (PCB).

IBIS models can be generated from the SPICE deck of an integrated circuit (IC) or in the lab. In both cases, the modeling engineer collects DC data to generate the power-clamp, ground-clamp, pull-up, and/or pull-down data for the various digital buffers on the chip. Following this, data is collected on the output buffer's transient or on the AC rise and fall times. See Reference 1 for more information on these data-collection processes. The IBIS model's transient data replicates the time behavior of output buffers. The modeling engineer acquires the model data with an array of power-supply conditions and junction temperatures. Further enhancements include the addition of the IC's package characteristics, buffer-input chip capacitance, and surrounding documentation. Once the IBIS model exists, the engineer reviews it to verify several quality stages and then produces a validation report that correlates the IBIS model to SPICE simulations or bench data.

Historically, IBIS models have had a reputation of poor quality because many IBIS users have received incorrect models from vendors. The errors range from simple format errors to the model not really portraying the behavior of the buffers in the IC at all. Texas Instruments (TI) is committed to generating quality, reliable IBIS models for customers' signal-integrity investigations.

The IBIS Open Forum's Quality Task Group and Model Review Task Group have formulated a quality-control (QC) process using four QC stages, which are described in the "IBIS Quality Specification," Version 2.0 (Reference 2).

The IBIS task groups are subcommittees of TechAmerica's Systems, Standards & Technology Council. Other model users and model makers across the industry have also contributed to this QC process. The four QC stages are:

- Stage 0: An automated quality check using an IBIS parser
- Stage 1: A manual and visual quality check of the model
- Stage 2: Correlation to SPICE or hardware test data
- Stage 3: Correlation to both SPICE and hardware test data

TI performs stages 0, 1, and 2 for its IBIS models, correlating them with SPICE for stage 2. This article will describe the nuances of performing stages 0, 1, and 2 (with SPICE correlation only).

## Stage 0: IBIS parsers

The first stage of QC for an IBIS model begins with an IBIS parser program. This computer program provides an essential first-stage model check, inspecting the IBIS file for the validity of the IBIS model data and for syntax errors. This type of program can create "Error," "Warning," and/or "Note" messages in relation to the IBIS model under test, but creating an IBIS model that is free of these messages is possible.

For instance, the parser program IBISCHK4 looks for illegal text types, verifies model types, insures that all proper variables are available for each model, validates end points of data, and performs other housekeeping checks. An example of the results of running an IBISCHK4 program with an IBIS model is shown in the sidebar below.

The "Error," "Warning," and "Note" messages from the parser check provide an opportunity for the IBIS-model designer to identify errors and easily correct them. Running a parser with an IBIS model is essential at the beginning of the quality check; however, the parser does not provide an exhaustive list of IBIS-model errors and does not necessarily guarantee a good model.


### Example IBISCHK4 results

```
ERROR (line 137) - Invalid Model_type ("InputX")
WARNING (line 154) - Vinl should not be specified for model type (null)
WARNING (line 155) - Vinh should not be specified for model type (null)
ERROR - Model `sdi_3p3`: Ramp Not Defined
```

```
Errors : 2
Warnings: 2
```

```
File Failed
```

**Figure 1. Pull-down I-V test circuit for three-state buffer**

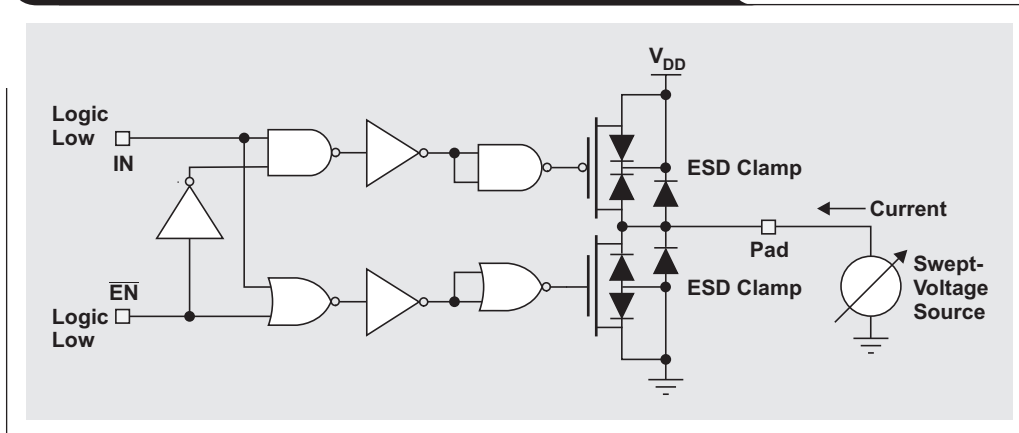

Parser freeware programs are available for dos32, hp\_111, Linux®, and Sun® platforms at the IBIS Open Forum's Web site (<http://www.eda.org/ibis>). To date there are four parsers available: IBISCHK2, IBISCHK3, IBISCHK4, and IBISCHK5. The level number of each parser program corresponds respectively to the version number of the documented IBIS specification. For example, the most recent parser program, IBISCHK5, corresponds to Version 5.0 of the IBIS specification (Reference 3). TI uses IBISCHK4 and IBISCHK5 to validate its IBIS models.


**Stage 1: Visual check**

A visual QC check of an IBIS model consists of a manual review of its text and waveforms. During this visual review, the modeling engineer verifies that the header section of the IBIS model contains accurate information. For instance, the header must have the proper products within the

product families listed and must have appropriate modeling comments and notes. Following the header, the model must have reasonable package parasitics and well-defined selector entries and must map directly to parameters in the product data sheet, including buffer types, load conditions, input-buffer thresholds, and operating or specified temperature range.

Additionally, the DC and transient waveforms must comply with IBIS standards. The measurement voltage span of the DC waveforms ranges from  $-V_{DD}$  to  $+2 \times V_{DD}$  (where  $V_{DD}$  is the power-supply voltage to the buffer). Across this range, the input and output current must not exceed 2 A. Notes in the comments section in the IBIS model header explain the reason for any excessive currents beyond 2 A. Figure 1 shows the pull-down test configuration for an output buffer, and Figure 2 shows a sample of a pull-down curve from an IBIS model.

**Figure 2. Pull-down IBIS graph for DAC7718 output buffer**

 

**Figure 3. Falling-edge V-t test circuit for an output buffer**

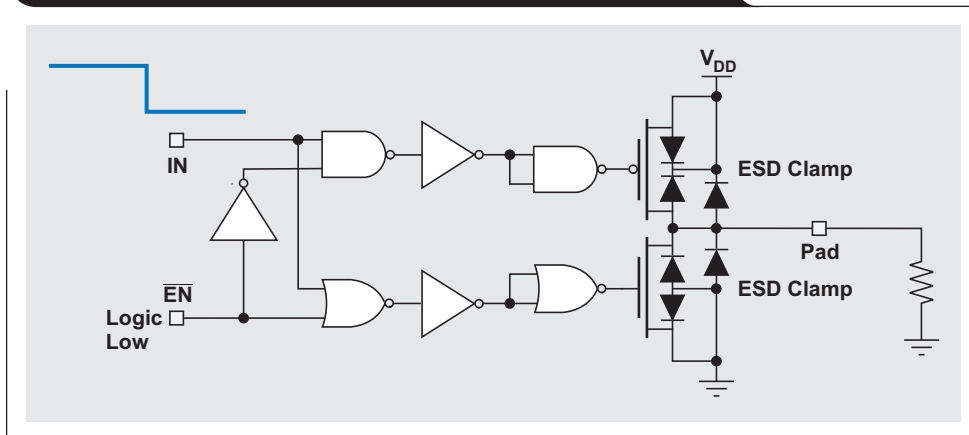


Figure 3 shows the proper test-circuit configuration for the transient falling edge of an output buffer. The resistor following the pad is usually 50 Ω; however, it can be a different value depending on the IC's requirements as stated in the product data sheet.

Figure 4 shows typical falling-edge data for an IBIS model. In this graph, the initial output voltage remains constant for at least two points in time. The data completes its migration to the final value within approximately two-thirds of the total x-axis time.

The text and graphics checks of the IBIS model can be found in Reference 2, where they are described in detail.

### Stage 2: Correlation to SPICE or hardware test data

A primary use for IBIS models is to simulate timing and signal integrity, including over/undershoot or crosstalk behavior on an IC's PCB. For stage 2 QC, the modeling engineer compares the performance of an IBIS model in this environment to the device's IC SPICE simulation or test data. The engineer selects appropriate models for a typical board's transmission lines for the specific product under test and compares the test results graphically and with a figure of merit.

**Figure 4. DAC7718 input-buffer fall-time analysis**


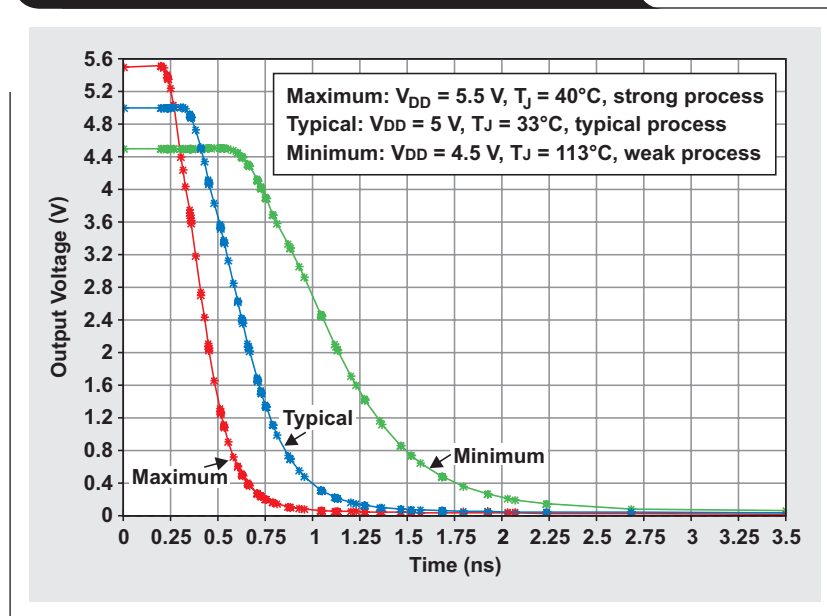


Figure 5 shows an example of a validation test circuit for a SPICE-deck output buffer. This circuit includes the resistive, inductive, and capacitive package parasitics ( $R_{pkg}$ ,  $L_{pkg}$ , and  $C_{pkg}$ , respectively) at the output of the SPICE buffer. Following these parasitics is a model of a PCB transmission line, T1. The SPICE simulation collects data at the far end of the transmission line,  $V_{(SPICE)}$ .


Figure 6 shows an example of an output-buffer IBIS circuit. Notice that the package parasitics do not appear in the circuit, as they are embedded in the IBIS model. This IBIS simulation circuit has the same model of a PCB transmission line (T1) as that in the SPICE-deck simulation circuit.

Figure 7 provides a simulation rise-time comparison between the SPICE and IBIS models based on TI's ADS8319. The outputs were compared at the  $V_{(SPICE)}$  node in Figure 5 and the  $V_{(IBIS)}$  node in Figure 6. Simulated model conditions were based on a nominal or 1.8-V power supply, a junction temperature of 27°C, and a typical process corner.


**Figure 5. Example circuit for SPICE test of an output buffer**

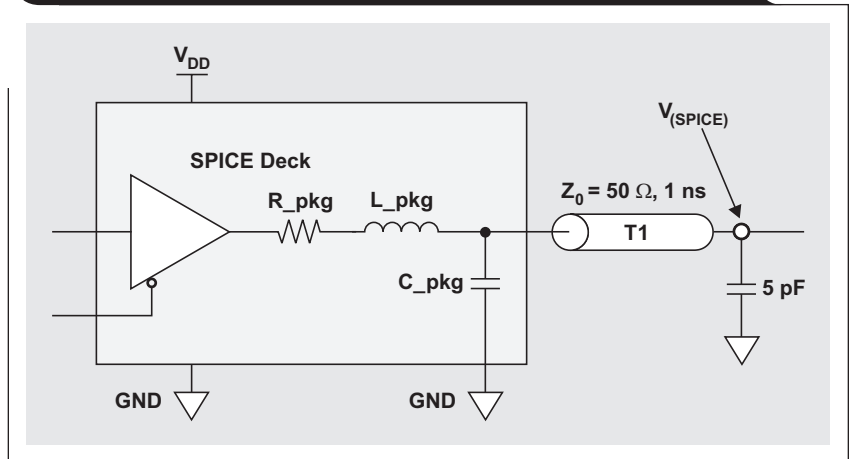

**Figure 6. Example circuit for IBIS-model test of an output buffer**

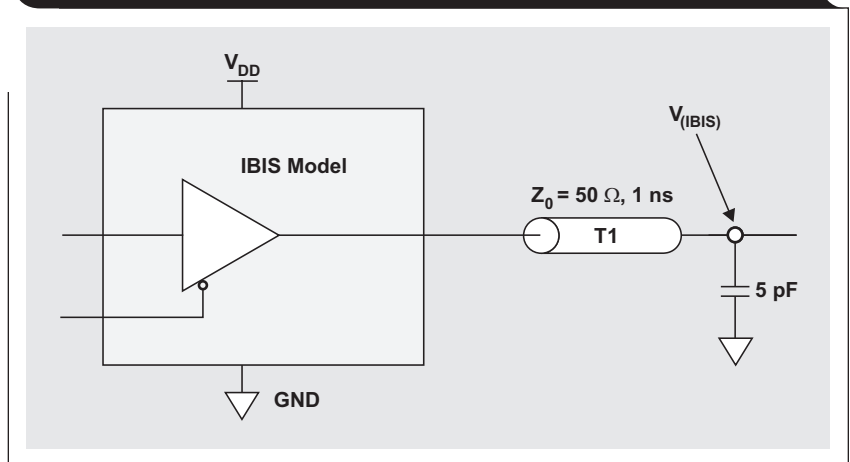

**Figure 7. Comparison of output rise times for SPICE and IBIS models**

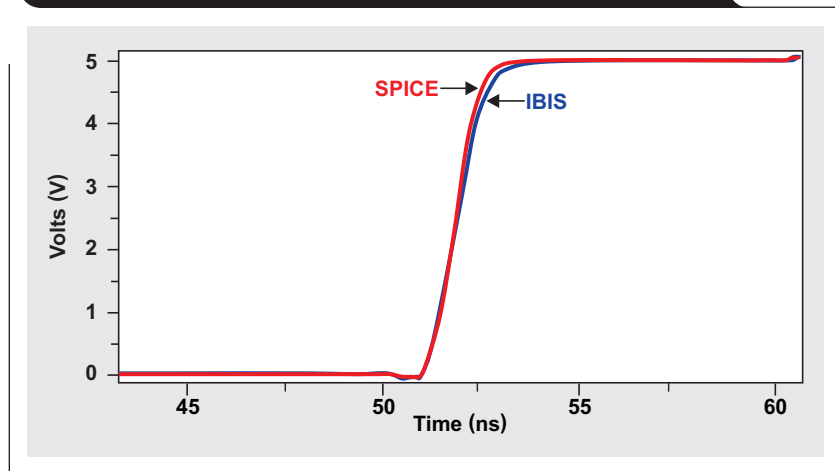



**Figure 8. Comparison of output fall times for SPICE and IBIS models**

 


Figure 8 shows a similar fall-time comparison between the SPICE and IBIS models, also based on the ADS8319. Simulated model conditions were based on a 5-V power supply, a junction temperature of 25°C, and a typical process corner.

It is common to calculate a figure of merit (FOM) when curves like those in Figures 7 and 8 are compared. The FOM calculation is

$$\text{FOM} = 100 \times \left[ 1 - \frac{\sum_{i=1}^N |X_i(\text{golden}) - X_i(\text{DUT})|}{\Delta X \times N} \right],$$

where  $X_i(\text{golden})$  is a time sample of the SPICE-deck curve,  $X_i(\text{DUT})$  is the matching time sample of the IBIS-model curve,  $\Delta X$  is the range of data points, and  $N$  is the number of samples. The FOM formula compares the two waveforms by summing the absolute value of the x-axis differences between two data points. This sum is divided by the range of the data points as well as by the number of data points. A preliminary numerical task must map each set of data points to a common x-y grid by interpolation. The FOM for the curves in Figures 7 and 8 combined is 0.68%.

## Conclusion

In the past, IBIS models have been known to be of poor quality. This lack of quality can be rectified by using the IBIS Open Forum's QC process. At stage 0 in this process, an IBIS parser software finds errors in syntax and in the IBIS model's format. Stage 1 IBIS QC is implemented with a visual inspection of the text and graphics. At stage 2, the IBIS model is mapped back to the product's data sheet. Finally, as the modeling engineer generates IBIS models for SPICE decks, it is important to complete the loop by validating that the IBIS model does match the SPICE-deck performance in a PCB environment. Using stages 0, 1, and

2 to validate the IBIS model insures reliable simulations with signal integrity.

## References

For more information related to this article, you can download an Acrobat® Reader® file at [www.ti.com/lit/litnumber](http://www.ti.com/lit/litnumber) and replace "litnumber" with the **TI Lit. #** for the materials listed below.

Document Title	TI Lit. #
1. Bonnie Baker, "The IBIS model: A conduit into signal-integrity analysis, Part 1," <i>Analog Applications Journal</i> (4Q 2010) . . . . .	slyt390
2. The IBIS Open Forum. (2009, Oct. 30). "IBIS Quality Specification," Version 2.0 [Online]. Available: <a href="http://www.eda.org/ibis/quality_ver2.0">http://www.eda.org/ibis/quality_ver2.0</a>	—
3. The IBIS Open Forum. (2008, Aug. 29). "IBIS (I/O Buffer Information Specification)," Version 5.0 [Online]. Available: <a href="http://www.eda.org/ibis/ver5.0">http://www.eda.org/ibis/ver5.0</a>	—
4. The IBIS Open Forum. (2000, Apr. 20). "I/O Buffer Accuracy Handbook," Rev. 2.0 [Online]. Available: <a href="http://www.eda.org/ibis/accuracy/handbook.pdf">http://www.eda.org/ibis/accuracy/handbook.pdf</a>	—
5. The IBIS Open Forum. (2000, Sept. 11). "I/O Buffer Accuracy Report," Rev. 2.1 [Online]. Available: <a href="http://www.eda.org/ibis/accuracy/report.pdf">http://www.eda.org/ibis/accuracy/report.pdf</a>	—

## Related Web sites

[dataconverter.ti.com](http://dataconverter.ti.com)  
[www.ti.com/sc/device/ADS8319](http://www.ti.com/sc/device/ADS8319)  
[www.ti.com/sc/device/DAC7718](http://www.ti.com/sc/device/DAC7718)  
[www.eda.org/ibis](http://www.eda.org/ibis)

# An introduction to the Wireless Power Consortium standard and TI's compliant solutions

By **Bill Johns**

Senior Applications Engineer

## Introduction

Wireless power is beginning to show great potential in the consumer market. The ability to power an electronic device without the use of wires provides a convenient solution for the users of portable devices and also gives designers the ability to develop more creative answers to problems. This technology's benefits can be seen in the many portable devices, from cell phones to electric cars, that normally operate on battery power.

Inductive coupling is the method by which efficient and versatile wireless power can be achieved. For ease of use and the benefit of both designers and consumers, the Wireless Power Consortium (WPC) has developed a standard (see Reference 1) that creates interoperability between the device providing power (power transmitter, charging station) and the device receiving power (power receiver, portable device). Established in 2008, the WPC is a group of Asian, European, and American companies in diverse industries, including electronics manufacturers and original equipment manufacturers (OEMs). The WPC standard defines the type of inductive coupling (coil configuration) and the communications protocol to be used for low-power wireless devices. Any device operating under this standard will be able to pair with any other WPC-compliant device. One key benefit to this approach is


that it makes use of the coils for communications between the power transmitter and the power receiver. See Figure 1 for a typical application diagram.

## WPC standard for wireless power

Under the WPC standard, "low power" for wireless transfer means a draw of 0 to 5 W. Systems that fall within the scope of this standard are those that use inductive coupling between two planar coils to transfer power from the power transmitter to the power receiver. The distance between the two coils is typically 5 mm. Regulation of the output voltage is provided by a global digital control loop where the power receiver communicates with the power transmitter and requests more or less power. Communication is unidirectional from the power receiver to the power transmitter via backscatter modulation. In backscatter modulation, the power-receiver coil is loaded, changing the current draw at the power transmitter. These current changes are monitored and demodulated into the information required for the two devices to work together.

The WPC standard defines the three key areas of the system—the power transmitter that will supply power, the power receiver that will use the power, and the communications protocol between the two devices. These three areas are explored next.

**Figure 1. Typical wireless-power functional diagram**

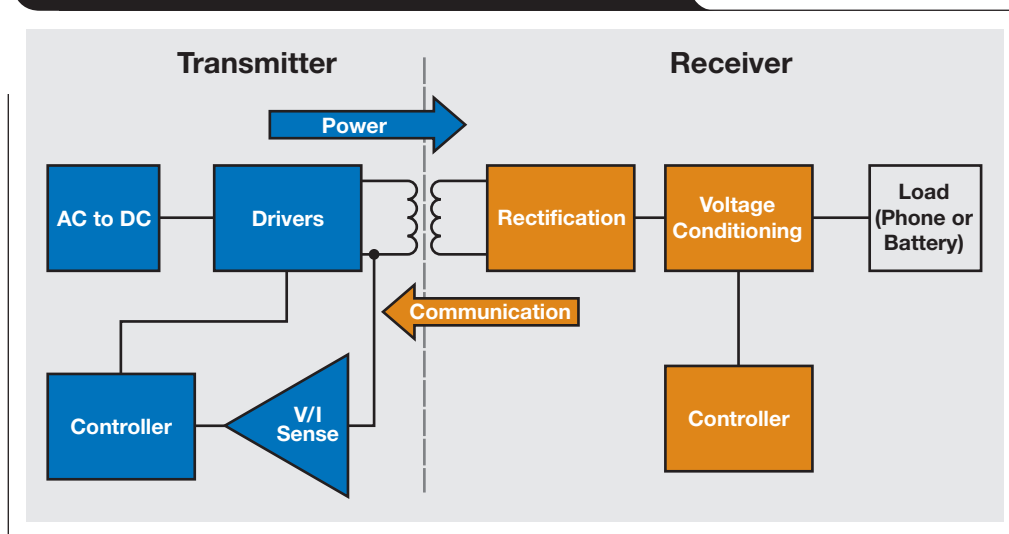

### Power transmitter

The direction of power transfer is always from the power transmitter to the power receiver. The key circuits of the power transmitter are the primary coil, used to transfer power to the power-receiver coil; the control unit for driving the primary coil; and the communications circuit for demodulating the voltage or current from the primary coil. Flexibility of the power-transmitter design is limited to provide consistent power and voltage levels to the power receiver.

The power receiver identifies itself to the power transmitter as a compliant device and also provides configuration information. Once the transmitter initiates power transfer, the power receiver sends error packets to the power transmitter requesting more or less power. The power transmitter stops supplying power upon receiving an “End Power” message, or if no packets are received for more than 1.25 seconds. While no power is being transmitted, the power transmitter enters a low-power standby mode.

The WPC specification allows for both fixed- and moving-coil configurations. A single fixed coil, referred to as type A1, is the solution that Texas Instruments (TI) supports.

The power transmitter, typically a flat surface upon which the user places the power receiver, is connected to the power source. The coils of a WPC-compliant device operate as a resonant half bridge on a 50% duty cycle, with a 19-VDC input ( $\pm 1$  V). If more or less power is needed at the power receiver, the frequency in the coil changes but stays between 110 and 205 kHz, depending on power demands.

### Power receiver

The power receiver is typically a portable device. The key circuits of the power receiver are the secondary coil, used to receive power from the power-transmitter coil; the rectification circuit, used to convert AC to DC; the power-conditioning circuit, which buffers the unregulated DC into regulated DC; and the communications circuit, which modulates the signal to the secondary coil. The power receiver is responsible for all communications of its authentication and power requirements, as the power transmitter is only a “listener.”

While design of the power transmitter is restricted to keep it WPC-compliant, much more freedom is permitted for designing the power receiver. The coil dimension of the power receiver can be adjusted to meet the device’s form factor. The coil voltage at the power receiver is full-wave rectified, with a typical efficiency of 70% for a 5-V, 500-mA output. Because communication between the two devices is unidirectional, the WPC selected the power receiver to be the “talker.” Inductive power transfer works by coupling a magnetic field from primary to secondary coils. Uncoupled field lines rotate around the primary coil and do not represent loss as long as the field lines don’t couple a parasitic load (for example, eddy-current loss in metal).

### Communications protocol

The communications protocol includes analog and digital pinging; identification and configuration; and power transfer. A typical start-up sequence that occurs when a power receiver is placed on a power transmitter proceeds as follows:

1. An analog ping from the power transmitter detects the presence of an object.
2. A digital ping from the power transmitter is a longer version of the analog ping and gives the power receiver time to reply with a signal-strength packet. If the signal-strength packet is valid, the power transmitter keeps power on the coil and proceeds to the next phase.
3. During the identification and configuration phase, the power receiver sends packets that identify it and that provide configuration and setup information to the power transmitter.
4. In the power-transfer phase, the power receiver sends control error packets to the power transmitter to increase or decrease the power supply. These packets are sent approximately every 250 ms during normal operation or every 32 ms during large signal changes. Also during normal operation, the power transmitter sends power packets every 5 seconds.
5. To end the power transfer, the power receiver sends an “End Power” message or sends no communications for 1.25 seconds. Either of these events places the power transmitter in a low-power state.

### TI’s WPC-compliant solutions

TI is a founding member of the WPC and has taken an active role in developing a robust wireless-power specification. TI has developed reliable solutions for both a power receiver and a power transmitter in the form of three newly developed ICs. The power receiver uses the MSP430bq1010 and bq25046 devices. The power transmitter is based on the bq500110, which supports type A1 (single-coil) configurations. Both receiver and transmitter ICs are designed to be interoperable with other WPC-compliant solutions.

The MSP430bq1010 in the power receiver handles all of the logic functions and communications. The onboard analog-to-digital converters monitor the levels of voltage into and current out of the bq25046. The bq25046 provides load-current information to the MSP430bq1010, which then uses this information to control the power transmitter’s operating point. The bq25046 provides a low-current, 3.3-V low-dropout regulator (LDO) to power the MSP430bq1010 and logic circuit, while a larger 5.0-V LDO is capable of providing up to 1 A of current to the main output.

The power-transmitter solution is provided with the bq500110. This device demodulates and decodes serial data from the power receiver. The control circuits first

certify that the power receiver is indeed a WPC-compliant device, then configure the power transmitter accordingly.

TI's BQTESLA100LP EVM kit combines separate transmitter and receiver designs into a single kit that includes mechanical packaging. This kit can be used for evaluation of the ICs or as a design example. The WPC has certified that both the power-transmitter and the power-receiver solutions meet the Version 1.0 specification. No software is required to operate the EVM, which needs only a 19-V input. The EVM kit's output will be 5 V at up to 1 A. The transmitter EVM includes multiple LED options for visual indication of power-transmission status. Also, two buzzer options provide audio indication of the start of power transfer.

**Conclusion**

The WPC standard is a set of guidelines that allows manufacturers to develop solutions with the confidence that their components will mesh with a variety of other WPC-certified components designed for inductive power transfer.

**References**

For more information related to this article, you can download an Acrobat® Reader® file at [www.ti.com/lit/litnumber](http://www.ti.com/lit/litnumber) and replace "litnumber" with the **TI Lit. #** for the materials listed below.

<b>Document Title</b>	<b>TI Lit. #</b>
1. Wireless Power Consortium. "System Description Wireless Power Transfer, Vol. 1, Part 1," Version 1.0 [Online]. Available: <a href="http://www.wirelesspowerconsortium.com/downloads/wireless-power-specification-part-1.html">http://www.wirelesspowerconsortium.com/downloads/wireless-power-specification-part-1.html</a>	—

<b>Document Title</b>	<b>TI Lit. #</b>
2. "Wireless Power Transmitter Manager," bq500110 Data Sheet. . . . .	slusae0
3. "1.1A, Single-Input 5-V Power Supply IC for Wireless Power Applications," bq25046 Data Sheet . . . . .	slusa83
4. "Wireless Receiver-Side Communication and Power Monitoring IC for Wireless Power," MSP430bq1010 Data Sheet. . . . .	slas696
5. "bq500110EVM-688 Evaluation Module," User's Guide . . . . .	slvu429a
6. "bq25046EVM-687 Evaluation Module," User's Guide . . . . .	slvu420

**Related Web sites**

[www.ti.com/wirelesspower](http://www.ti.com/wirelesspower)  
[www.ti.com/sc/device/partnumber](http://www.ti.com/sc/device/partnumber)  
 Replace *partnumber* with bq25046, bq500110, or MSP430bq1010

# Fine-tuning TI's Impedance Track™ battery fuel gauge with LiFePO<sub>4</sub> cells in shallow-discharge applications

By Keith James Keller

Analog Field Applications

The Impedance Track™ battery-fuel-gauging technology from Texas Instruments (TI) is a powerful adaptive algorithm that learns how a battery's characteristics change over time. Combining this algorithm with knowledge of the battery pack's specific chemistry permits a very accurate determination of the battery's state of charge (SOC) for the life of the pack.


However, certain conditions are required for updating information about the total chemical capacity ( $Q_{\max}$ ) of the cell. This becomes more difficult with the extremely flat voltage profile of lithium-iron-phosphate (LiFePO<sub>4</sub>) cells (see Figure 1), especially if it is not possible to fully discharge the battery and let it rest for several hours. Figure 1 shows typical open-circuit voltage (OCV) characteristics versus depth of discharge (DOD) for LiCoO<sub>2</sub> and LiFePO<sub>4</sub> battery chemistries. This article builds on the discussions about Impedance Track technology in References 1 and 2.

TI recommends using the Impedance Track 3 (IT3) algorithm with any LiFePO<sub>4</sub> cell. The IT3's improvements to earlier Impedance Track algorithms include:

- Better cold-temperature performance from improved temperature compensation
- Added filtering to prevent capacity jumps in SOC
- Improved accuracy for unfavorable OCV readings with LiFePO<sub>4</sub> cells
- Conservative remaining-capacity estimation with additional load-selection configurations

IT3 is included in TI's bq20z4x, bq20z6x, and bq27541-V200 gas gauges (not a comprehensive list).

Figure 1. Battery OCV measurements based on DOD

 

## Typical conditions for $Q_{\max}$ update

The Impedance Track algorithm defines  $Q_{\max}$  as the total chemical capacity of a cell, measured in milliampere-hours (mAh). For a proper  $Q_{\max}$  update, two conditions must be met:

1. Two OCV measurements must be taken outside of the disqualified voltage range, which is based on the cell's chemical identification (ID) number established by TI. An OCV measurement can be done only on a relaxed cell that has not been charged or discharged for several hours.

Reference 3 lists a subset of the disqualified voltage ranges, some of which are shown in Table 1. It can be seen that, for chemical ID 100, no OCV measurements are allowed if any cell voltages are above 3737 mV or below 3800 mV. This is essentially a “keep out” range for OCV measurements for best accuracy. Even though an SOC percentage is given in this article, the gauge determines disqualification based only on voltage.

2. A minimum amount of passed charge must be integrated by the fuel gauge. By default, it is set at 37% of the total cell capacity. This percentage of passed charge can be decreased to as low as 10% for a shallow-discharge  $Q_{max}$  update. This decrease will be at the expense of SOC accuracy but will be tolerable in a system that would not otherwise be able to update  $Q_{max}$ .

Now that we have an understanding of what is required for a shallow-discharge  $Q_{max}$  update, let’s look at an example of data-flash parameters that need to be changed in a configuration with a lower-capacity pack. The default Impedance Track algorithm is based on typical laptop battery packs having 2 parallel strings of 3 cells in series (3s2p). Each string has a 2200-mAh capacity, giving a total capacity of 4400 mAh. LiFePO<sub>4</sub> cells have approximately half of that capacity, so if they are used in a 3s1p configuration, the total pack capacity will be 1100 mAh. With smaller-capacity packs like this, specific data-flash parameters need to be fine-tuned in TI’s gas-gauge evaluation software for optimal performance. The remainder of this article describes this process.

### Example calculations


Consider a 3s1p-configuration battery pack using A123 Systems™ 1100-mAh 18650 LiFePO<sub>4</sub>/carbon cells. TI’s chemical ID number for this cell type is 404. This battery will be used in a storage system with normal temperatures of around 50°C. The discharge rate is 1C, and a 5-mΩ sense resistor is used with the gauge for coulomb counting.

As can be seen in Table 1, the disqualified voltage range for OCV measurements for chemical ID 404 is 3274 mV minimum (~34% SOC) and 3351 mV maximum (~93% SOC). Most LiFePO<sub>4</sub> cells have a very wide disqualified voltage range (see chemical ID 409 as a comparison). However, depending on the cell characteristics, it may be

**Table 1. Excerpt from Reference 3 showing disqualified voltage ranges based on chemistry for  $Q_{max}$  update**

Description	Chemical ID	Vqdis_min (mV)	Vqdis_max (mV)	SOC_min, %	SOC_max, %
LiCoO2/graphitized carbon (default)	100	3737	3800	26	54
Mixed Co/Ni/Mn cathode	101	3749	3796	28	51
Mixed Co/Mn cathode	102	3672	3696	6	14
LiCoO2/carbon 2	103	3737	3800	26	54
Mixed Co/Mn cathode 2	104	4031	4062	77	88
<b>LiFePO4/carbon</b>	<b>404</b>	<b>3274</b>	<b>3351</b>	<b>34</b>	<b>93</b>
LiFePO4/carbon	409	3193	3329	12	92

**Figure 2. SOC correlation error for 1-mV voltage error**

 

possible to identify a higher minimum disqualified voltage for a shallow-discharge  $Q_{max}$  update. For chemical ID 404 it is possible to raise this value to 3322 mV, allowing for a shallow  $Q_{max}$ -update window from 3309 to 3322 mV (see Figure 2). The designer can use this midrange low-error window with data-flash modifications. Since only a high and low disqualified voltage range can be programmed, the host system must guarantee that the lower OCV measurement will not happen below 3309 mV. (As the correlation error increases, OCV-measurement error increases dramatically between 3274 and 3309 mV.) Even though there is only a 13-mV window to work with for the lower OCV measurement (3322 – 3309 mV = 13 mV), it corresponds to an SOC range of 70% to 64%.

LiFePO<sub>4</sub> cells have a very long relaxation time, so let’s increase the data-flash parameter “OCV Wait Time” to 18,000 seconds (5 hours). Since the battery’s normal

operating temperature is elevated, the parameter “Q Invalid Max Temperature” should be changed to 55°C. Additionally, “Q<sub>max</sub> Max Time” should be changed to 21,600 seconds (6 hours).

To decrease the Q<sub>max</sub> passed charge from 37% to 10%, the “DOD Max Capacity Error,” “Max Capacity Error,” and “Q<sub>max</sub> Filter” need to be modified, as they all play a part in the disqualification time between the OCV1 and OCV2 measurements. “Q<sub>max</sub> Filter” is a compensation factor that varies Q<sub>max</sub> relative to passed charge.

The goal of these parameters is to have less than 1% “Max Capacity Error” based on measured passed charge and including ADC maximum offset error (“CC Deadband”). However, these values need to be changed to allow for the shallow-discharge Q<sub>max</sub> update.

#### Example 1: Time-out period for Q<sub>max</sub> update

To have less than 1% of accumulated error across a 10-mΩ sense resistor with a 1000-mAh cell and “CC Deadband” set by the hardware to a fixed value of 10 μV, the time-out period for the Q<sub>max</sub> update can be determined as follows:

$$10 \mu\text{V}/10 \text{ m}\Omega = 1\text{-mA offset current.}$$

$$1000\text{-mAh capacity} \times 1\% \text{ allowed error} \\ = 10\text{-mAh capacity error.}$$

$$10\text{-mAh capacity error}/1\text{-mA offset current} \\ = 10 \text{ hours.}$$

Therefore, from start to finish, including rest periods, only 10 hours are available to complete a Q<sub>max</sub> update. After the 10-hour time-out, once the gauge takes its next proper OCV reading, this timer will restart.

#### Example 2: Modifying data-flash parameters

In the design scenario using 1100-mAh cells with a 5-mΩ sense resistor, the time-out period for the Q<sub>max</sub> update is determined in the same way:

$$10 \mu\text{V}/5 \text{ m}\Omega = 2\text{-mA offset current.}$$

$$1100 \text{ mAh} \times 1\% = 11 \text{ mAh.}$$

$$11 \text{ mAh}/2\text{-mA offset current} = 5.5 \text{ hours.}$$

In this case, the percentage of capacity error needs to be relaxed to increase the Q<sub>max</sub> time-out. Changing the “Max Capacity Error” to 3% (from the default of 1%) gives

$$1.1 \text{ Ah} \times 3\% = 33 \text{ mAh,}$$

which will increase the Q<sub>max</sub> disqualification time to

$$33 \text{ mAh}/2\text{-mA capacity error} = 16.5 \text{ hours.}$$

The “DOD Capacity Error” needs to be set to twice the “Max Capacity Error,” so let’s change it to 6% (from the default of 2%).

The default value of 96 for “Q<sub>max</sub> Filter” needs to be decreased proportionally, based on the percentage of passed charge:

$$\text{“Q}_{\text{max}} \text{ Filter”} = 96/(37\%/10\%) = 96/3.7 = 26$$

Table 2 shows typical data-flash parameters in gas-gauge evaluation software that must be modified to implement a shallow-discharge Q<sub>max</sub> update. These particular parameters are protected (classified as “hidden”) but can be unlocked by TI’s applications staff. The example battery pack used for this table is the one mentioned earlier,

**Table 2. Protected data-flash parameters that can be changed by TI applications staff based on system usage**

DATA-FLASH PARAMETER	DEFAULT VALUE	NEW VALUE
Min % Passed Charge for Q <sub>max</sub>	37%	10%
Min % Passed Charge for 1st Q <sub>max</sub>	90%	Keep default at 90% <sup>1</sup>
Q Invalid MaxV	3351 mV (chemical ID 404 default)	Keep chemical ID 404 default at 3351 mV
Q Invalid MinV	3274 mV (chemical ID 404 default)	3322 mV
OCV Wait Time	1800 seconds	18,000 seconds
DOD Capacity Err	2%	6%
Q <sub>max</sub> Max Time	18,000 seconds	21,600 seconds
Max Capacity Error	1.0%	3.0%
Q <sub>max</sub> Filter	96	26
Q Invalid MaxT	40.0°C	55.0°C
Q Invalid MinT	10.0°C	Keep default at 10.0°C <sup>2</sup>

<sup>1</sup>This parameter is important during the golden-image process. If a standard 4.2-V Li-ion cell is being used and charged only to 4.1 V in-system, it is still necessary for the first Q<sub>max</sub> update to occur after the cell is charged to 4.2 V to meet the requirement for a 90% change in capacity. The capacity change is checked against both the specified cell capacity, or “Design Capacity,” and the estimated DOD for the start and end points based on the chemical ID number programmed in the gauge.

<sup>2</sup>A wide-ranging temperature change can cause errors when Q<sub>max</sub> is calculated. In a system with normal operation at high or low temperatures, it is necessary to modify this parameter.

a 3s1p pack using A123 1100-mAh 18650 LiFePO<sub>4</sub>/carbon cells with chemical ID 404.

### Events of Q<sub>max</sub> update

The following events describe a practical approach to achieving a Q<sub>max</sub> update after the data-flash parameters described in Examples 1 and 2 have been changed.

1. A Q<sub>max</sub> update should start when the battery voltages are within the low-correlation-error window as shown in Figure 2. The designer's own algorithm can be used to discharge/charge the cells into this range.\*
2. In this example, to be in the valid measurement range (for chemical ID 404), all cell voltages must be greater than or equal to 3309 mV and less than or equal to 3322 mV. If cell voltages happen to relax outside the valid range during the discharge routine, another discharge or charge cycle must be started prior to the programmed "OCV Wait Time" of 18,000 seconds. If all cell voltages are within 3309 to 3322 mV after 6 hours and 10 minutes, a proper OCV measurement has been taken.
3. The next step is to fully charge the battery. Once the battery is full, or at 100% SOC, it should rest for another 6 hours and 10 minutes before the second OCV measurement is taken. The Q<sub>max</sub> value will then be updated. If charging takes approximately 2 hours, then a minimum of 8 hours will be needed for the time-out period. From the calculation of the 16.5-hour time-out period in Example 2, we know there is more than enough time with an additional cushion of 8.5 hours.
4. The OCV timer can always be reset by issuing the gas gauge a ResetCommand (0x41) while the gauge is in unsealed mode.

Table 3 shows the results from cycling the battery as just described when the example pack configuration is used.

### Conclusion

TI's Impedance Track technology is a very accurate algorithm for determining battery SOC over the life of the cell. In LiFePO<sub>4</sub> applications where a full discharge of the battery with a rest period is not possible, it is necessary to explore a shallow-discharge option for the Q<sub>max</sub> update. This article has described the considerations and data-flash

**Table 3. Results from full-cycle and shallow-charge Q<sub>max</sub> updates**

	NORMAL CHARGE CYCLE <sup>1</sup>	SHALLOW CHARGE CYCLE	
	UPDATED Q <sub>max</sub> (mAh)	UPDATED Q <sub>max</sub> (mAh)	RESTING VOLTAGE BEFORE CHARGING (mV)
Cell 0	1062	1062	3312
Cell 1	1066	1038	3310
Cell 2	1064	1063	3311
Pack	1062 (cell minimum)	1038 (cell minimum)	9933 (total)

<sup>1</sup>Charging from empty after rest to full charge with rest.

programming configurations for implementing a shallow-discharge Q<sub>max</sub> update. Changes to these parameters must be approved by TI applications staff based on system configuration and requirements.

### References

For more information related to this article, you can download an Acrobat® Reader® file at [www.ti.com/lit/litnumber](http://www.ti.com/lit/litnumber) and replace "litnumber" with the **TI Lit. #** for the materials listed below.

Document Title	TI Lit. #
1. "Theory and implementation of Impedance Track™ battery fuel-gauging algorithm in bq20zxx product family," Application Report . . . slua364	
2. Keith James Keller, "Fuel-gauging considerations in battery backup storage systems," <i>Analog Applications Journal</i> (1Q 2010) . . . slyt364	
3. chemistry_specific_Qmax_disqv_voltages_table.xls [Online]. Available: <a href="http://www.ti.com/litv/zip/slua372r">http://www.ti.com/litv/zip/slua372r</a>	—

### Related Web sites

[power.ti.com](http://power.ti.com)  
[www.ti.com/sc/device/partnumber](http://www.ti.com/sc/device/partnumber)  
 Replace *partnumber* with BQ20Z40-R1 or BQ27541-V200

\*Because of the long voltage hysteresis of LiFePO<sub>4</sub> cells after charge or discharge, it is preferable to discharge the battery only into the shallow-discharge range. It is okay to charge the battery during the hone-in algorithm as long as the voltage does not rise above the specified "Q Invalid Max Voltage" at any time. It is also permissible to have multiple discharges to get the cells into the range of 3309 to 3322 mV after the OCV wait time.



# Designing an isolated I<sup>2</sup>C Bus<sup>®</sup> interface by using digital isolators

By Thomas Kugelstadt  
Senior Applications Engineer

The continuing changes in legislation concerning both the design and use of machinery and equipment require the isolation of almost any type of industrial system or interface. The inter-integrated circuit bus (I<sup>2</sup>C Bus<sup>®</sup>) is a single-ended, multi-master, two-wire bus; and, while designed only for short-distance I<sup>2</sup>C communication, it is no exception to isolation requirements.

The particular challenge in designing an isolated I<sup>2</sup>C interface by using standard digital isolators lies in the different operation modes between the two. The I<sup>2</sup>C Bus operates in bidirectional, half-duplex mode, while standard digital isolators are unidirectional devices. To make efficient use of one technology supporting the other, external circuitry is required that separates the bidirectional bus into two unidirectional signal paths without introducing significant propagation delay.


This article provides a short introduction to I<sup>2</sup>C Bus operation and then describes how to design an isolated I<sup>2</sup>C interface by adding only a few external components to a digital capacitive isolator.

## I<sup>2</sup>C Bus operation


The I<sup>2</sup>C uses open-drain technology, thus requiring the serial data line (SDA) and serial clock line (SCL) to be connected to V<sub>DD</sub> by resistors (see Figure 1). Pulling the line to ground is considered a logic “0,” and letting the line float is a logic “1.” This logic configuration is used as a channel-access method. Transitions of logic states must occur while SCL is low, because transitions while SCL is high indicate START and STOP conditions. Typical supply voltages are 3.3 V and 5 V, although systems with higher or lower voltages are permitted.

I<sup>2</sup>C communication uses a 7-bit address space with 16 reserved addresses, so a theoretical maximum of 112 nodes can communicate on the same bus. In praxis, however, the number of nodes is limited by the specified total bus capacitance of 400 pF, which restricts communication distances to a few meters. The specified signaling rates are 100 kbps (standard mode), 400 kbps (fast mode), 1 Mbps (fast mode plus), and 3.4 Mbps (high-speed mode).

Figure 1. The I<sup>2</sup>C Bus<sup>®</sup>

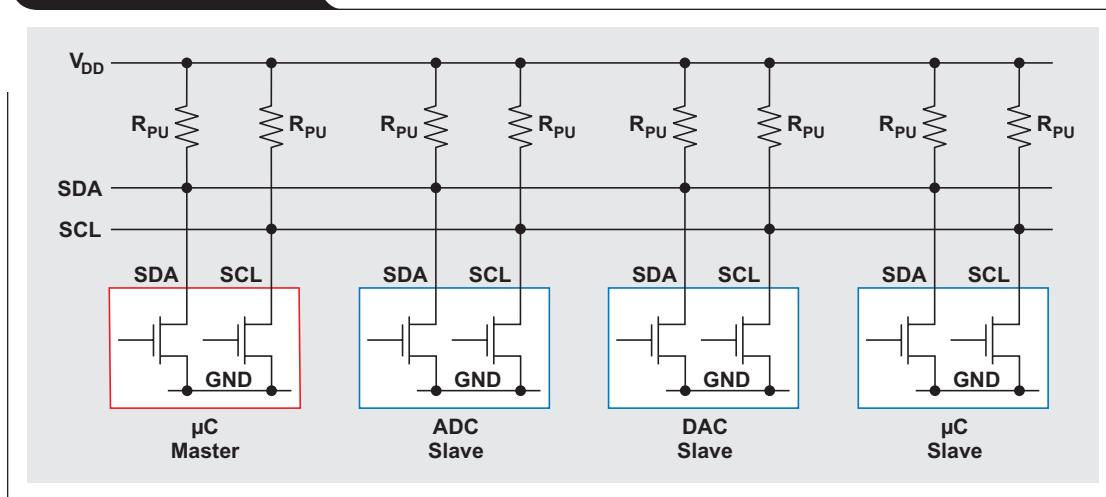

**Figure 2. Timing diagram of a complete data transfer**

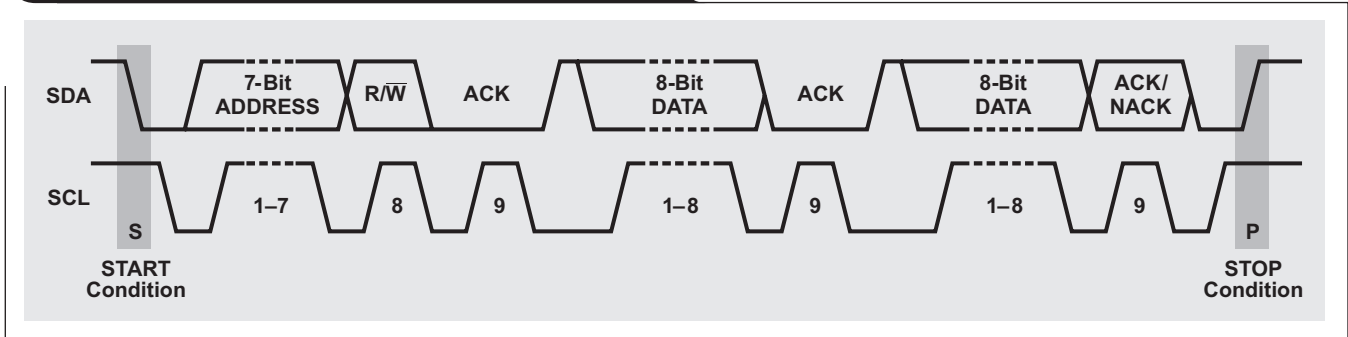

The bus has two roles for nodes: master and slave. A master issues the clock and slave addresses and also initiates and ends data transactions. A slave receives the clock and addresses and responds to requests from the master. Figure 2 shows a typical data transfer between master and slave.

The master initiates a transaction by creating a START condition, then transmits the 7-bit address of the slave it wishes to communicate with. This is followed by a single READ/WRITE (R/W) bit, representing whether the master wishes to write to “0” or to read from “1,” the slave. The master then releases the SDA line to allow the slave to acknowledge the receipt of data.

The slave responds with an acknowledge (ACK) bit by pulling SDA low during the entire high time of the ninth clock pulse on SCL. Then the master continues in either transmit or receive mode (according to the R/W bit sent), while the slave continues in the complementary mode (receive or transmit, respectively).

The address and 8-bit data bytes are sent with the most significant bit (MSB) first. The START bit is indicated by a high-to-low transition of SDA while SCL is high. The STOP condition is created by a low-to-high transition of SDA while SCL is high.

If the master writes to a slave, it repeatedly sends a byte to the slave, which sends an ACK bit for each byte received. In this case, the master is in master-transmit mode and the slave is in slave-receive mode.

If the master reads from a slave, it repeatedly receives a byte from the slave while sending an ACK bit to acknowledge the receipt of every byte but the last one (see Figure 3). In this situation the master is in master-receive mode and the slave is in slave-transmit mode.

The master ends the transmission with a STOP bit or may send another START bit to maintain bus control for further transfers.

When writing to a slave, a master mainly operates in transmit mode and changes to receive mode only when receiving acknowledgment from the slave.

When reading from a slave, the master starts in transmit mode and then changes to receive mode after sending a READ request (R/W bit = 1) to the slave. The slave continues in the complementary mode until the end of a transaction.

Note that the master ends a reading sequence by not acknowledging the last byte received—i.e., by sending a NACK. This procedure resets the slave state machine and allows the master to send the STOP command.

**Figure 3. Changes in transmit/receive modes during a data transfer**

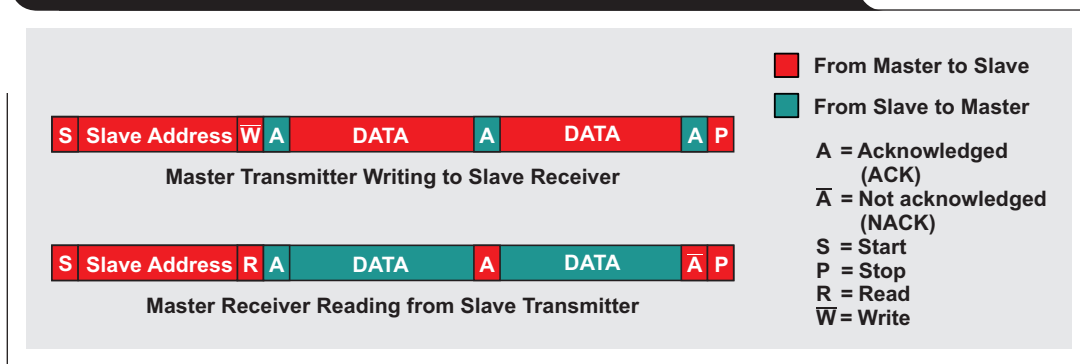
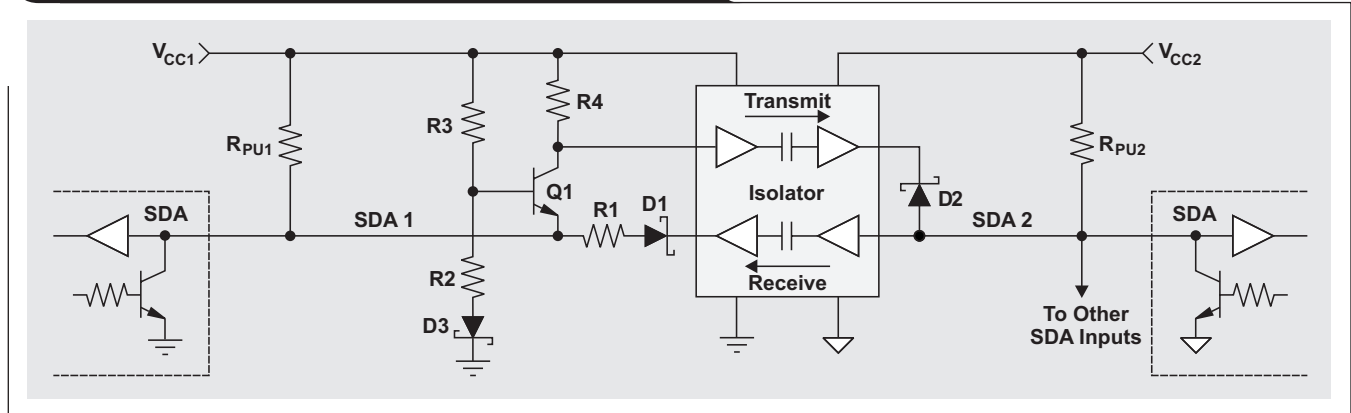


Figure 4. Isolating an I<sup>2</sup>C line by using a digital isolator

### Isolator design

Isolating an I<sup>2</sup>C signal path by using standard digital isolators requires splitting the half-duplex line into separate transmit and receive paths and converting the isolator's push-pull outputs into open-collector outputs via Schottky diodes (Figure 4). To prevent a transmitted signal from feeding back to its source, a comparator function is implemented that detects the direction of the signal flow and switches the signal paths accordingly.

Transistor Q1 and its surrounding resistor network provide the comparator function. Since the dominant switching level in I<sup>2</sup>C is logic low, the base of Q1 is so biased that a low level applied to SDA1 turns the transistor on, and a low level sent from SDA2 keeps Q1 at high impedance. While the R3/R2 voltage divider primarily determines the biasing, diode D3 provides temperature compensation. To prevent SDA2 from turning Q1 on, the low-level output at D1 is raised by a voltage drop across R1, which raises Q1's emitter potential,  $V_E$ , and decreases the base-emitter voltage below the minimum turn-on level. However, care must be taken to maintain  $V_E$  below the minimum input high-level threshold of SDA1, which the I<sup>2</sup>C specification lists as  $V_{IHmin} = 0.3 \times V_{CC}$ .

So, when the I<sup>2</sup>C Bus at SDA2 is pulled low, the low state passing in receive direction causes a voltage increase at

SDA1 that is just enough to block Q1 but well below  $V_{IHmin}$ , thus presenting a valid low for an I<sup>2</sup>C input. At the same time, R4 provides a logic high to the isolator input in transmit direction, preventing diode D2 from conducting. Once SDA2 is released and returns to the level of  $V_{CC2}$ , SDA1 follows after one propagation delay through the isolator. When the isolator is driven from the bus side (SDA2), the added signal delays for both the falling and the rising edges mainly consist of only one propagation delay through the isolator.

In the opposite direction, when SDA1 is pulled low, its maximum low-level output,  $V_{OLmax}$ , is significantly lower than  $V_E$  and causes Q1 to conduct. The low-state signal passing through the isolator in transmit direction forward biases D2, and SDA2 goes low. However, when SDA1 is released, its voltage cannot return to the level of  $V_{CC1}$  immediately due to the remaining low-level signal at SDA2. Instead, SDA1 rises to the necessary  $V_E$  potential that blocks Q1, and it will stay at this level until a high-impedance Q1 allows R4 to provide a logic high to the isolator input, thus releasing SDA2 and D1. Only then will SDA1 be able to return to the level of  $V_{CC1}$ .

When the isolator is driven from the device side (SDA1), the added signal delays for both edges increase due to the involvement of the comparator function.



# Index of Articles

Title	Issue	Page	Lit. No.
<b>Data Acquisition</b>			
Aspects of data acquisition system design	August 1999	1	SLYT191
Low-power data acquisition sub-system using the TI TLV1572	August 1999	4	SLYT192
Evaluating operational amplifiers as input amplifiers for A-to-D converters	August 1999	7	SLYT193
Precision voltage references	November 1999	1	SLYT183
Techniques for sampling high-speed graphics with lower-speed A/D converters	November 1999	5	SLYT184
A methodology of interfacing serial A-to-D converters to DSPs	February 2000	1	SLYT175
The operation of the SAR-ADC based on charge redistribution	February 2000	10	SLYT176
The design and performance of a precision voltage reference circuit for 14-bit and 16-bit A-to-D and D-to-A converters	May 2000	1	SLYT168
Introduction to phase-locked loop system modeling	May 2000	5	SLYT169
New DSP development environment includes data converter plug-ins	August 2000	1	SLYT158
Higher data throughput for DSP analog-to-digital converters	August 2000	5	SLYT159
Efficiently interfacing serial data converters to high-speed DSPs	August 2000	10	SLYT160
Smallest DSP-compatible ADC provides simplest DSP interface	November 2000	1	SLYT148
Hardware auto-identification and software auto-configuration for the TLV320AIC10 DSP Codec — a “plug-and-play” algorithm	November 2000	8	SLYT149
Using quad and octal ADCs in SPI mode	November 2000	15	SLYT150
Building a simple data acquisition system using the TMS320C31 DSP	February 2001	1	SLYT136
Using SPI synchronous communication with data converters — interfacing the MSP430F149 and TLV5616	February 2001	7	SLYT137
A/D and D/A conversion of PC graphics and component video signals, Part 1: Hardware	February 2001	11	SLYT138
A/D and D/A conversion of PC graphics and component video signals, Part 2: Software and control	July 2001	5	SLYT129
Intelligent sensor system maximizes battery life: Interfacing the MSP430F123 Flash MCU, ADS7822, and TPS60311	1Q, 2002	5	SLYT123
SHDSL AFE1230 application	2Q, 2002	5	SLYT114
Synchronizing non-FIFO variations of the THS1206	2Q, 2002	12	SLYT115
Adjusting the A/D voltage reference to provide gain	3Q, 2002	5	SLYT109
MSC1210 debugging strategies for high-precision smart sensors	3Q, 2002	7	SLYT110
Using direct data transfer to maximize data acquisition throughput	3Q, 2002	14	SLYT111
Interfacing op amps and analog-to-digital converters	4Q, 2002	5	SLYT104
ADS82x ADC with non-uniform sampling clock	4Q, 2003	5	SLYT089
Calculating noise figure and third-order intercept in ADCs	4Q, 2003	11	SLYT090
Evaluation criteria for ADSL analog front end	4Q, 2003	16	SLYT091
Two-channel, 500-kSPS operation of the ADS8361	1Q, 2004	5	SLYT082
ADS809 analog-to-digital converter with large input pulse signal	1Q, 2004	8	SLYT083
Streamlining the mixed-signal path with the signal-chain-on-chip MSP430F169	3Q, 2004	5	SLYT078
Supply voltage measurement and ADC PSRR improvement in MSC12xx devices	1Q, 2005	5	SLYT073
14-bit, 125-MSPS ADS5500 evaluation	1Q, 2005	13	SLYT074
Clocking high-speed data converters	1Q, 2005	20	SLYT075
Implementation of 12-bit delta-sigma DAC with MSC12xx controller	1Q, 2005	27	SLYT076
Using resistive touch screens for human/machine interface	3Q, 2005	5	SLYT209A
Simple DSP interface for ADS784x/834x ADCs	3Q, 2005	10	SLYT210
Operating multiple oversampling data converters	4Q, 2005	5	SLYT222
Low-power, high-intercept interface to the ADS5424 14-bit, 105-MSPS converter for undersampling applications	4Q, 2005	10	SLYT223
Understanding and comparing datasheets for high-speed ADCs	1Q, 2006	5	SLYT231
Matching the noise performance of the operational amplifier to the ADC	2Q, 2006	5	SLYT237
Using the ADS8361 with the MSP430 USI port	3Q, 2006	5	SLYT244
Clamp function of high-speed ADC THS1041	4Q, 2006	5	SLYT253
Conversion latency in delta-sigma converters	2Q, 2007	5	SLYT264
Calibration in touch-screen systems	3Q, 2007	5	SLYT277
Using a touch-screen controller's auxiliary inputs	4Q, 2007	5	SLYT283

Title	Issue	Page	Lit. No.
<b>Data Acquisition (Continued)</b>			
Understanding the pen-interrupt (PENIRQ) operation of touch-screen controllers	2Q, 2008	5	SLYT292
A DAC for all precision occasions	3Q, 2008	5	SLYT300
Stop-band limitations of the Sallen-Key low-pass filter	4Q, 2008	5	SLYT306
How the voltage reference affects ADC performance, Part 1	2Q, 2009	5	SLYT331
Impact of sampling-clock spurs on ADC performance	3Q, 2009	5	SLYT338
How the voltage reference affects ADC performance, Part 2	3Q, 2009	13	SLYT339
How the voltage reference affects ADC performance, Part 3	4Q, 2009	5	SLYT355
How digital filters affect analog audio-signal levels	2Q, 2010	5	SLYT375
Clock jitter analyzed in the time domain, Part 1	3Q, 2010	5	SLYT379
Clock jitter analyzed in the time domain, Part 2	4Q, 2010	5	SLYT389
The IBIS model: A conduit into signal-integrity analysis, Part 1	4Q, 2010	11	SLYT390
The IBIS model, Part 2: Determining the total quality of an IBIS model	1Q, 2011	5	SLYT400
<b>Power Management</b>			
Stability analysis of low-dropout linear regulators with a PMOS pass element	August 1999	10	SLYT194
Extended output voltage adjustment (0 V to 3.5 V) using the TI TPS5210	August 1999	13	SLYT195
Migrating from the TI TL770x to the TI TLC770x	August 1999	14	SLYT196
TI TPS5602 for powering TI's DSP	November 1999	8	SLYT185
Synchronous buck regulator design using the TI TPS5211 high-frequency hysteretic controller	November 1999	10	SLYT186
Understanding the stable range of equivalent series resistance of an LDO regulator	November 1999	14	SLYT187
Power supply solutions for TI DSPs using synchronous buck converters	February 2000	12	SLYT177
Powering Celeron-type microprocessors using TI's TPS5210 and TPS5211 controllers	February 2000	20	SLYT178
Simple design of an ultra-low-ripple DC/DC boost converter with TPS60100 charge pump	May 2000	11	SLYT170
Low-cost, minimum-size solution for powering future-generation Celeron™-type processors with peak currents up to 26 A	May 2000	14	SLYT171
Advantages of using PMOS-type low-dropout linear regulators in battery applications	August 2000	16	SLYT161
Optimal output filter design for microprocessor or DSP power supply	August 2000	22	SLYT162
Understanding the load-transient response of LDOs	November 2000	19	SLYT151
Comparison of different power supplies for portable DSP solutions working from a single-cell battery	November 2000	24	SLYT152
Optimal design for an interleaved synchronous buck converter under high-slew-rate, load-current transient conditions	February 2001	15	SLYT139
–48-V/+48-V hot-swap applications	February 2001	20	SLYT140
Power supply solution for DDR bus termination	July 2001	9	SLYT130
Runtime power control for DSPs using the TPS62000 buck converter	July 2001	15	SLYT131
Power control design key to realizing InfiniBand™ benefits	1Q, 2002	10	SLYT124
Comparing magnetic and piezoelectric transformer approaches in CCFL applications	1Q, 2002	12	SLYT125
Why use a wall adapter for ac input power?	1Q, 2002	18	SLYT126
SWIFT™ Designer power supply design program	2Q, 2002	15	SLYT116
Optimizing the switching frequency of ADSL power supplies	2Q, 2002	23	SLYT117
Powering electronics from the USB port	2Q, 2002	28	SLYT118
Using the UCC3580-1 controller for highly efficient 3.3-V/100-W isolated supply design	4Q, 2002	8	SLYT105
Power conservation options with dynamic voltage scaling in portable DSP designs	4Q, 2002	12	SLYT106
Understanding piezoelectric transformers in CCFL backlight applications	4Q, 2002	18	SLYT107
Load-sharing techniques: Paralleling power modules with overcurrent protection	1Q, 2003	5	SLYT100
Using the TPS61042 white-light LED driver as a boost converter	1Q, 2003	7	SLYT101
Auto-Track™ voltage sequencing simplifies simultaneous power-up and power-down	3Q, 2003	5	SLYT095
Soft-start circuits for LDO linear regulators	3Q, 2003	10	SLYT096
UCC28517 100-W PFC power converter with 12-V, 8-W bias supply, Part 1	3Q, 2003	13	SLYT097
UCC28517 100-W PFC power converter with 12-V, 8-W bias supply, Part 2	4Q, 2003	21	SLYT092
LED-driver considerations	1Q, 2004	14	SLYT084
Tips for successful power-up of today's high-performance FPGAs	3Q, 2004	11	SLYT079
A better bootstrap/bias supply circuit	1Q, 2005	33	SLYT077
Understanding noise in linear regulators	2Q, 2005	5	SLYT201
Understanding power supply ripple rejection in linear regulators	2Q, 2005	8	SLYT202
Miniature solutions for voltage isolation	3Q, 2005	13	SLYT211

Title	Issue	Page	Lit. No.
<b>Power Management (Continued)</b>			
New power modules improve surface-mount manufacturability	3Q, 2005	18	SLYT212
Li-ion switching charger integrates power FETs	4Q, 2005	19	SLYT224
TLC5940 dot correction compensates for variations in LED brightness	4Q, 2005	21	SLYT225
Powering today's multi-rail FPGAs and DSPs, Part 1	1Q, 2006	9	SLYT232
TPS79918 RF LDO supports migration to StrataFlash® Embedded Memory (P30)	1Q, 2006	14	SLYT233
Practical considerations when designing a power supply with the TPS6211x	1Q, 2006	17	SLYT234
TLC5940 PWM dimming provides superior color quality in LED video displays	2Q, 2006	10	SLYT238
Wide-input dc/dc modules offer maximum design flexibility	2Q, 2006	13	SLYT239
Powering today's multi-rail FPGAs and DSPs, Part 2	2Q, 2006	18	SLYT240
TPS61059 powers white-light LED as photoflash or movie light	3Q, 2006	8	SLYT245
TPS65552A powers portable photoflash	3Q, 2006	10	SLYT246
Single-chip bq2403x power-path manager charges battery while powering system	3Q, 2006	12	SLYT247
Complete battery-pack design for one- or two-cell portable applications	3Q, 2006	14	SLYT248
A 3-A, 1.2-V <sub>OUT</sub> linear regulator with 80% efficiency and P <sub>LOST</sub> < 1 W	4Q, 2006	10	SLYT254
bq25012 single-chip, Li-ion charger and dc/dc converter for Bluetooth® headsets	4Q, 2006	13	SLYT255
Fully integrated TPS6300x buck-boost converter extends Li-ion battery life	4Q, 2006	15	SLYT256
Selecting the correct IC for power-supply applications	1Q, 2007	5	SLYT259
LDO white-LED driver TPS7510x provides incredibly small solution size	1Q, 2007	9	SLYT260
Power management for processor core voltage requirements	1Q, 2007	11	SLYT261
Enhanced-safety, linear Li-ion battery charger with thermal regulation and input overvoltage protection	2Q, 2007	8	SLYT269
Current balancing in four-pair, high-power PoE applications	2Q, 2007	11	SLYT270
Power-management solutions for telecom systems improve performance, cost, and size	3Q, 2007	10	SLYT278
TPS6108x: A boost converter with extreme versatility	3Q, 2007	14	SLYT279
Get low-noise, low-ripple, high-PSRR power with the TPS717xx	3Q, 2007	17	SLYT280
Simultaneous power-down sequencing with the TPS74x01 family of linear regulators	3Q, 2007	20	SLYT281
Driving a WLED does not always require 4 V	4Q, 2007	9	SLYT284
Host-side gas-gauge-system design considerations for single-cell handheld applications	4Q, 2007	12	SLYT285
Using a buck converter in an inverting buck-boost topology	4Q, 2007	16	SLYT286
Understanding output voltage limitations of DC/DC buck converters	2Q, 2008	11	SLYT293
Battery-charger front-end IC improves charging-system safety	2Q, 2008	14	SLYT294
New current-mode PWM controllers support boost, flyback, SEPIC, and LED-driver applications	3Q, 2008	9	SLYT302
Getting the most battery life from portable systems	4Q, 2008	8	SLYT307
Compensating and measuring the control loop of a high-power LED driver	4Q, 2008	14	SLYT308
Designing DC/DC converters based on SEPIC topology	4Q, 2008	18	SLYT309
Paralleling power modules for high-current applications	1Q, 2009	5	SLYT320
Improving battery safety, charging, and fuel gauging in portable media applications	1Q, 2009	9	SLYT321
Cell balancing buys extra run time and battery life	1Q, 2009	14	SLYT322
Using a portable-power boost converter in an isolated flyback application	1Q, 2009	19	SLYT323
Taming linear-regulator inrush currents	2Q, 2009	9	SLYT332
Designing a linear Li-Ion battery charger with power-path control	2Q, 2009	12	SLYT333
Selecting the right charge-management solution	2Q, 2009	18	SLYT334
Reducing radiated EMI in WLED drivers	3Q, 2009	17	SLYT340
Using power solutions to extend battery life in MSP430 applications	4Q, 2009	10	SLYT356
Designing a multichemistry battery charger	4Q, 2009	13	SLYT357
Efficiency of synchronous versus nonsynchronous buck converters	4Q, 2009	15	SLYT358
Fuel-gauging considerations in battery backup storage systems	1Q, 2010	5	SLYT364
Li-ion battery-charger solutions for JEITA compliance	1Q, 2010	8	SLYT365
Power-supply design for high-speed ADCs	1Q, 2010	12	SLYT366
Discrete design of a low-cost isolated 3.3- to 5-V DC/DC converter	2Q, 2010	12	SLYT371
Designing DC/DC converters based on ZETA topology	2Q, 2010	16	SLYT372
Coupled inductors broaden DC/DC converter usage	3Q, 2010	10	SLYT380
Computing power going "Platinum"	3Q, 2010	13	SLYT382
A low-cost, non-isolated AC/DC buck converter with no transformer	4Q, 2010	16	SLYT391
Save power with a soft Zener clamp	4Q, 2010	19	SLYT392
An introduction to the Wireless Power Consortium standard and TI's compliant solutions	1Q, 2011	10	SLYT401

Title	Issue	Page	Lit. No.
<b>Power Management (Continued)</b>			
Fine-tuning TI's Impedance Track™ battery fuel gauge with LiFePO <sub>4</sub> cells in shallow-discharge applications . . . . .	1Q, 2011 . . . . .	13	SLYT402
<b>Interface (Data Transmission)</b>			
TIA/EIA-568A Category 5 cables in low-voltage differential signaling (LVDS) . . . . .	August 1999 . . . . .	16	SLYT197
Keep an eye on the LVDS input levels . . . . .	November 1999 . . . . .	17	SLYT188
Skew definition and jitter analysis . . . . .	February 2000 . . . . .	29	SLYT179
LVDS receivers solve problems in non-LVDS applications . . . . .	February 2000 . . . . .	33	SLYT180
LVDS: The ribbon cable connection . . . . .	May 2000 . . . . .	19	SLYT172
Performance of LVDS with different cables . . . . .	August 2000 . . . . .	30	SLYT163
A statistical survey of common-mode noise . . . . .	November 2000 . . . . .	30	SLYT153
The Active Fail-Safe feature of the SN65LVDS32A . . . . .	November 2000 . . . . .	35	SLYT154
The SN65LVDS33/34 as an ECL-to-LVTTL converter . . . . .	July 2001 . . . . .	19	SLYT132
Power consumption of LVPECL and LVDS . . . . .	1Q, 2002 . . . . .	23	SLYT127
Estimating available application power for Power-over-Ethernet applications . . . . .	1Q, 2004 . . . . .	18	SLYT085
The RS-485 unit load and maximum number of bus connections . . . . .	1Q, 2004 . . . . .	21	SLYT086
Failsafe in RS-485 data buses . . . . .	3Q, 2004 . . . . .	16	SLYT080
Maximizing signal integrity with M-LVDS backplanes . . . . .	2Q, 2005 . . . . .	11	SLYT203
Device spacing on RS-485 buses . . . . .	2Q, 2006 . . . . .	25	SLYT241
Improved CAN network security with TI's SN65HVD1050 transceiver . . . . .	3Q, 2006 . . . . .	17	SLYT249
Detection of RS-485 signal loss . . . . .	4Q, 2006 . . . . .	18	SLYT257
Enabling high-speed USB OTG functionality on TI DSPs . . . . .	2Q, 2007 . . . . .	18	SLYT271
When good grounds turn bad— isolate! . . . . .	3Q, 2008 . . . . .	11	SLYT298
Cascading of input serializers boosts channel density for digital inputs . . . . .	3Q, 2008 . . . . .	16	SLYT301
RS-485: Passive failsafe for an idle bus . . . . .	1Q, 2009 . . . . .	22	SLYT324
Message priority inversion on a CAN bus . . . . .	1Q, 2009 . . . . .	25	SLYT325
Designing with digital isolators . . . . .	2Q, 2009 . . . . .	21	SLYT335
Magnetic-field immunity of digital capacitive isolators . . . . .	3Q, 2010 . . . . .	19	SLYT381
Interfacing high-voltage applications to low-power controllers . . . . .	4Q, 2010 . . . . .	20	SLYT393
Designing an isolated I <sup>2</sup> C Bus® interface by using digital isolators . . . . .	1Q, 2011 . . . . .	17	SLYT403
<b>Amplifiers: Audio</b>			
Reducing the output filter of a Class-D amplifier . . . . .	August 1999 . . . . .	19	SLYT198
Power supply decoupling and audio signal filtering for the Class-D audio power amplifier . . . . .	August 1999 . . . . .	24	SLYT199
PCB layout for the TPA005D1x and TPA032D0x Class-D APAs . . . . .	February 2000 . . . . .	39	SLYT182
An audio circuit collection, Part 1 . . . . .	November 2000 . . . . .	39	SLYT155
1.6- to 3.6-volt BTL speaker driver reference design . . . . .	February 2001 . . . . .	23	SLYT141
Notebook computer upgrade path for audio power amplifiers . . . . .	February 2001 . . . . .	27	SLYT142
An audio circuit collection, Part 2 . . . . .	February 2001 . . . . .	41	SLYT145
An audio circuit collection, Part 3 . . . . .	July 2001 . . . . .	34	SLYT134
Audio power amplifier measurements . . . . .	July 2001 . . . . .	40	SLYT135
Audio power amplifier measurements, Part 2 . . . . .	1Q, 2002 . . . . .	26	SLYT128
Precautions for connecting APA outputs to other devices . . . . .	2Q, 2010 . . . . .	22	SLYT373
<b>Amplifiers: Op Amps</b>			
Single-supply op amp design . . . . .	November 1999 . . . . .	20	SLYT189
Reducing crosstalk of an op amp on a PCB . . . . .	November 1999 . . . . .	23	SLYT190
Matching operational amplifier bandwidth with applications . . . . .	February 2000 . . . . .	36	SLYT181
Sensor to ADC — analog interface design . . . . .	May 2000 . . . . .	22	SLYT173
Using a decompensated op amp for improved performance . . . . .	May 2000 . . . . .	26	SLYT174
Design of op amp sine wave oscillators . . . . .	August 2000 . . . . .	33	SLYT164
Fully differential amplifiers . . . . .	August 2000 . . . . .	38	SLYT165
The PCB is a component of op amp design . . . . .	August 2000 . . . . .	42	SLYT166
Reducing PCB design costs: From schematic capture to PCB layout . . . . .	August 2000 . . . . .	48	SLYT167
Thermistor temperature transducer-to-ADC application . . . . .	November 2000 . . . . .	44	SLYT156
Analysis of fully differential amplifiers . . . . .	November 2000 . . . . .	48	SLYT157
Fully differential amplifiers applications: Line termination, driving high-speed ADCs, and differential transmission lines . . . . .	February 2001 . . . . .	32	SLYT143



Title	Issue	Page	Lit. No.
<b>Amplifiers: Op Amps (Continued)</b>			
Pressure transducer-to-ADC application	February 2001	38	SLYT144
Frequency response errors in voltage feedback op amps	February 2001	48	SLYT146
Designing for low distortion with high-speed op amps	July 2001	25	SLYT133
Fully differential amplifier design in high-speed data acquisition systems	2Q, 2002	35	SLYT119
Worst-case design of op amp circuits	2Q, 2002	42	SLYT120
Using high-speed op amps for high-performance RF design, Part 1	2Q, 2002	46	SLYT121
Using high-speed op amps for high-performance RF design, Part 2	3Q, 2002	21	SLYT112
FilterPro™ low-pass design tool	3Q, 2002	24	SLYT113
Active output impedance for ADSL line drivers	4Q, 2002	24	SLYT108
RF and IF amplifiers with op amps	1Q, 2003	9	SLYT102
Analyzing feedback loops containing secondary amplifiers	1Q, 2003	14	SLYT103
Video switcher using high-speed op amps	3Q, 2003	20	SLYT098
Expanding the usability of current-feedback amplifiers	3Q, 2003	23	SLYT099
Calculating noise figure in op amps	4Q, 2003	31	SLYT094
Op amp stability and input capacitance	1Q, 2004	24	SLYT087
Integrated logarithmic amplifiers for industrial applications	1Q, 2004	28	SLYT088
Active filters using current-feedback amplifiers	3Q, 2004	21	SLYT081
Auto-zero amplifiers ease the design of high-precision circuits	2Q, 2005	19	SLYT204
So many amplifiers to choose from: Matching amplifiers to applications	3Q, 2005	24	SLYT213
Getting the most out of your instrumentation amplifier design	4Q, 2005	25	SLYT226
High-speed notch filters	1Q, 2006	19	SLYT235
Low-cost current-shunt monitor IC revives moving-coil meter design	2Q, 2006	27	SLYT242
Accurately measuring ADC driving-circuit settling time	1Q, 2007	14	SLYT262
New zero-drift amplifier has an $I_Q$ of 17 $\mu$ A	2Q, 2007	22	SLYT272
A new filter topology for analog high-pass filters	3Q, 2008	18	SLYT299
Input impedance matching with fully differential amplifiers	4Q, 2008	24	SLYT310
A dual-polarity, bidirectional current-shunt monitor	4Q, 2008	29	SLYT311
Output impedance matching with fully differential operational amplifiers	1Q, 2009	29	SLYT326
Using fully differential op amps as attenuators, Part 1: Differential bipolar input signals	2Q, 2009	33	SLYT336
Using fully differential op amps as attenuators, Part 2: Single-ended bipolar input signals	3Q, 2009	21	SLYT341
Interfacing op amps to high-speed DACs, Part 1: Current-sinking DACs	3Q, 2009	24	SLYT342
Using the infinite-gain, MFB filter topology in fully differential active filters	3Q, 2009	33	SLYT343
Using fully differential op amps as attenuators, Part 3: Single-ended unipolar input signals	4Q, 2009	19	SLYT359
Interfacing op amps to high-speed DACs, Part 2: Current-sourcing DACs	4Q, 2009	23	SLYT360
Operational amplifier gain stability, Part 1: General system analysis	1Q, 2010	20	SLYT367
Signal conditioning for piezoelectric sensors	1Q, 2010	24	SLYT369
Interfacing op amps to high-speed DACs, Part 3: Current-sourcing DACs simplified	1Q, 2010	32	SLYT368
Operational amplifier gain stability, Part 2: DC gain-error analysis	2Q, 2010	24	SLYT374
Operational amplifier gain stability, Part 3: AC gain-error analysis	3Q, 2010	23	SLYT383
Using single-supply fully differential amplifiers with negative input voltages to drive ADCs	4Q, 2010	26	SLYT394
<b>Low-Power RF</b>			
Using the CC2430 and TIMAC for low-power wireless sensor applications: A power-consumption study	2Q, 2008	17	SLYT295
Selecting antennas for low-power wireless applications	2Q, 2008	20	SLYT296
<b>General Interest</b>			
Synthesis and characterization of nickel manganite from different carboxylate precursors for thermistor sensors	February 2001	52	SLYT147
Analog design tools	2Q, 2002	50	SLYT122
Spreadsheet modeling tool helps analyze power- and ground-plane voltage drops to keep core voltages within tolerance	2Q, 2007	29	SLYT273

## TI Worldwide Technical Support

### Internet

#### TI Semiconductor Product Information Center Home Page

support.ti.com

#### TI E2E™ Community Home Page

e2e.ti.com

### Product Information Centers

<b>Americas</b>	Phone	+1(972) 644-5580
<b>Brazil</b>	Phone	0800-891-2616
<b>Mexico</b>	Phone	0800-670-7544
	Fax	+1(972) 927-6377
	Internet/Email	support.ti.com/sc/pic/americas.htm

#### Europe, Middle East, and Africa

Phone	
European Free Call	00800-ASK-TEXAS (00800 275 83927)
International	+49 (0) 8161 80 2121
Russian Support	+7 (4) 95 98 10 701

**Note:** The European Free Call (Toll Free) number is not active in all countries. If you have technical difficulty calling the free call number, please use the international number above.

Fax	+ (49) (0) 8161 80 2045
Internet	support.ti.com/sc/pic/euro.htm
Direct Email	asktexas@ti.com

#### Japan

Phone	Domestic	0120-92-3326
Fax	International	+81-3-3344-5317
	Domestic	0120-81-0036
Internet/Email	International	support.ti.com/sc/pic/japan.htm
	Domestic	www.tij.co.jp/pic

#### Asia

Phone	
International	+91-80-41381665
Domestic	<u>Toll-Free Number</u>
<b>Note:</b> Toll-free numbers do not support mobile and IP phones.	
Australia	1-800-999-084
China	800-820-8682
Hong Kong	800-96-5941
India	1-800-425-7888
Indonesia	001-803-8861-1006
Korea	080-551-2804
Malaysia	1-800-80-3973
New Zealand	0800-446-934
Philippines	1-800-765-7404
Singapore	800-886-1028
Taiwan	0800-006800
Thailand	001-800-886-0010
Fax	+8621-23073686
Email	tiasia@ti.com or ti-china@ti.com
Internet	support.ti.com/sc/pic/asia.htm

**Important Notice:** The products and services of Texas Instruments Incorporated and its subsidiaries described herein are sold subject to TI's standard terms and conditions of sale. Customers are advised to obtain the most current and complete information about TI products and services before placing orders. TI assumes no liability for applications assistance, customer's applications or product designs, software performance, or infringement of patents. The publication of information regarding any other company's products or services does not constitute TI's approval, warranty or endorsement thereof.

A122010

DLP is a registered trademark and Auto-Track, E2E, FilterPro, Impedance Track, and SWIFT are trademarks of Texas Instruments. A123 Systems is a trademark of A123 Systems, Inc. Acrobat and Reader are registered trademarks of Adobe Systems Incorporated. The Bluetooth word mark and logos are owned by the Bluetooth SIG, Inc., and any use of such marks by Texas Instruments is under license. Celeron is a trademark and StrataFlash is a registered trademark of Intel Corporation. I<sup>2</sup>C Bus is a registered trademark of NXP B.V. Corporation. InfiniBand is a service mark of the InfiniBand Trade Association. Linux is a registered trademark of Linus Torvalds. Sun is a registered trademark of Sun Microsystems Inc. ZigBee is a registered trademark of the ZigBee Alliance. All other trademarks are the property of their respective owners.